

TAIWO DAMILOLA


18/ENG05/058

MECHATRONICS


1.) The Zener diode behaves just like a normal general-purpose diode consisting of a silicon PN-junction and when biased in the forward direction, it behaves just like a normal signal diode passing the rated current. However, unlike a conventional diode that blocks any flow of current through itself when reversed biased, the Zener diode begins to conduct in the reverse direction as soon as the reverse voltage reaches a pre-determined value. This is because when the reverse voltage applied across the Zener diode exceeds the rated voltage of the device.

Avalanche Breakdown occurs in the semiconductor depletion layer and a current starts to flow through the diode to limit its increase in voltage.

Zener Diode I-V characteristics curve.

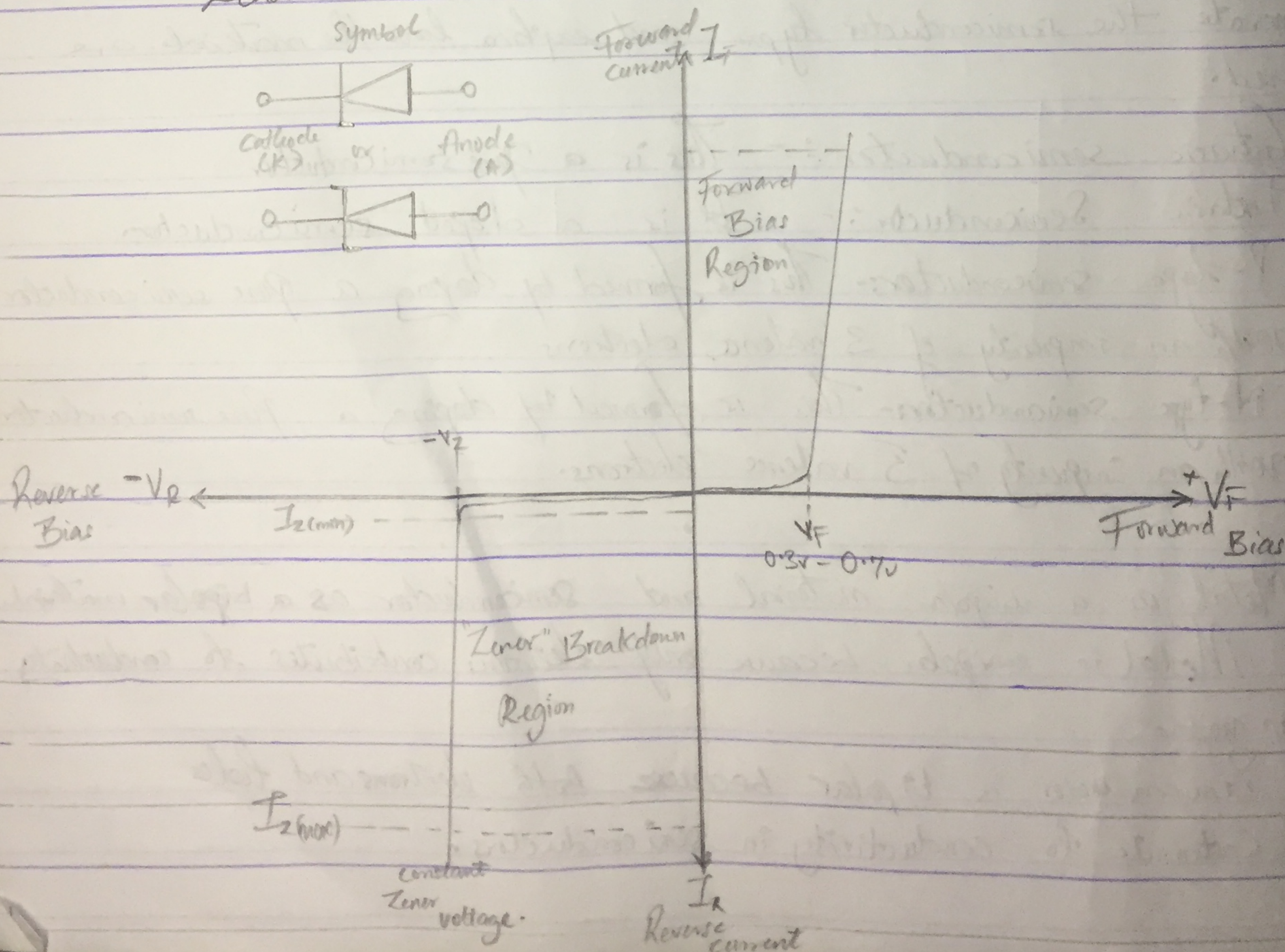

# Zener Circuit Diagram.

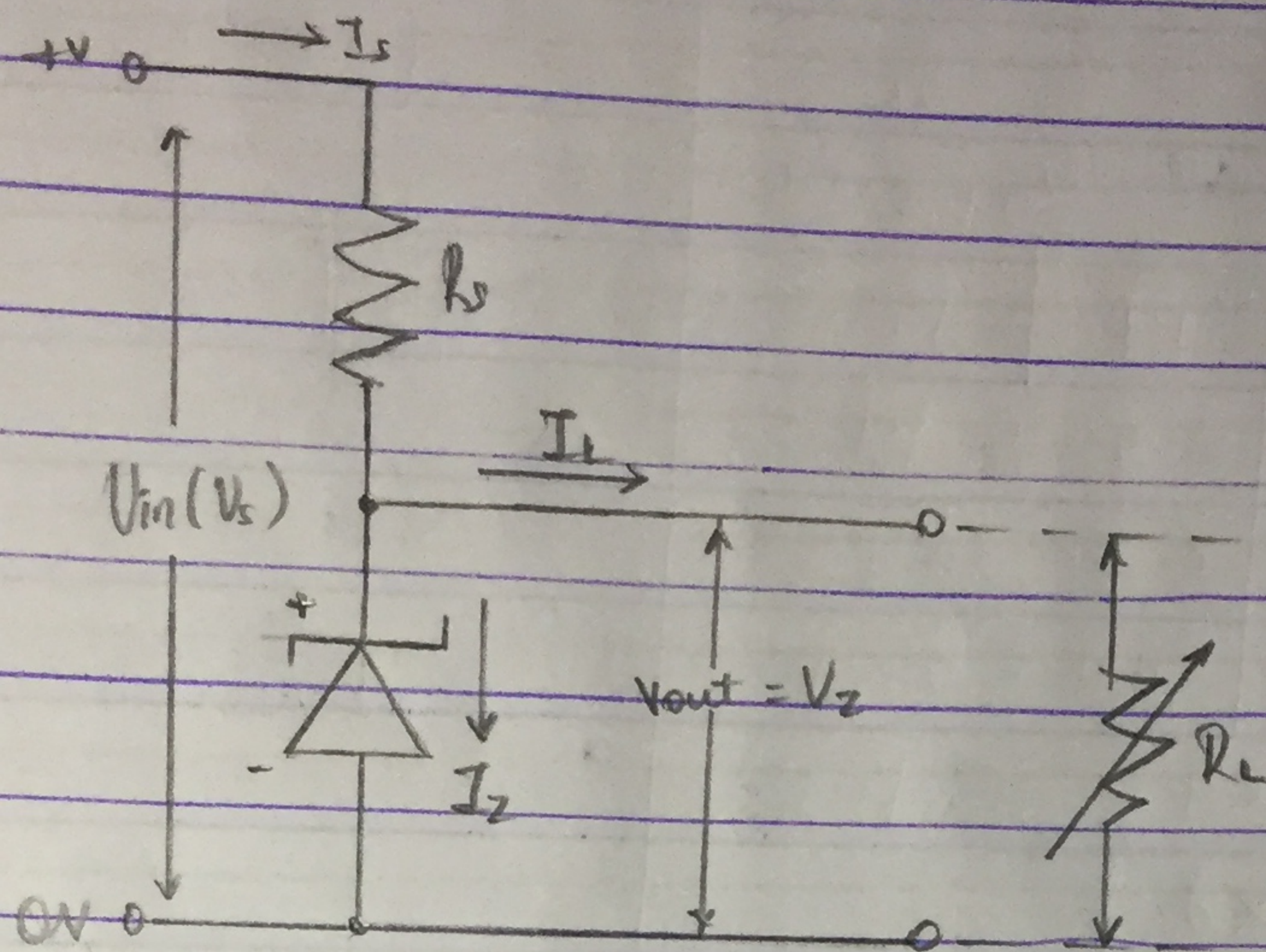

2)  $P = 5W$ ,  $I_{zmax} = 500mA = 0.5A$

$V_{max} = 20$   $R = ?$   $P = IV$

$$R_s = \frac{V_{in} - V_z}{I_{zmax}}$$

$$V_m = \frac{2V_{max}}{\sqrt{2}} = \frac{2 \times 20}{\sqrt{2}} = 12.732V$$

$$V = \frac{P}{I_{zmax}} = \frac{5}{0.5} = 10V$$

$$\therefore R_s = \frac{12.732 - 10}{0.5} = 5.46\Omega$$

ii) When load is  $500\Omega$

$$I_{zmin} = I_{zmax} - I_L$$

$$I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02A$$

$$0.02A = 20mA$$

$$I = 500 - 20 = 480mA$$