

OKORENI ALAMEEN TOMIWA


COMPUTER ENGINEERING

191ENGG02/081


BASIC ELECT

i) A zener diode is a diode similar to the standard PN junction diode but they are specially designed to have a low and specified reverse break down voltage.

SYMBOL

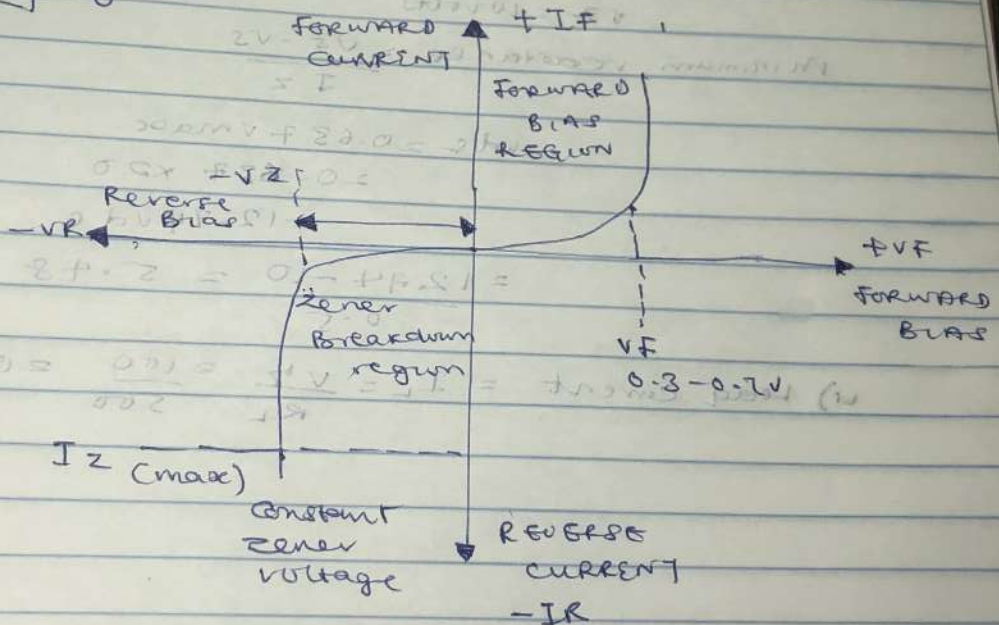

I-V characteristics curve

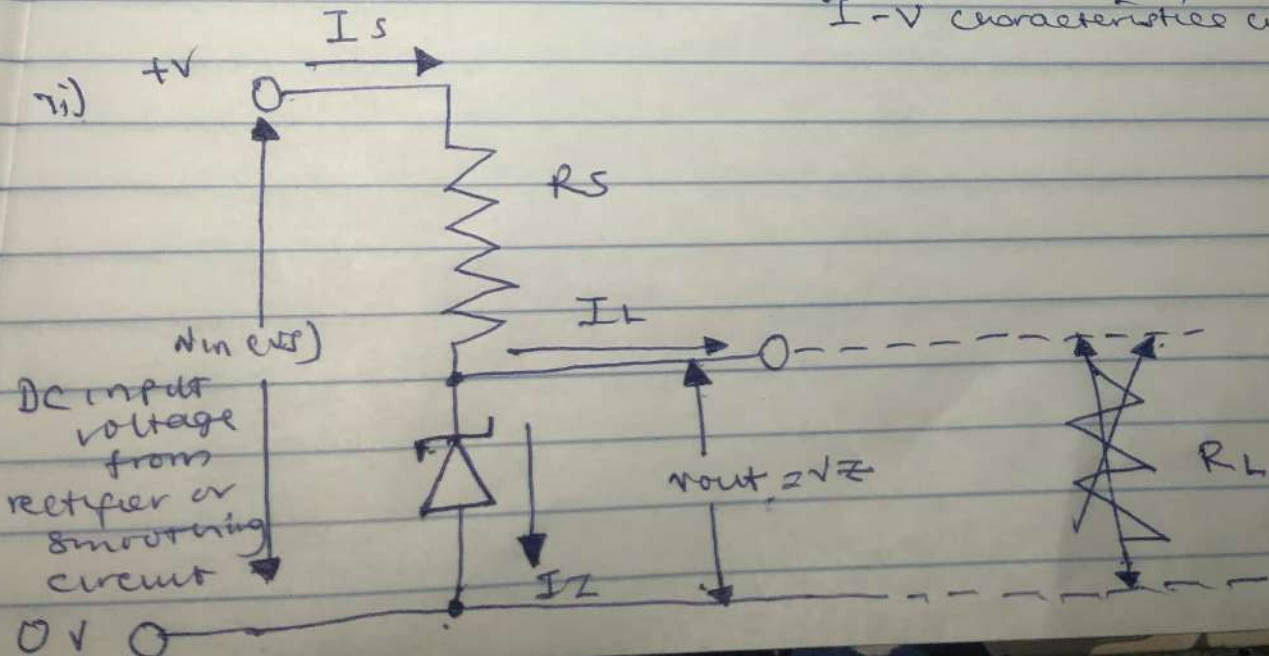

+ R_S = Resistor

+ V_S = voltage source

+ V_{out} = stabilised output voltage

+ R_L = Load resistance

+ I_Z = Load current across Zener diode

i) max power = 5W

$$I_Z = 800\text{mA} = 0.8\text{A}$$

$$20\text{V max } = V_S$$

$$ii) \text{ max current} = \frac{\text{max power}}{\text{voltage}} = \frac{5\text{W}}{V} = 0.5\text{A}$$

$$V_Z = 10\text{V}$$

$$\text{Minimum resistance} = \frac{V_S - V_Z}{I_Z}$$

$$V_S = 20\text{V dc} = 0.637 V_{max}$$

$$= 0.637 \times 20$$

$$= 12.74\text{V dc}$$

$$= \frac{12.74 - 10}{0.5} = 5.48$$

ii) Load current = $I_L = \frac{V_Z}{R_L} = \frac{10}{500} = 0.02\text{A}$

or 20mA

(300mA) 5V

Current
voltage
-IR

I-V Characteristics curve

