

J. G. BOOTH & VALENTINA CHINWANZO

2007/2008



MATRIC NO: 181EN08/023

DEPT: BIOMEDICAL ENGINEERING
ELECT - ELECT


① A zener diode regulator consists of a current limiting resistor R_S connected in "Series" with the input voltage V_S with the zener diode connected in "Parallel" with the load R_L in this reverse biased condition. The stabilised output voltage is always selected to be the same as the breakdown voltage V_Z of the diode.

Symbols

a) Anode

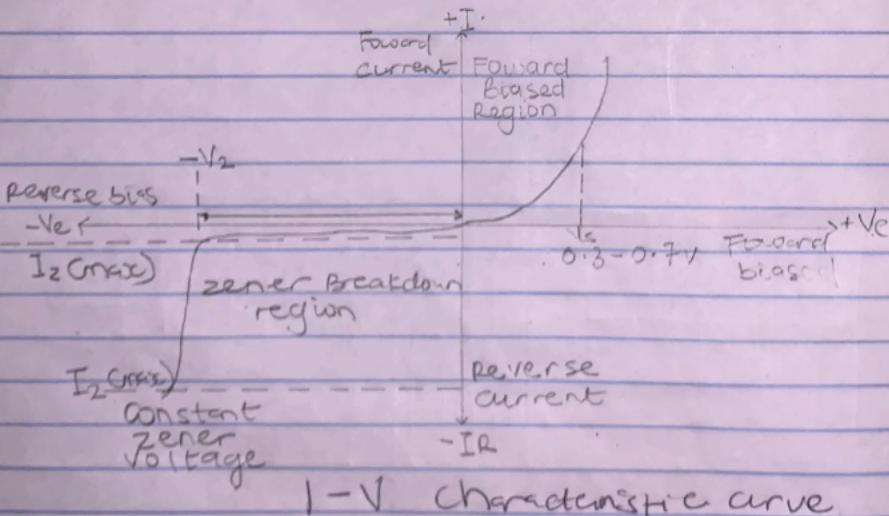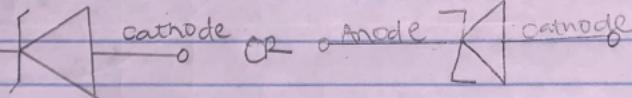

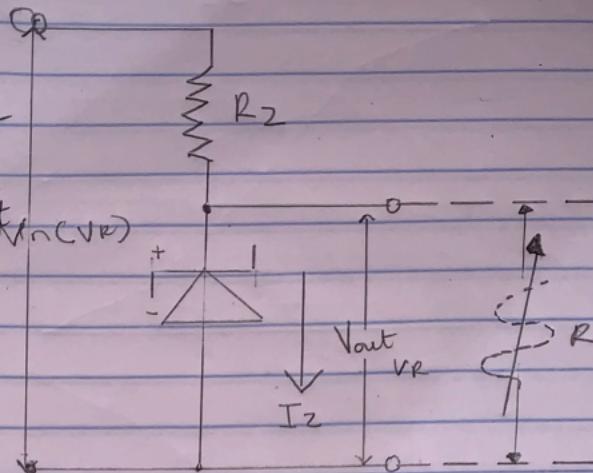Input voltage
in rectifier or
smoothing circuit



Circuit diagram of a zener diode regu

voltage of zener diode (First)

$$V_z = \frac{\text{Watt}}{\text{Current}} = \frac{5}{500 \text{mA}} = 10 \text{V}$$

$$\therefore 500 \text{mA} \approx 0.5 \text{Amperes}$$

$$\therefore \frac{500}{1000} \approx 0.5 \text{A}$$

$$= \frac{5}{0.5} = 10 \text{Volts.}$$

\therefore The minimum value;

$$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500 \text{mA}} = \frac{10}{0.5 \text{A}} = 20 \Omega$$

$$\therefore R_s = 20 \Omega$$

other current is ~~500~~ 500 Ω - resistance.

$$I_z = \frac{V_z}{R_L} = \frac{10}{500 \Omega} = 0.02 \text{Amperes}$$