
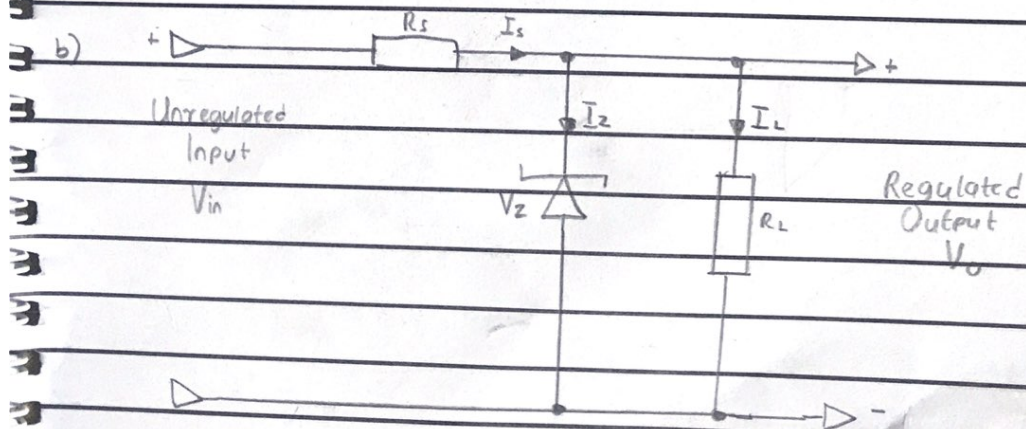


NAME: AMADI-DURU, C. MELVIN

MAT NO: 18/ENGE04/013

DEPT: ELECT/ELECT

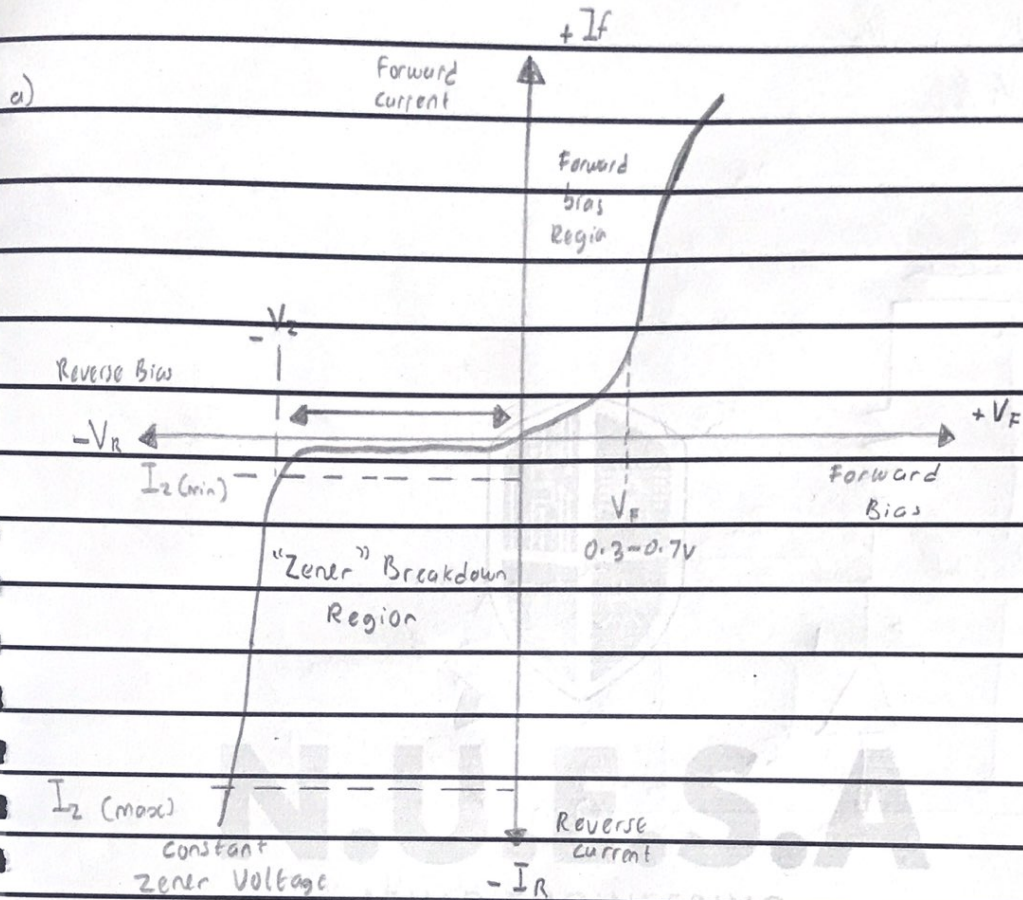

$$V_{in} - V_z = \text{Volt drop}$$


$$I_s = I_{z \text{ min}} + I_{L \text{ max}}$$

$$I_{z \text{ min}}$$


$$V_s = V_{in \text{ min}} - V_z$$

$$R_{s \text{ min}} = V_s / I_s$$

OR

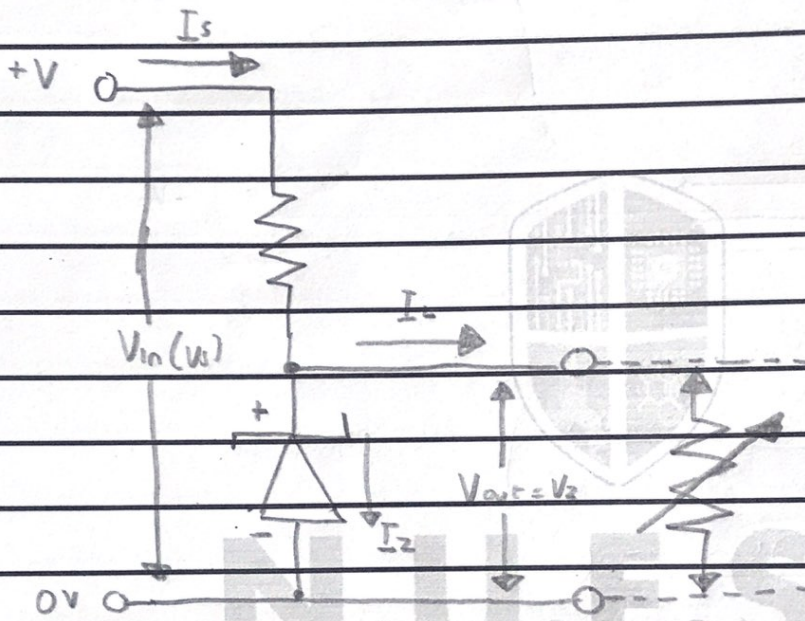

Zener Diode Symbol

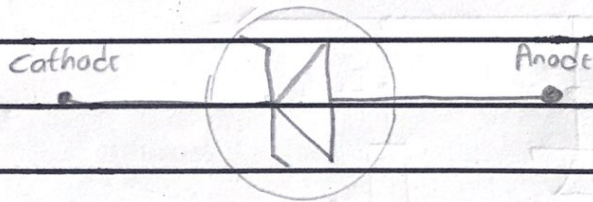

a) minimum value, current 500mA , power = 5W

$$V_z = 10\text{V}, V_{\text{max}} = 20\text{V}$$

$$\text{max current} = \frac{\text{watts}}{\text{voltage}}$$

$$500\text{mA} = \frac{5}{V}$$

$$\text{Voltage} = \frac{5}{500 \times 10^{-3}} = 10\text{ volts}$$

$$V_{dc} = \frac{2V_{\text{max}}}{R} = \frac{2 \times 20}{R} = 12.732\text{V}$$

$$\text{Using } R_s = \frac{V_s - V_z}{I_z} = \frac{12.732 - 10}{500\text{mA}} = 5.46\Omega$$

$$R_s \therefore 5.46\text{ohms}$$

b) $V = IR$

$$I = \frac{V}{R} = \frac{10}{500} = 20\text{mA}$$

$$I_p = I_L + I_z$$


$$500\text{mA} = I_z + 20\text{mA}$$

$$I_z = 500\text{mA} - 20\text{mA} = 480\text{mA}$$

A MADI - DURU, MECUW

18/11/2020

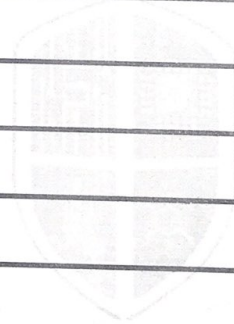Zener diodes are widely used as voltage references & as shunt regulators to regulate the voltage across small circuits. When connected in parallel with a variable voltage source so that it is reverse biased, a Zener diode conducts when the voltage reaches the diode's reverse breakdown voltage.



N.U.E.S.A.
NATIONAL UNIVERSITY OF ENGINEERING AND TECHNOLOGY