
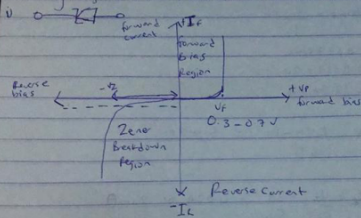


Gafari Okidapo Yemi
18/ENG03/028
Civil Engineering
Basic Elect

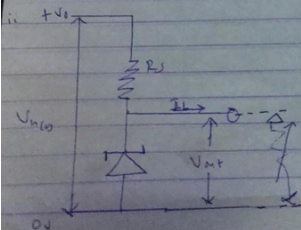A Zener diode is a diode similar to the standard PN junction but they are specially designed to have a low specified reverse breakdown voltage



I - V Characteristic Curve



2) Max power = 5W $I_z = 500mA = 0.5A$, 20V

1) Maximum Current = $\frac{\text{Max Power}}{\text{Voltage}} = \frac{5W}{V} = 0.5A$

$V_z = 10 \text{ volts}$

Minimum resistance = $\frac{V_s - V_z}{I_z}$

$V_{dc} = 0.637V_{ms}$
 $= 0.637 \times 20$
 $= 12.74 V_{dc}$

Minimum resistance = $\frac{12.74 - 10}{0.5} = 5.48\Omega$

1.1) Load Current $I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02A$ or 20mA

$I_z = I_s - I_L$
 $= 500 - 20 = 480mA$

