


KAKAMA FESTA NENG1

18/SC114/025

CIVIL ENGINEERING

i) The Zener diode is like a general purpose signal diode. When biased in the forward direction it behaves just like a normal signal diode, but when a reverse voltage is applied to it, the voltage remains constant for a wide range of currents. It consists of a silicon PN junction. The diode's breakdown voltage of the devices, the diode's breakdown voltage is reached at which point a process called Avalanche Breakdown occurs in the semiconductor depletion layer and a current starts to flow through the diode to limit this increase in voltage.

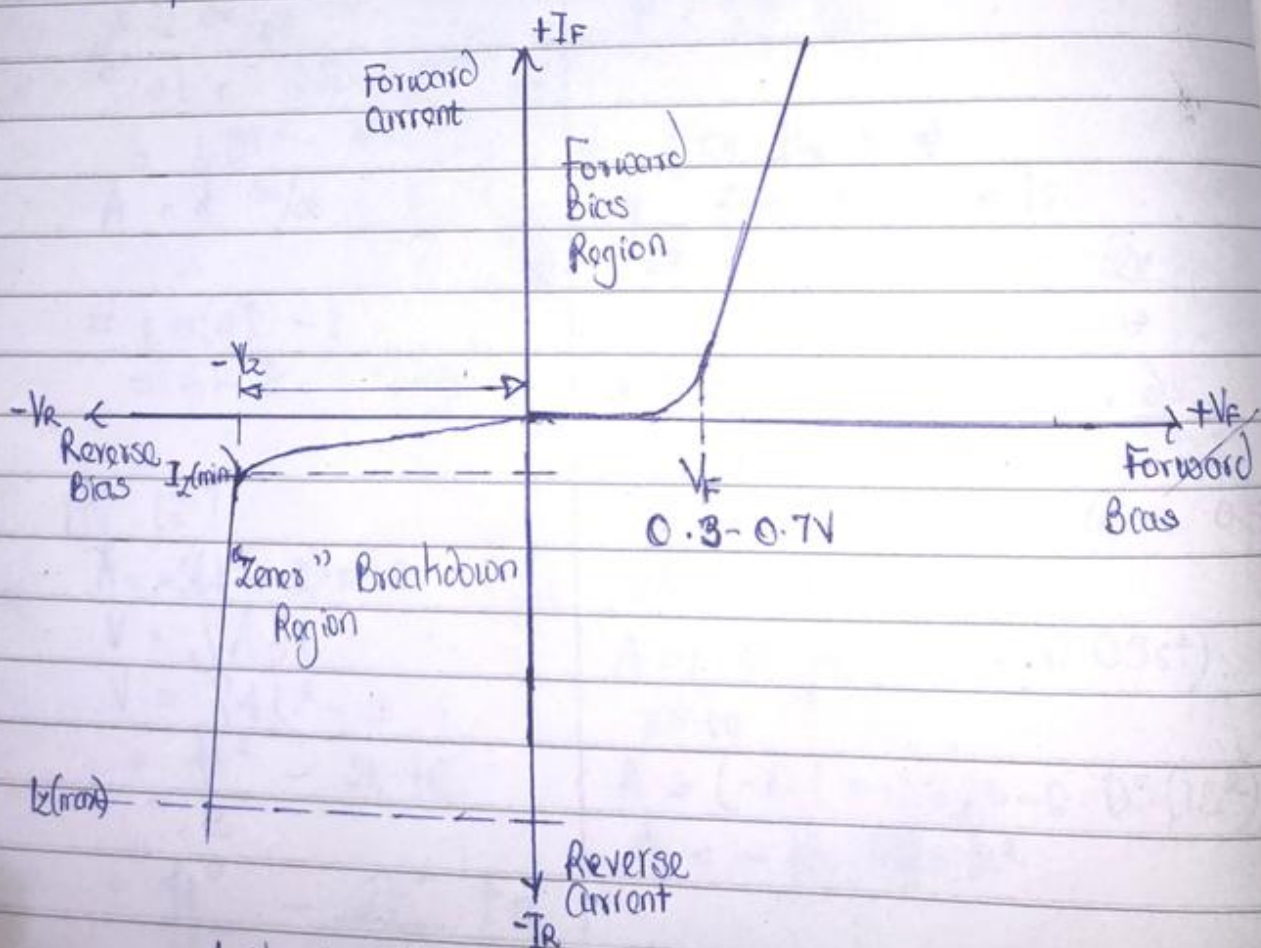i. The symbol and I-V characteristics curve,




I-V Characteristics Curve.



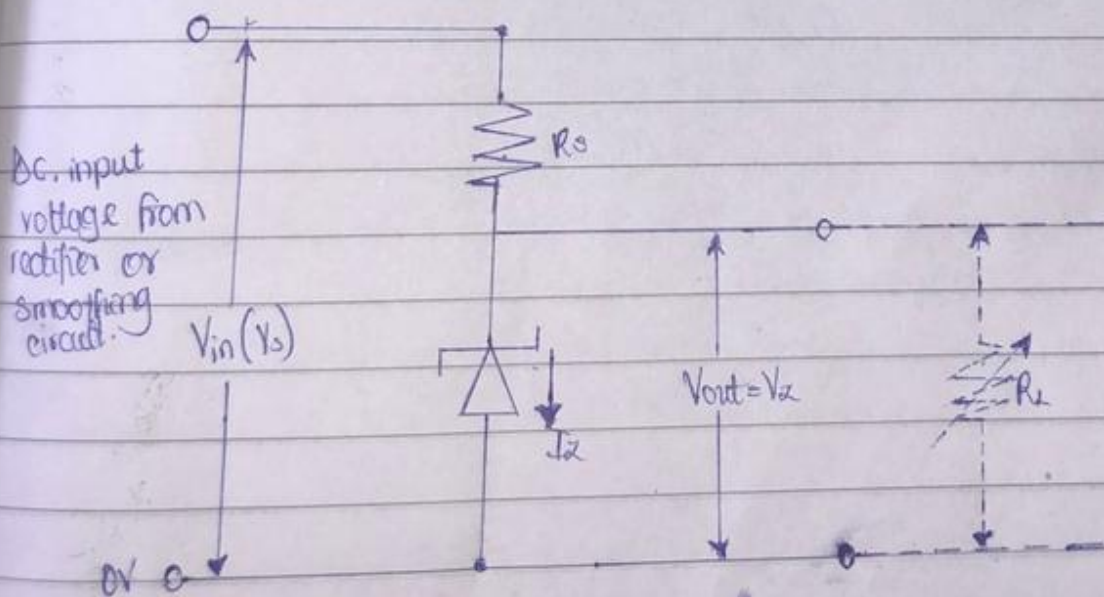ii) Circuit Diagram

The function of a regulator is to provide a constant output voltage to a load connected in parallel with it in spite of the ripples in the supply voltage or the variation in the load current and the zener diode will continue to regulate the voltage until the diode current falls below the minimum $I_Z(\text{min})$ value in the reverse breakdown region.



2) Max p Maximum power = 5W

$$I_z = 500 \text{ mA} = 0.5 \text{ A}$$

$$20 \text{ V}_{\text{max}} = V$$

$$\therefore \text{The max current} = \frac{\text{Max Power}}{\text{voltage}} = \frac{5 \text{ W}}{V}$$

$$= 0.5 \text{ A}$$

$$V_z = 10 \text{ Volts}$$

Series

$$V_R + V_z = V_{dc}$$

$$V_c = \frac{2V_{\text{max}}}{\pi}$$

$$= 0.637 V_{\text{max}}$$

$$V_R + V_z = 12.74 \text{ V}$$

$$V_R + 10 = 12.74 \text{ V}$$

$$V_R = 12.74 - 10 \text{ V}$$

$$V_R = 2.74 \text{ V}$$

Wattage

$$V_{dc} = 0.637 \times 20$$

$$= 12.74 \text{ V}_{dc}$$

$$\text{max } R_{\text{max}} = \frac{V_s - V_z}{I_z}$$

$$= \frac{12.74 - 10}{0.5}$$

$$= 5.48 \Omega$$

(i) Load Current $I_L = \frac{V_z}{R} = \frac{10}{500} = 0.02 \text{ A}$

$$\approx 0.02 \text{ A} = 20 \text{ mA}$$

$$I_z = I_s - I_L$$

$$500 - 20 = 480 \text{ mA}$$