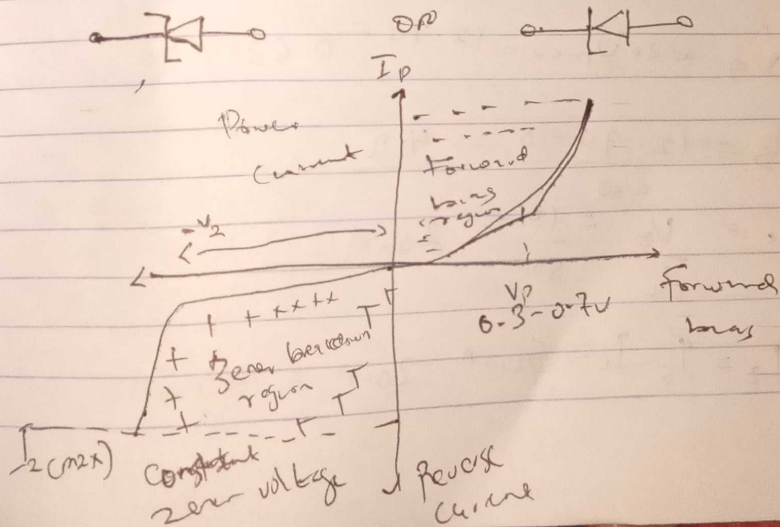



ALEXANDER Jumbo
 18/ENG 03/044

1 Zener diode as a voltage regulator. They are widely used as voltage regulators to regulate voltage across small loads. Zener diodes have a sharp reverse breakdown voltage and breakdown voltage is constant across a wide range of currents. Therefore ~~the~~ the Zener diode will be connected such that the applied voltage will reverse bias it. Therefore if the reverse bias voltage across the Zener diode exceeds the voltage across the Zener diode load will be constant.

DIAGRAM



(11)

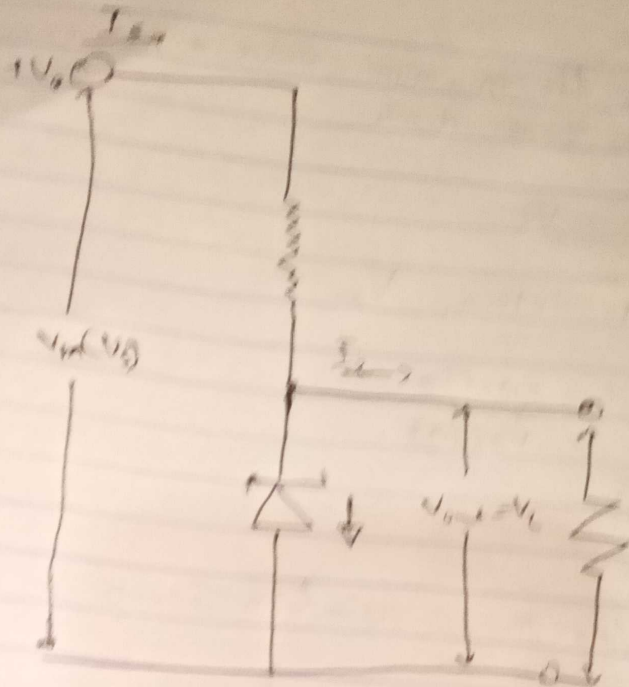

Zener diode regulator circuit

2 To determine the minimum value of the series resistor in the Zener diode

$$R_s = \frac{V_s - V_z}{I_z}$$

We need to determine V_z

$$\text{Max current} = \frac{\text{Watts}}{\text{Volts}}$$

$$\frac{500}{2} = \frac{5}{2}$$

$$2 = 10$$

$$V_s = 20V_{\text{max}} = 12.74 = 0.637 \times 20$$

$$R_s = \frac{12.74 - 10}{500} = 4 \Omega$$

$$I_z = \frac{V_z}{R_z} = \frac{10}{500} = 20 \text{mA}$$

$$I_s = I_z + I_L = 50 \text{mA} - 50 \text{mA} = 480 \text{mA}$$