

2. A 5W maximum rated Zener diode has 500mA maximum current flowing through it. If a Diemans bridge rectifier is connected as input to the regulator circuit - Calculate

- i) The minimum value of the series resistor to the Zener diode
- ii) The current across the diode at full load of 500mA

Solution

Maximum current = ~~V~~ Power,  $500 \text{ mA} = 0.5 \text{ A} = I_z$

Voltage  $V_z = 20 \text{ V}$

$P = 5 \text{ W}$

$R_z = 500 \Omega$

$$I_z = \frac{P}{V_z}$$

$$V_z = \frac{P}{I_z} = \frac{5}{0.5} = 10 \text{ V}$$

i) minimum value of the series resistor,  $R_s$

$$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{0.5} = 20 \Omega$$



ii) The current across the diode at full load of 500mA

$$I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02 \text{ A or } 20 \text{ mA}$$

$$I_z = I_s - I_L = 500 - 20 = 300 \text{ mA}$$

Zener current at full load = 300mA

Zener diode circuit diagram

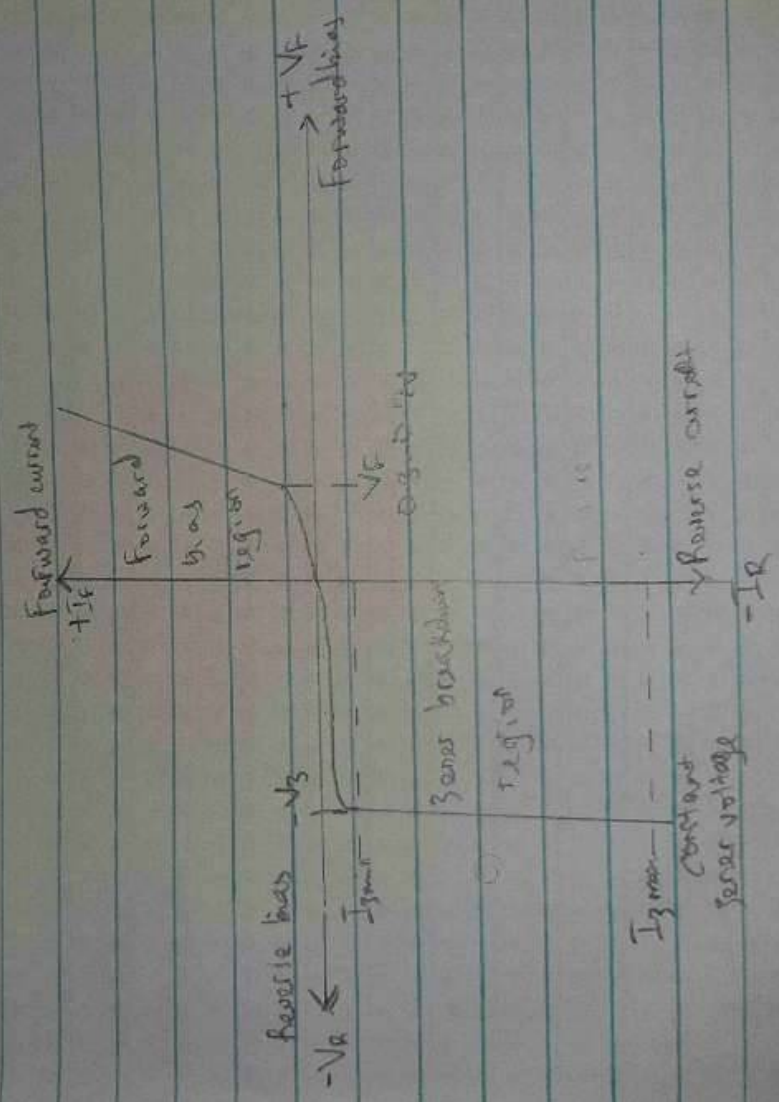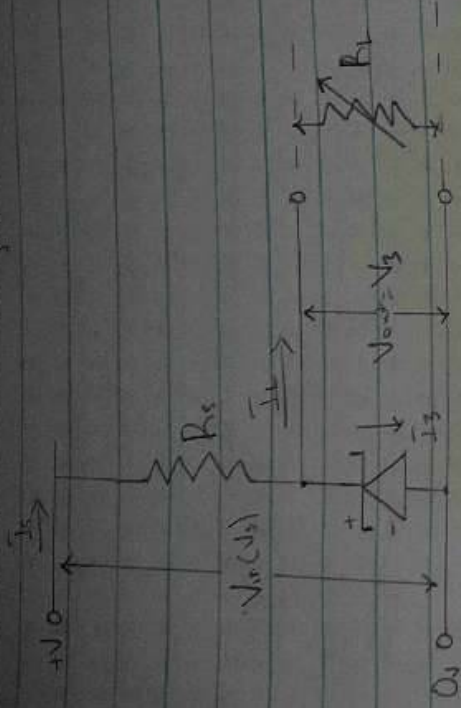

Zener diode I-V characteristics curve

### Assignment

1) A particle moves along a straight line with a velocity of  $v = (4t - 3t^2)$  m/s where  $t$  is in seconds. Determine the position of the particle when  $t = 4$ s.  $s = 0$  when  $t = 0$

Solution

$$v = (4t - 3t^2)$$

$$v = \frac{ds}{dt}$$

$$\int ds = \int v dt$$

$$s = \int v dt$$

$$s = \int_0^4 (4t - 3t^2) dt = \int_0^4 (4t - 3t^2) dt$$

$$s = \left( \frac{4t^2}{2} - \frac{3t^3}{3} \right)_0^4 = 2(4)^2 - 4^3 - 0 - 0 = -32 = 32$$

Position of particle = 32.

2. A particle moves along a straight line with a speed  $v = (0.5t^3 - 8t)$  m/s where  $t$  is in seconds. Determine the acceleration of the particle when  $t = 2$ s

Solution

$$v = (0.5t^3 - 8t)$$

$$a = \frac{dv}{dt}$$