

Ejuoneatse Tosan Dorcas

17/ENG06/029

Mechanical Engineering


Autocad assignment

A. Benefits of filters in engineering system are:

- They remove any unwanted components or features from a signal.
- They eliminate background noise.
- They are used in medical electronic systems.
- They are used in signal processing circuits and data conversion.
- They are used in radio tuning to a specific frequency.

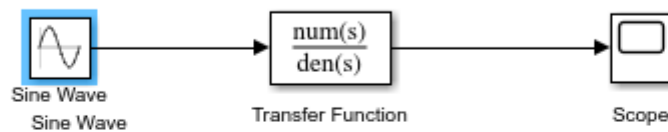B. Designing a Low-Pass Filter with 0.005Ω resistor and 0.01F capacitor

A 100V Amplitude was selected with a frequency of 1Hz for the Sine Wave Source.



C. Determining the Cut-off frequency

The cut-off frequency is calculated by $F = \frac{1}{2} * (\pi * R * C)$

When $R = 0.005\Omega$ and $C = 0.01F$

$$F = 0.5 * \pi * 0.005 * 0.01 = 3189.099 \text{ Hz}$$


D. Design Output

The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When R= 0.005Ω and C= 0.01F
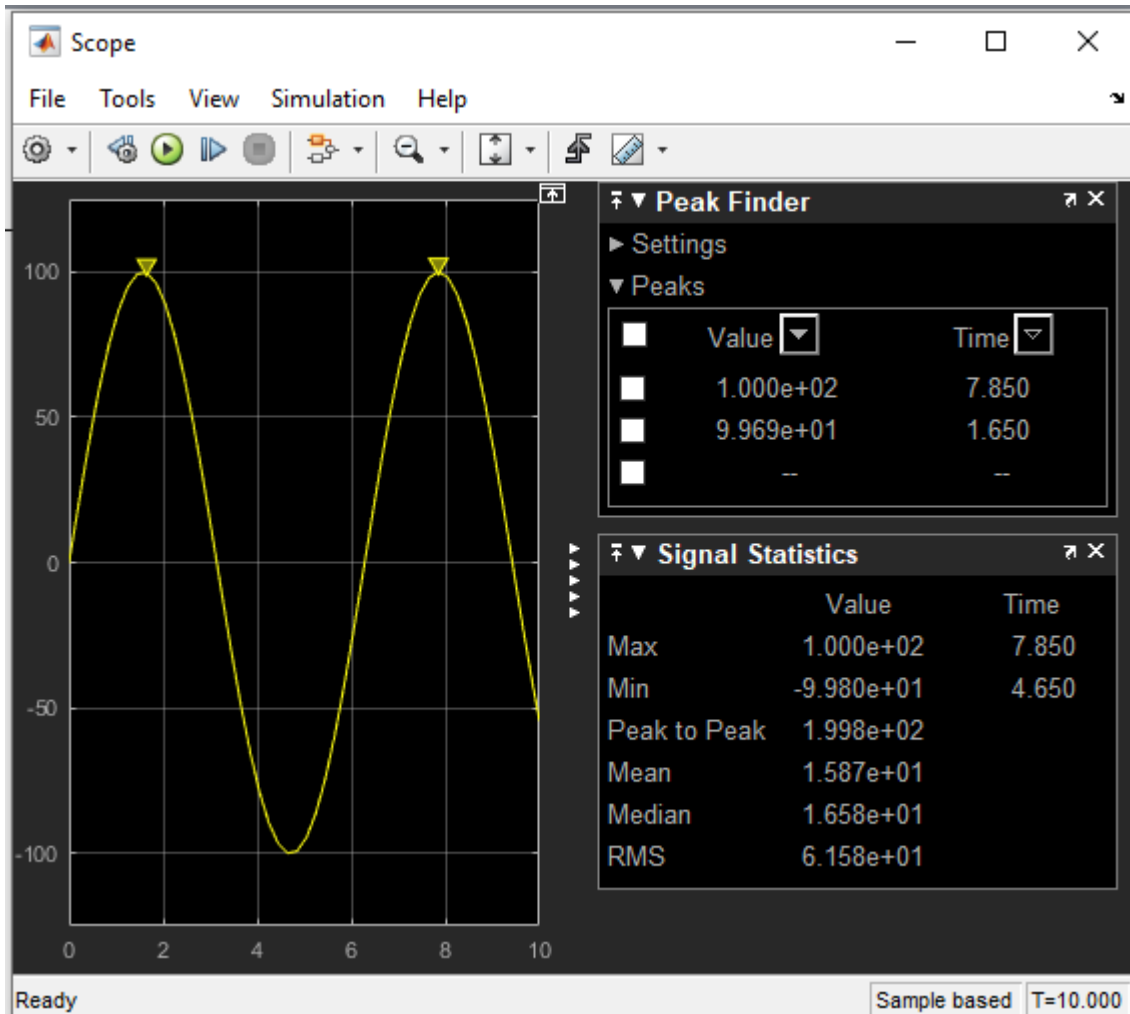
$$\text{Transfer Fcn}=(1/0.005*0.01)/(S + (0.005*0.01))= (20000)/(s+ 20000)$$



A. If two signals of 5 KΩ and 2 KΩ are pass through the filter at different intervals. Discuss your observation


When the signal of 5 KΩ is passed through the filter, the following result is obtained:

The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When R= 5000Ω and C= 0.01F
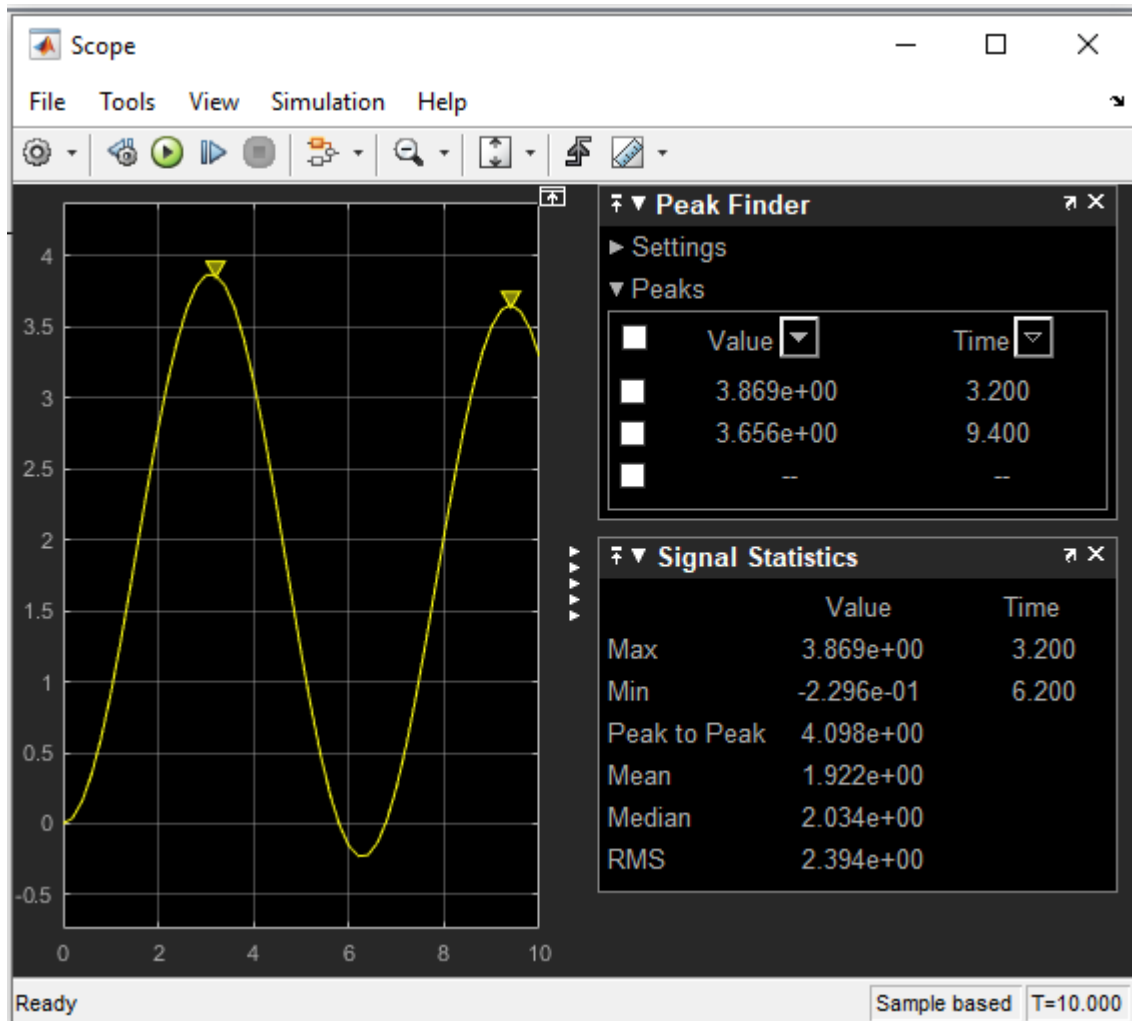
$$\text{Transfer Fcn}=(1/5000*0.01)/(S + (5000*0.01))= (0.02)/(s+ 0.02)$$




Observations: The signal is attenuated to 3.869 ohms

When the signal of 2K ohms is passed through the filter the following results are obtained: The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When R= 2000Ω and C= 0.01F

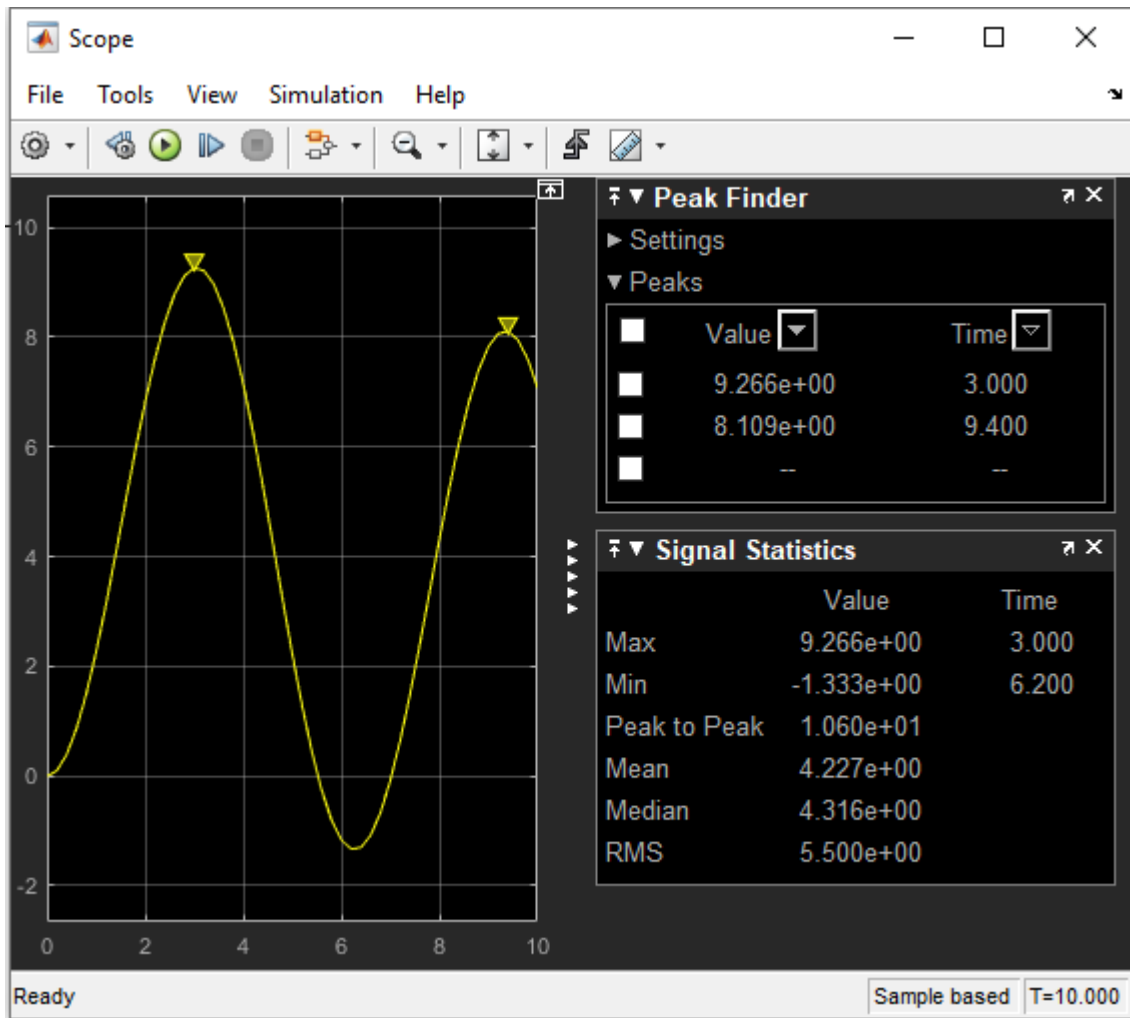Transfer Fcn=(1/2000*0.01)/(S + (2000*0.01))= (0.05)/(s+ 0.05)



Observations: The signal is attenuated to 9.266 ohms