

IWATT ENOBONG UDO

18/ENG04/080

ELECTRICAL/ELECTRONICS ENGINEERING

ENG 342

Assignment

A.) Discuss the benefits of filters in engineering system

Answer: Some benefits of filters in engineering systems include;

The tuner in radio: The bandpass filter in the tuner of the radio allows a fixed frequency to the output speaker.

Treble & bass of the speaker: The bass has lower frequencies & treble has higher frequencies. They are separated using high pass & low pass filter and are separately routed to corresponding bass speaker & treble speaker for clear music.

Anti-Aliasing: it is a low pass filter that filters out the high-frequency components from a signal before sampling. It prevents the aliasing component from being sampled.


Notch Filter: they are band rejects filters with a narrow bandwidth that filter out any interfering signal.

Power Supply Smoothing: The output of the power supply which is a rectifier has an AC ripple in it. These frequencies are filtered out using a low pass filter which results in smoothing the output signal.

Noise suppression: They are used in communication systems for noise removal from the received signals.

B.) Design a low pass filter of 0.005Ω and $0.01F$ using **building blocks only**; you are free to determine your amplitude value.

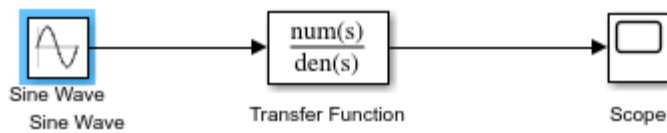Answer: A 100V Amplitude was selected with a frequency of 1Hz for the Sine Wave Source.



C.) Determine the cut-off frequency

Answer: The cut-off frequency is calculated by $F = \frac{1}{2} * (\pi * R * C)$

When $R = 0.005\Omega$ and $C = 0.01F$

$$F = 0.5 * \pi * 0.005 * 0.01 = 3189.099 \text{ Hz}$$


D.) Determine the cut-off frequency

Answer: The transfer function equation for the circuit is given as

$$\frac{1/RC}{S + 1/RC}$$

When $R = 0.005\Omega$ and $C = 0.01F$
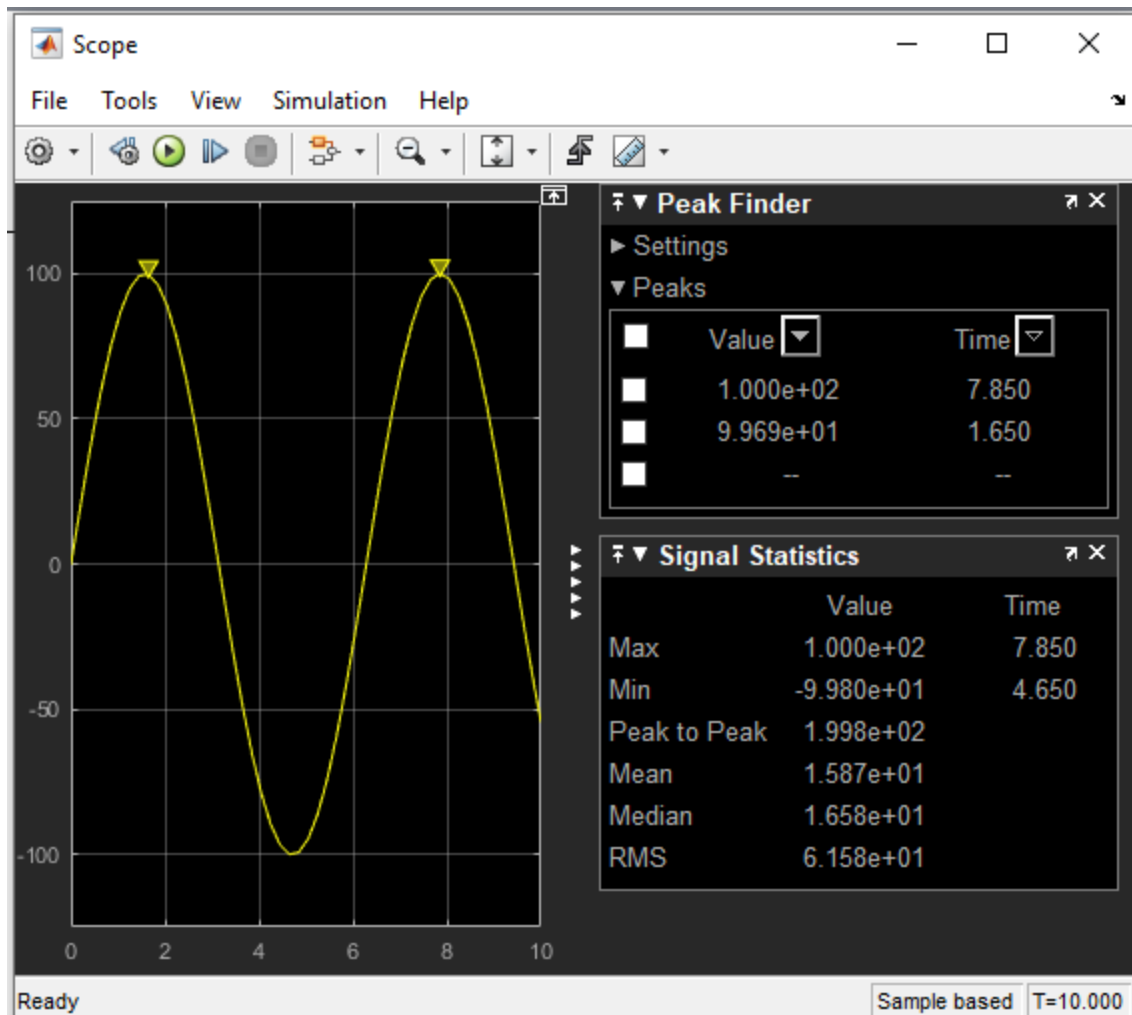
$$\text{Transfer Fcn} = \frac{1/0.005*0.01}{S + (0.005*0.01)} = \frac{20000}{s + 20000}$$



E.) If two signals of 5 KΩ and 2 KΩ are pass through the filter at different intervals. Discuss your observation(s)


Answer: When the signal of 5 KΩ is passed through the filter, the following result is obtained:

The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When R= 5000Ω and C= 0.01F
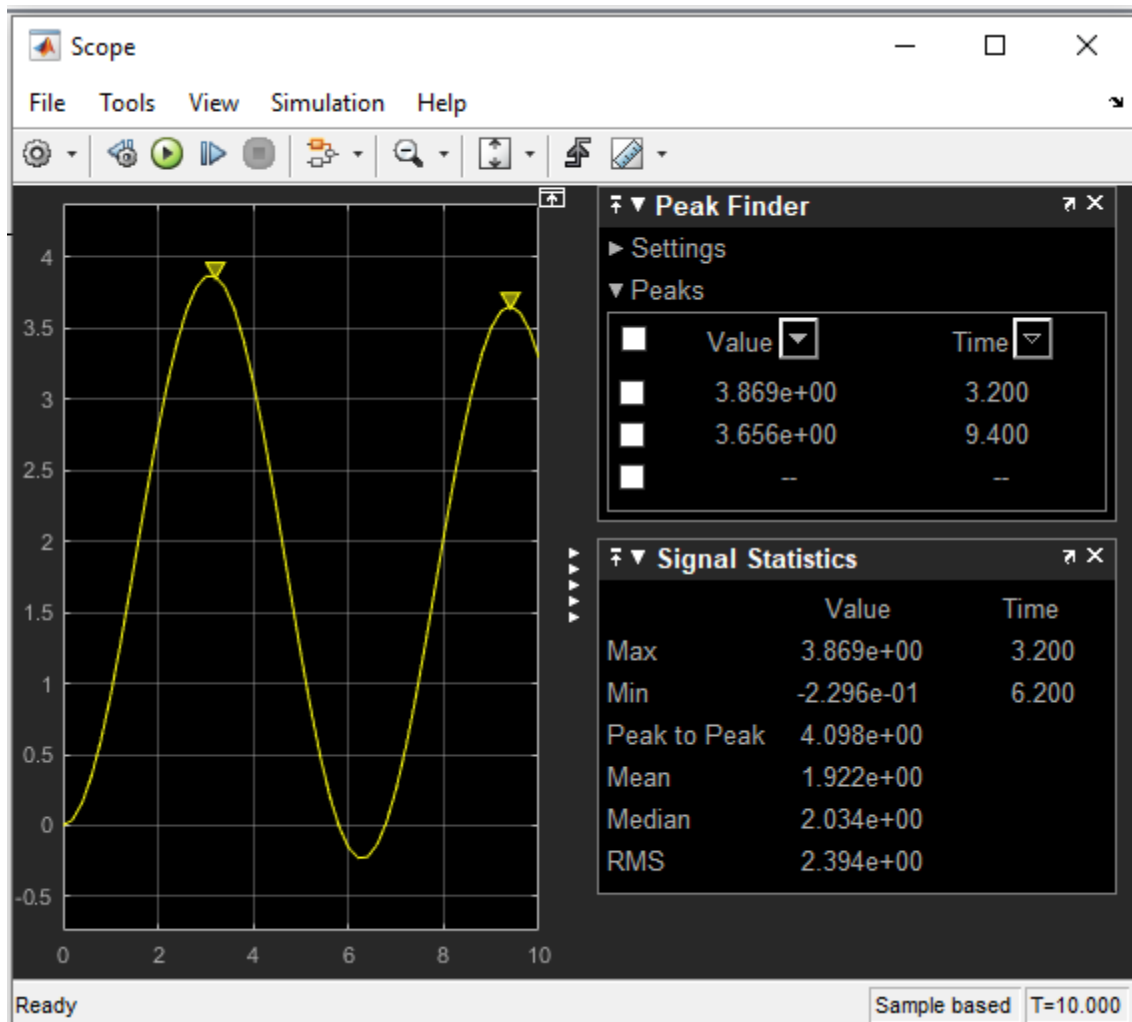
$$\text{Transfer Fcn}=(1/5000*0.01)/(S + (5000*0.01))= (0.02)/(s+ 0.02)$$




Observations: The signal is attenuated to 3.869 ohms

When the signal of 2K ohms is passed through the filter the following results are obtained:
 The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When R= 2000Ω and C= 0.01F

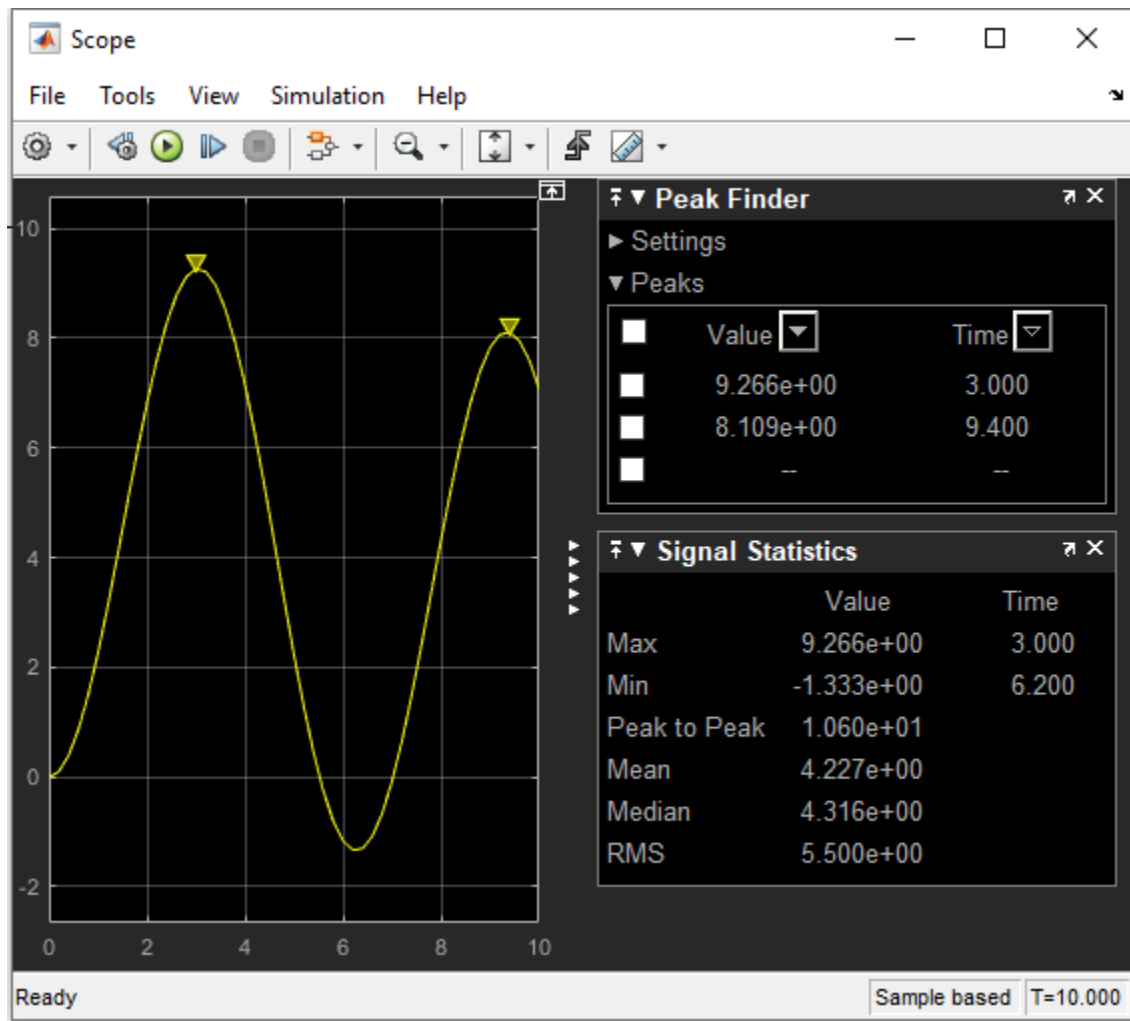Transfer Fcn=(1/2000*0.01)/(S + (2000*0.01))= (0.05)/(s+ 0.05)



Observations: The signal is attenuated to 9.266 ohms