

NAME: ALEGBELEYE OLUWAFEMI OLADIPUPO

MATRIC NO: 17/ENG04/011

DEPARTMENT: ELECT/ELECT

ENG 342

ANSWERS

A. Benefits of filters in engineering

- Filters are essential building blocks of any Electronics and Communication Systems that alter the amplitude and phase characteristics.
- Filters is basically linear circuit that helps remove unwanted components such as Noise, Interference and Distortion from the input signal
- They are used in Radio tuning
- They are used In Signal Processing Circuits and Data Conversion
- Filters are used in pre-amplification, Equalization in Audio systems

B. Building a low pass filter with 0.005ohms and 0.01F

Gathering Blocks

Step 1: Create new model

Step 2: Insert *Scope*

Step 3: Insert *AC Voltage Supply*

Step 4: Insert *Series RLC Branch and another Series RLC Branch*

Step 5: Insert *Ground*

Step 6: Insert *powergui*

Step 7: Insert *Voltage Measurement*

untitled* - Simulink

File Edit View Display Diagram Simulation Analysis Code Tools Help

10.0

untitled

untitled

Quickly insert blocks by double clicking in the diagram and typing part of the block name. [More information.](#)

The diagram contains the following blocks and components:

- powergui**: A block labeled "Continuous" with a question mark icon, used for continuous-time simulation.
- AC Voltage Source**: A block representing an AC voltage source.
- RL Circuits**: Two identical series combinations of a resistor, an inductor, and a capacitor.
- Scope**: A block used for capturing and displaying simulation data.
- Summing Junction**: A block with a plus sign and a minus sign, used for combining signals.
- Ground**: A standard ground symbol.


Ready 100% auto(ode15s)

Modifying the Blocks

Step 1: Double click on the first *Series RLC Branch*, edit Branch type to **R** and Resistance (ohms) to **0.005**

Step 2: Double click on the second *Series RLC Branch*, edit Branch type to **C** and Resistance (farrads) to **0.01**

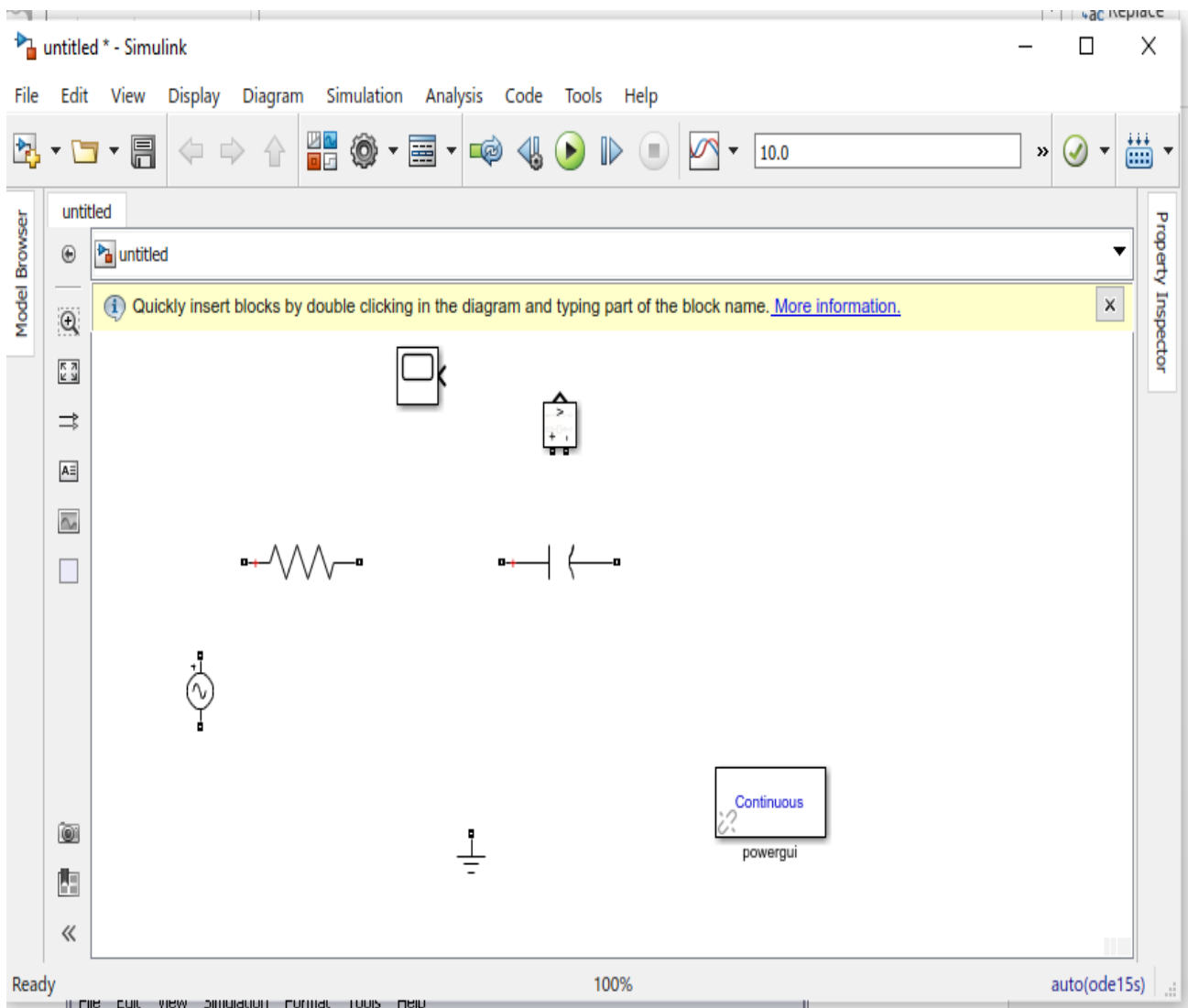Step 3: Double click on the *AC Voltage Supply*, edit the Peak Amplitude to 50V and Frequency to 10Hz



Connecting Blocks with Lines


Step 1: Drag the mouse from the output terminal of the *AC Voltage Supply* to the *Series Resistor* and to the *Series Capacitor*.

Step 2: Negative terminal of the *Series Capacitor* is connected to the Negative terminal of *Voltage Measurement*. The Positive terminal of the *Voltage Terminal* is bridged to the connection between the *Series Resistor* and *Series Capacitor*

Step 3: Drag the mouse from the output terminal of the *Voltage Measurement* to the input of the *Scope*

Step 4: Drag the mouse from the negative terminal of the *AC Voltage Supply* to the *Ground*

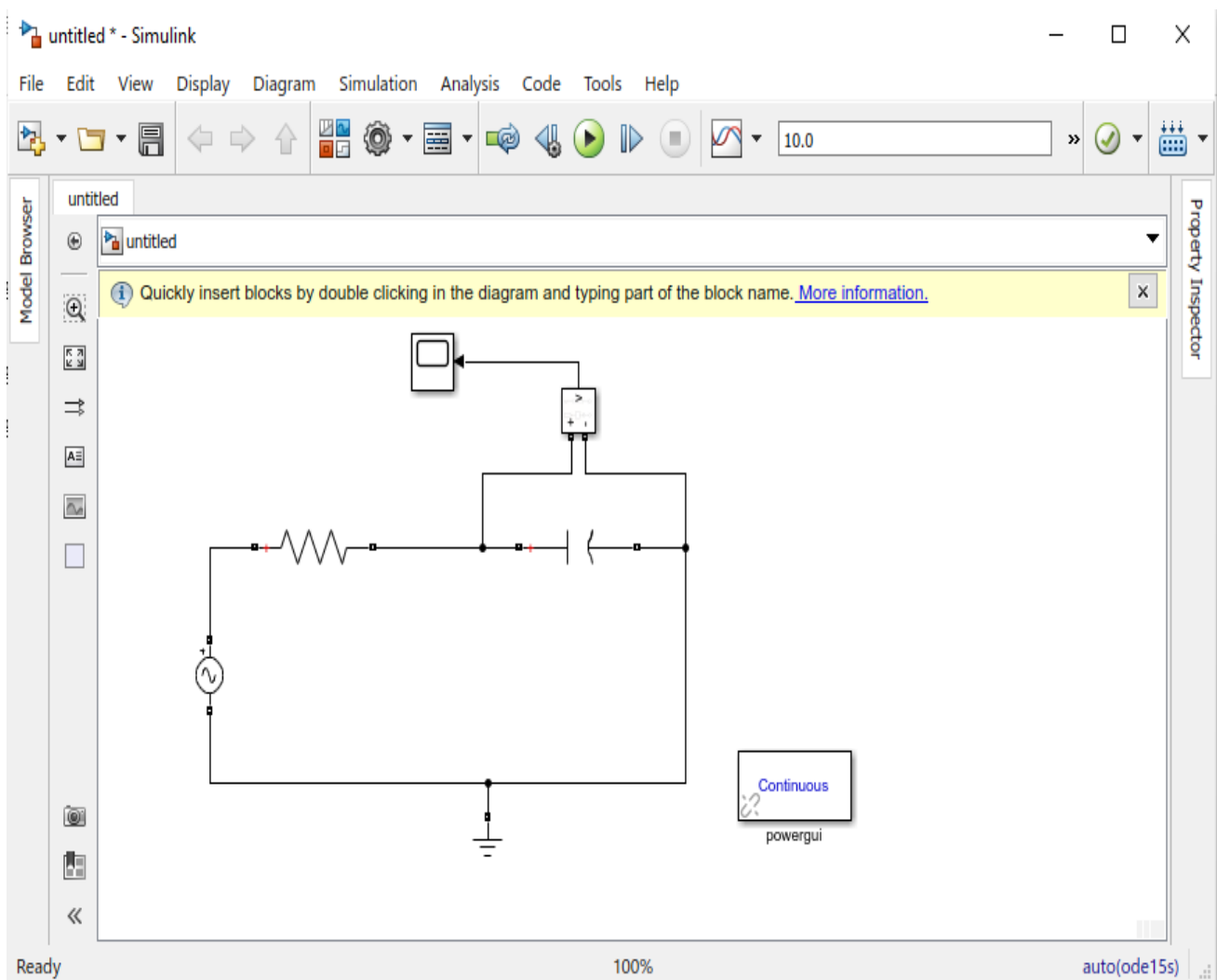Step 5: Drag the mouse from the *Ground* to the negative terminal of the *Series Capacitor*.




C. To determine the cutoff frequency

$$f_c = \frac{1}{2\pi R C} = \frac{1}{2\pi \times 0.005 \times 0.01} = 3183.0988 \text{ Hz}$$

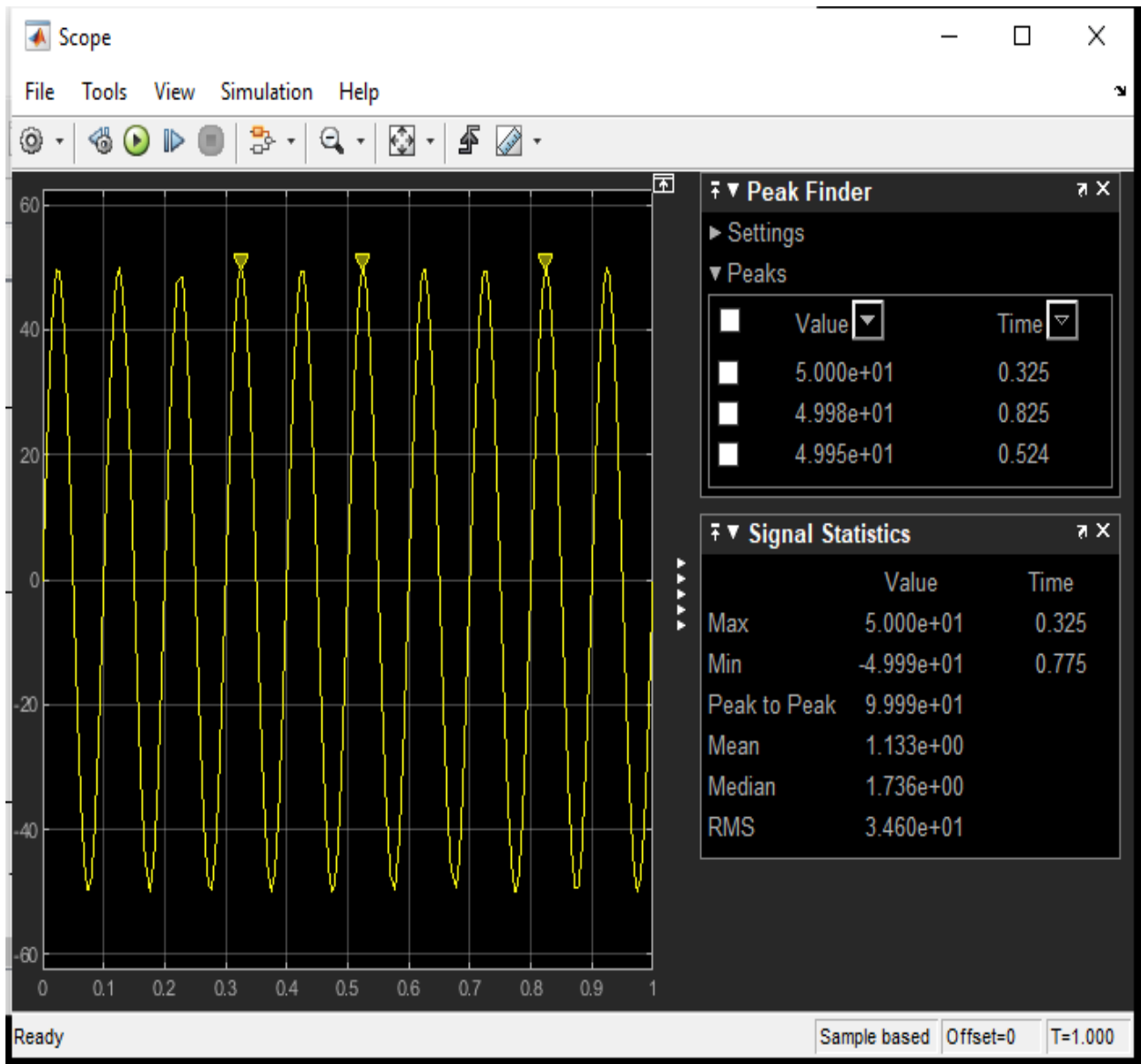
D. Simulation of Model

Now that the model is complete, you can simulate the model. Select **Start** from the **Simulation** menu to run the simulation. Double-click on the `_Scope_block` to view its output. Hit the **autoscale** button (binoculars) and you should see the following:



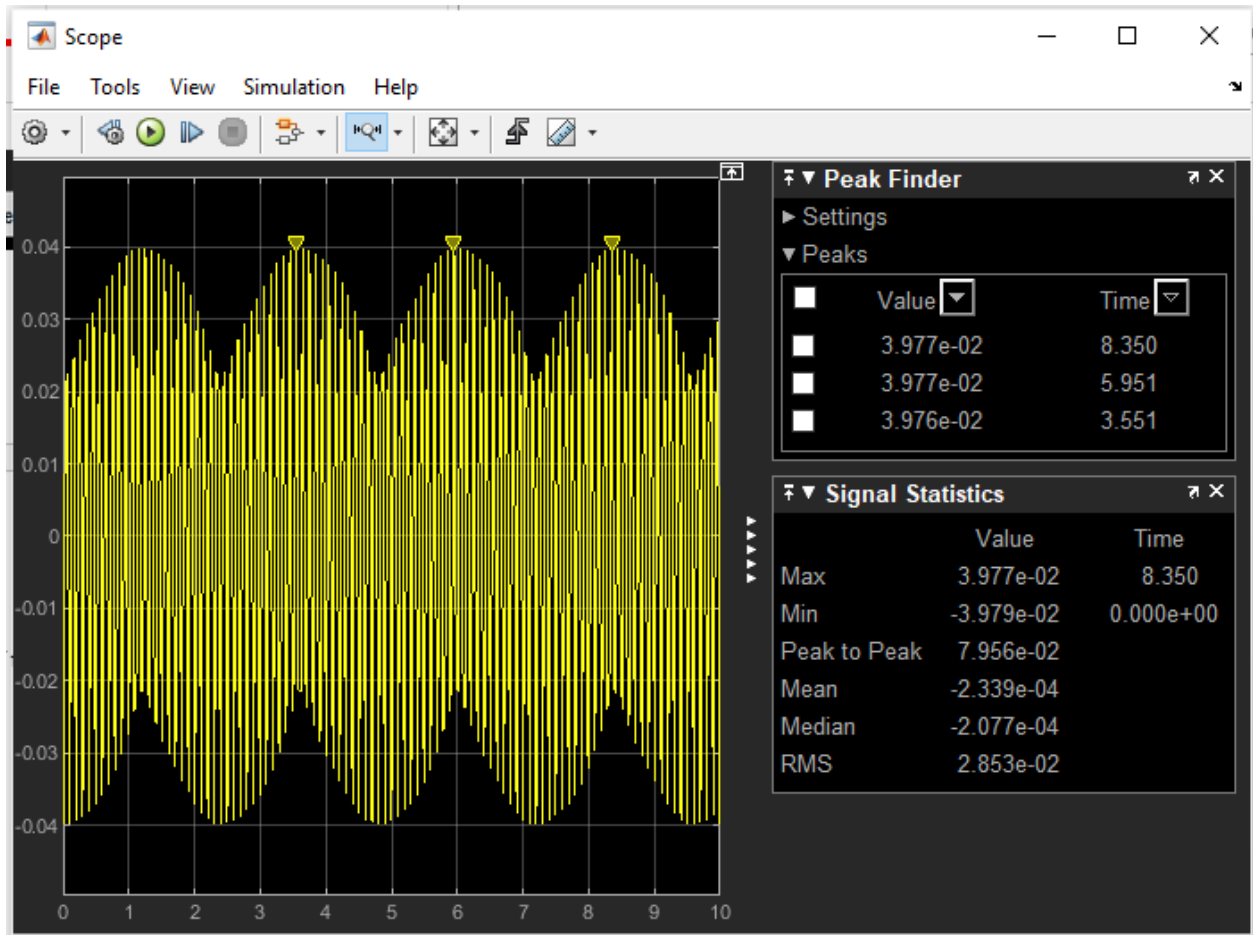E. If two signals of 5K and 2k ohms are passed through a filter


When 2k ohms signal passes through the filter



$$\text{Transfer function} = \frac{(0.02)}{(s+0.02)}$$

Observation: When signal of 5k ohms was passed through the filter, the signal was attenuated at **3.977e-02**. The high frequency signal was blocked out while the low frequency signal passed through. The peak to peak was 7.956e-02

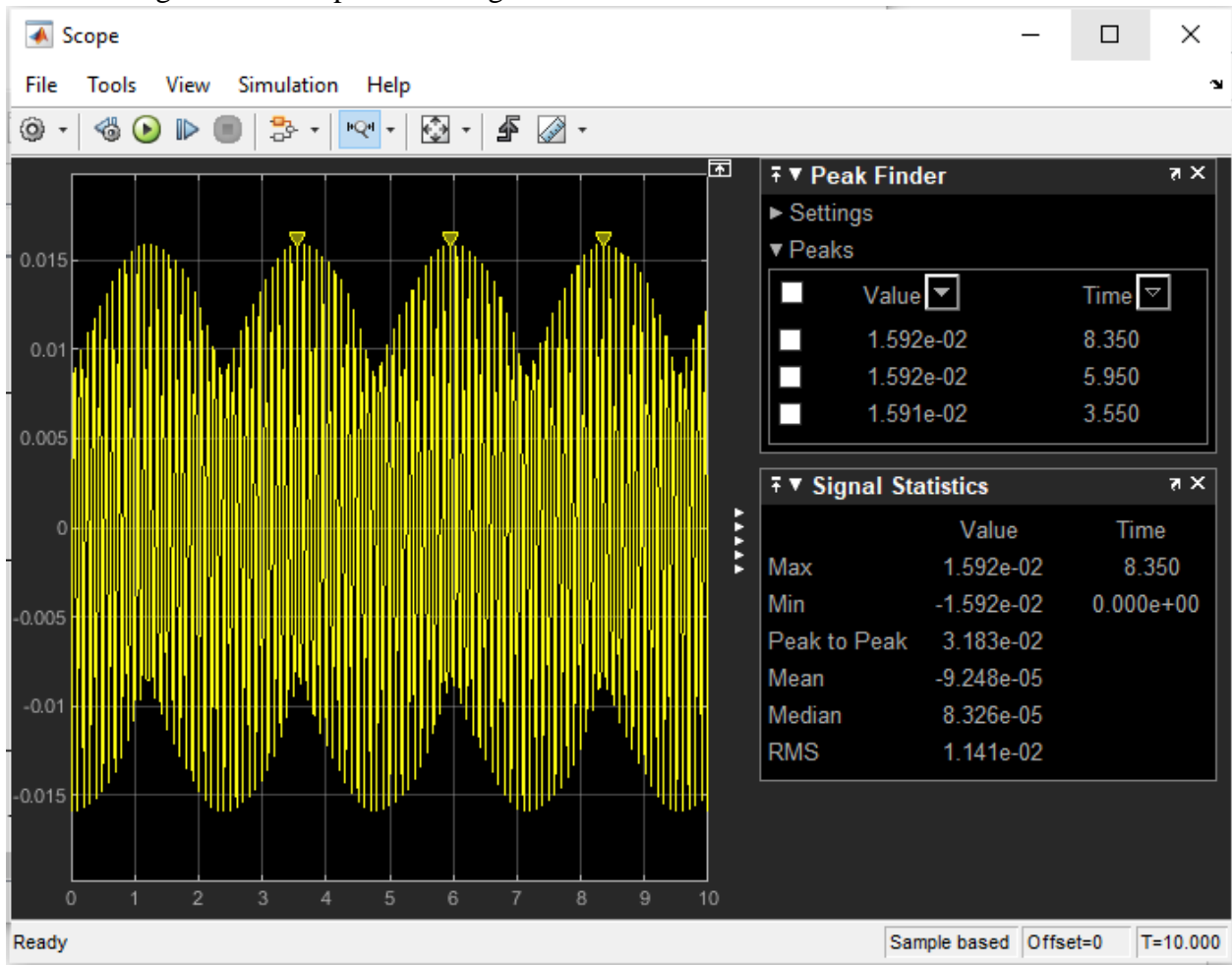When the signal 5k ohms passes through the filter



$$\text{Transfer function} = \frac{(0.05)}{(s+0.05)}$$

Observation: When signal of 5k ohms was passed through the filter, the signal was attenuated at **1.592e-02**. The high frequency signal was blocked out while the low frequency signal passed through.

The peak to peak for 5k ohms was **3.183e-02**

Conclusion

The value of peak to peak for both 5k ohms and 2k ohms are **3.183e-02** and **3.977e-02** respectively.