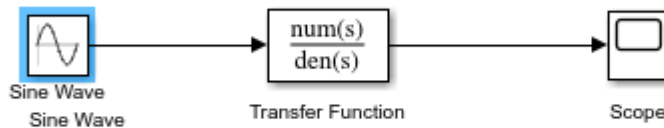


A.

- **Radio Communications:** Filters enable radio receivers to only "see" the desired signal while rejecting all other signals (assuming the other signals have different frequency content).
- **DC power supplies:** Filters are used to eliminate undesired high frequencies (i.e., noise) that are present on AC input lines. Additionally, filters are used on a power supply's output to reduce ripple.
- **Audio electronics:** A crossover network is a network of filters used to channel low-frequency audio to woofers, mid-range frequencies to midrange speakers, and high-frequency sounds to tweeters.
- Used in Audio Applications for Equalization purposes.
- Used in Receivers such as Superheterodyne etc for efficient reception of the baseband signals.

B. Designing a Low-Pass Filter with 0.005Ω resistor and 0.01F capacitor

A 100V Amplitude was selected with a frequency of 1Hz for the Sine Wave Source.



C. Determining the Cut-off frequency

The cut-off frequency is calculated by $F = \frac{1}{2} * (\pi * R * C)$

When $R = 0.005\Omega$ and $C = 0.01F$

$$F = 0.5 \cdot \pi \cdot 0.005 \cdot 0.01 = 3189.099 \text{ Hz}$$


D. Design Output

The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When $R = 0.005\Omega$ and $C = 0.01F$
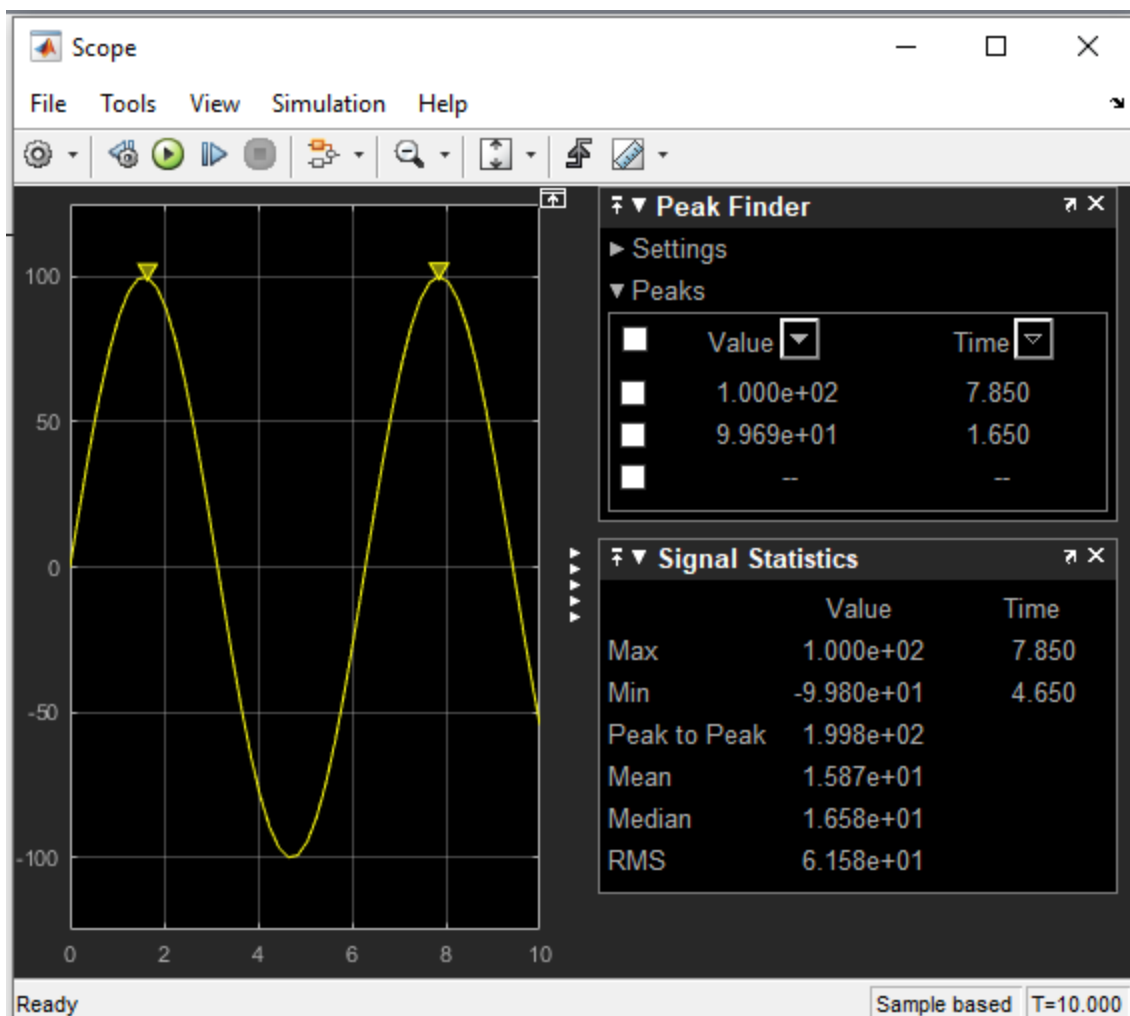
$$\text{Transfer Fcn} = (1/0.005 \cdot 0.01)/(S + (0.005 \cdot 0.01)) = (20000)/(s + 20000)$$



- A. If two signals of 5 KΩ and 2 KΩ are pass through the filter at different intervals. Discuss your observation**


When the signal of 5 KΩ is passed through the filter, the following result is obtained:

The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When $R = 5000\Omega$ and $C = 0.01F$
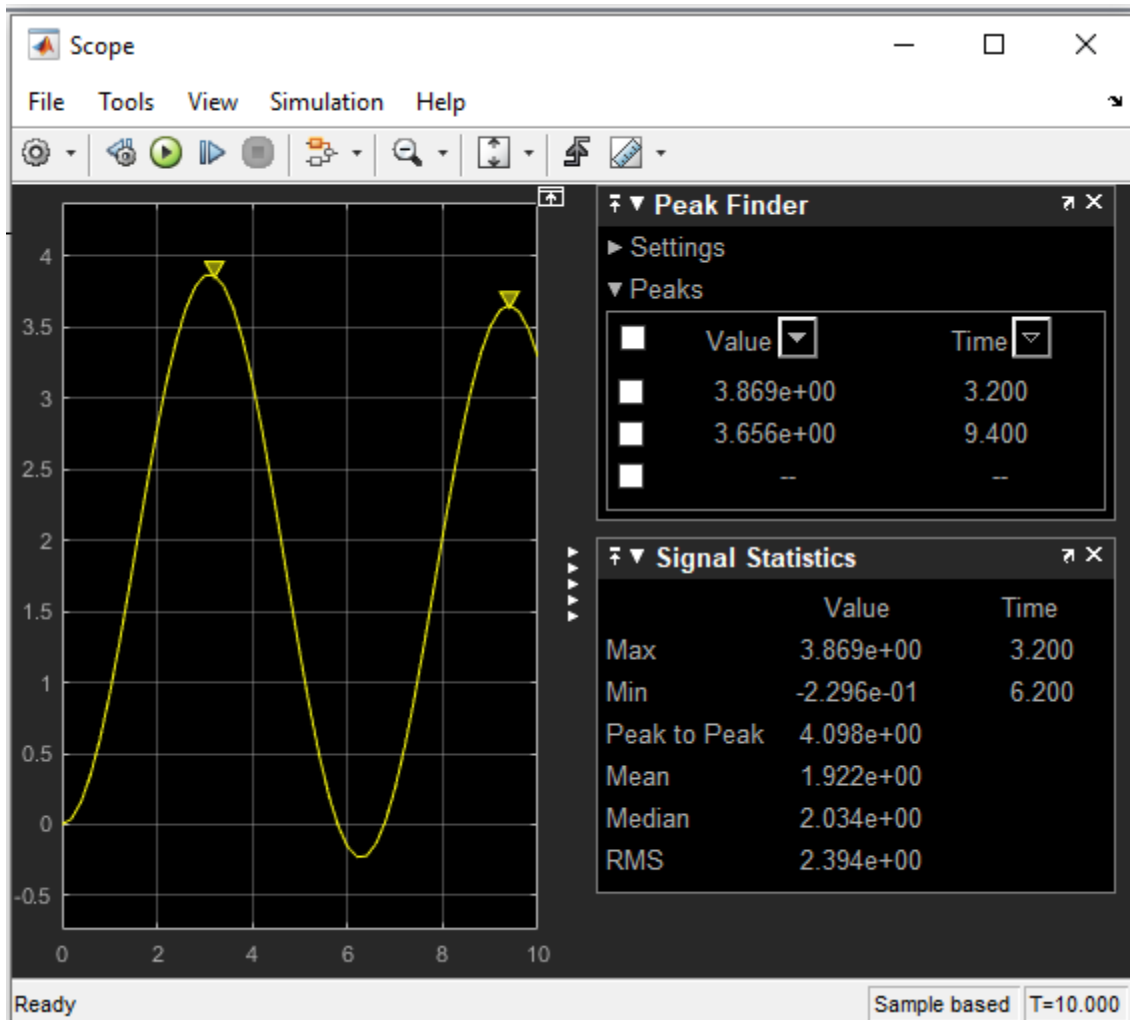
$$\text{Transfer Fcn} = (1/5000 \cdot 0.01)/(S + (5000 \cdot 0.01)) = (0.02)/(s + 0.02)$$



Observations: The signal is attenuated to 3.869 ohms


When the signal of 2K ohms is passed through the filter the following results are obtained:

The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When R= 2000Ω and C= 0.01F
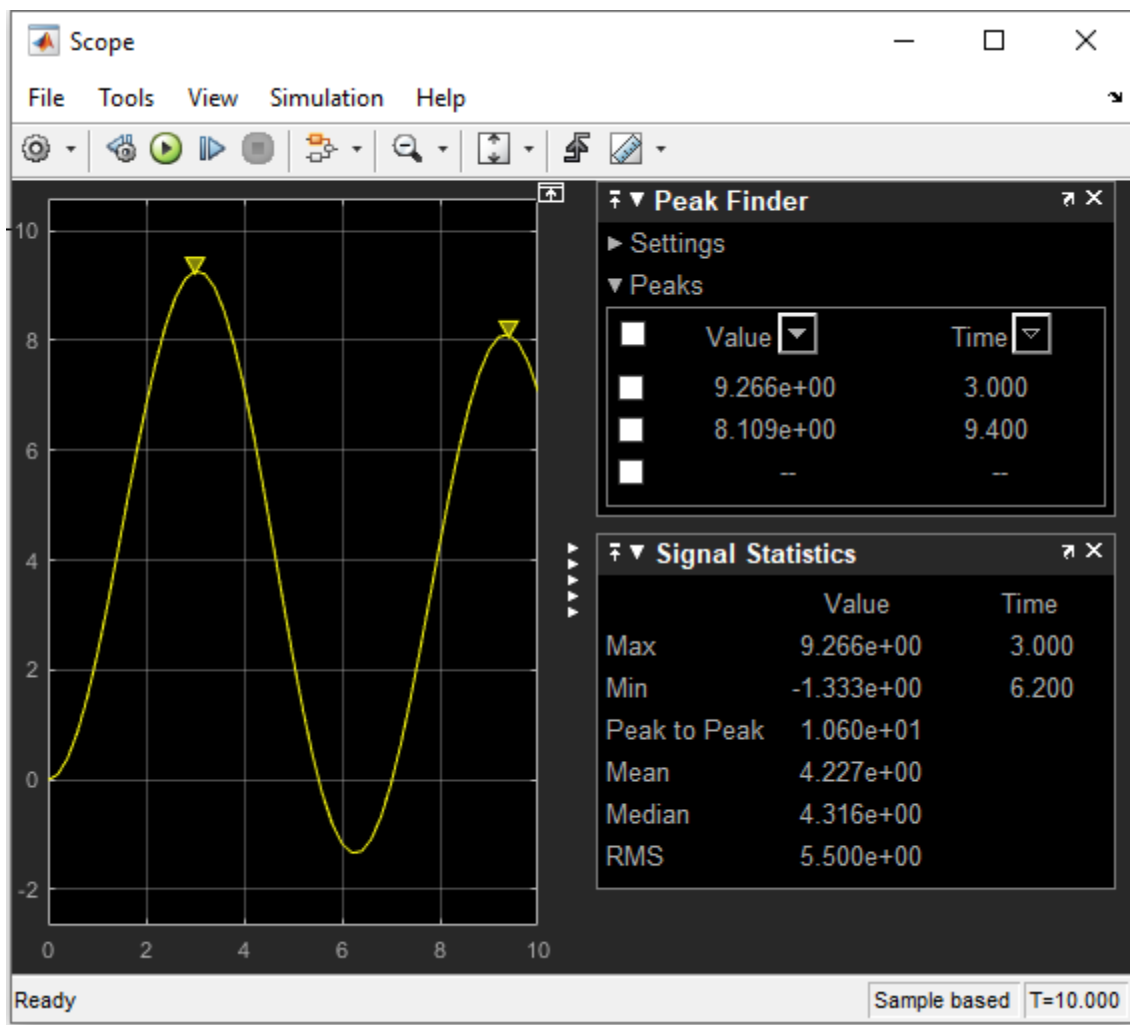
$$\text{Transfer Fcn}=(1/2000*0.01)/(S + (2000*0.01))= (0.05)/(s+ 0.05)$$



Observations: The signal is attenuated to 9.266 ohms