

**A. Benefits of filters in Engineering Systems**

A filter is a circuit capable of passing (or amplifying) certain frequencies while attenuating other frequencies. Thus, a filter can extract important frequencies from signals that also contain undesirable or irrelevant frequencies. The four primary types of filters are the Low-pass filter, the high-pass filter, the band-pass and the notch filter. There are many practical applications for filters. Examples include:

- **Radio Communications:** Filters enable radio receivers to only "see" the desired signal while rejecting all other signals (assuming the other signals have different frequency content).
- **DC power supplies:** Filters are used to eliminate undesired high frequencies (i.e., noise) that are present on AC input lines. Additionally, filters are used on a power supply's output to reduce ripple.
- **Audio electronics:** A crossover network is a network of filters used to channel low-frequency audio to woofers, mid-range frequencies to midrange speakers, and high-frequency sounds to tweeters.
- **Analog-to-digital conversion:** Filters are placed in front of an ADC input to minimize aliasing.
- High-pass and low-pass filters are also used in digital image processing to perform image modifications, enhancements, noise reduction, etc.
- Used in Audio Applications for Equalization purposes.
- Used in Receivers such as Superheterodyne etc for efficient reception of the baseband signals.

**B. Designing a Low-Pass Filter with 0.005Ω resistor and 0.01F capacitor**

A 70V Amplitude was selected with a frequency of 10Hz for the Ac Voltage source.

We used the following equations in generating our design:

$$V_{in}(t) - V_{out}(t) = Ri(t)$$

$$Q_c(t) = CV_{out}(t)$$


$$I(t) = dQ_c/dt$$

$$V_{in}(t) - V_{out}(t) = RCdV_{out}/dt \text{ —————(*)}$$

Equation (\*) is used in the design

- The simulink was created and named

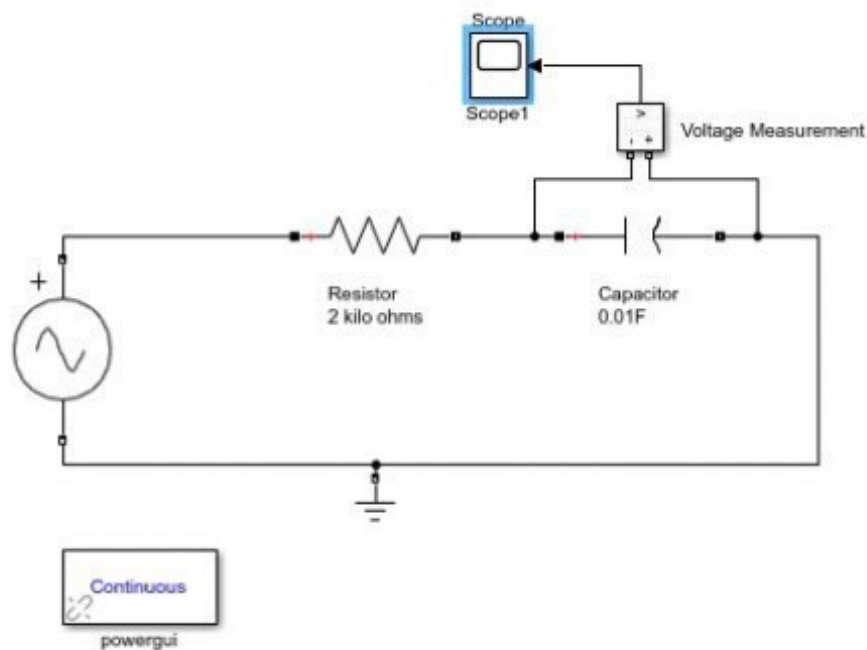- A sine wave was chosen
  - A noise was added to the sine wave
  - To see the output, an addition was added
  - Furthermore, a scope was added
- The signal was tested and the output was viewed




### C. Determining the Cut-off frequency

Theoretically, the cut-off frequency can be determined by  $F = \frac{1}{2\pi RC}$

Where  $R = 0.005\Omega$  and  $C = 0.01F$

$$F = \frac{1}{2\pi \cdot 0.005 \cdot 0.01} = 3183.099 \text{ Hz}$$


### D. Design Output

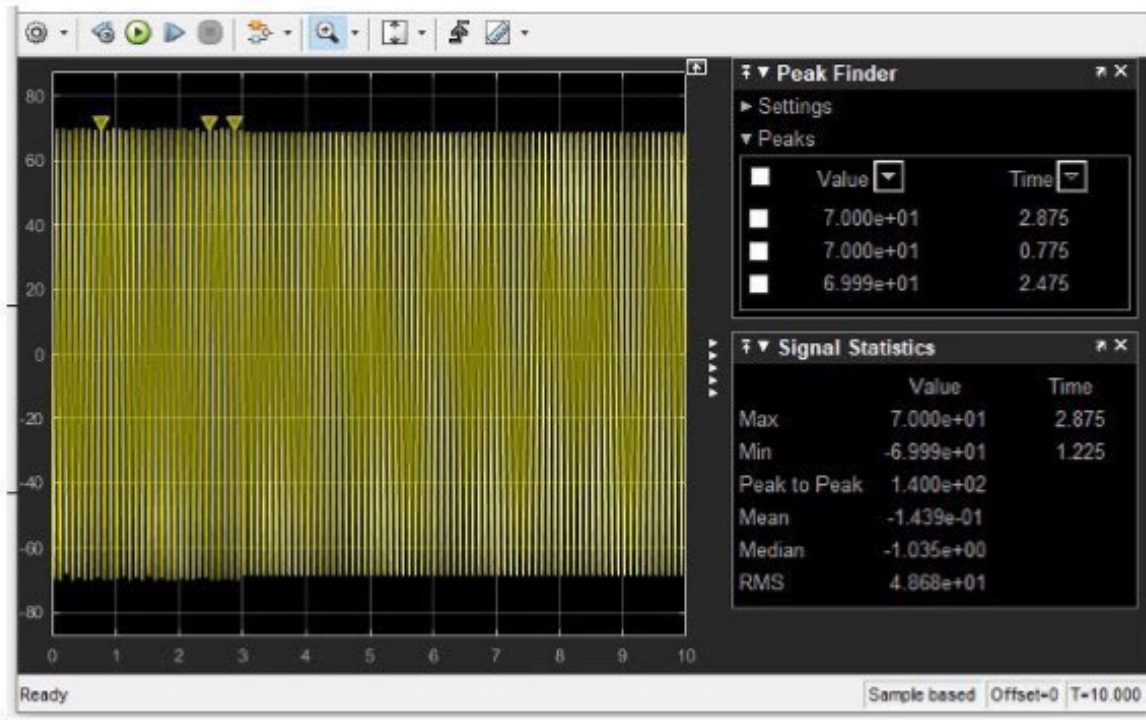

The curve is shown above with the peak value 70 which is the input voltage.

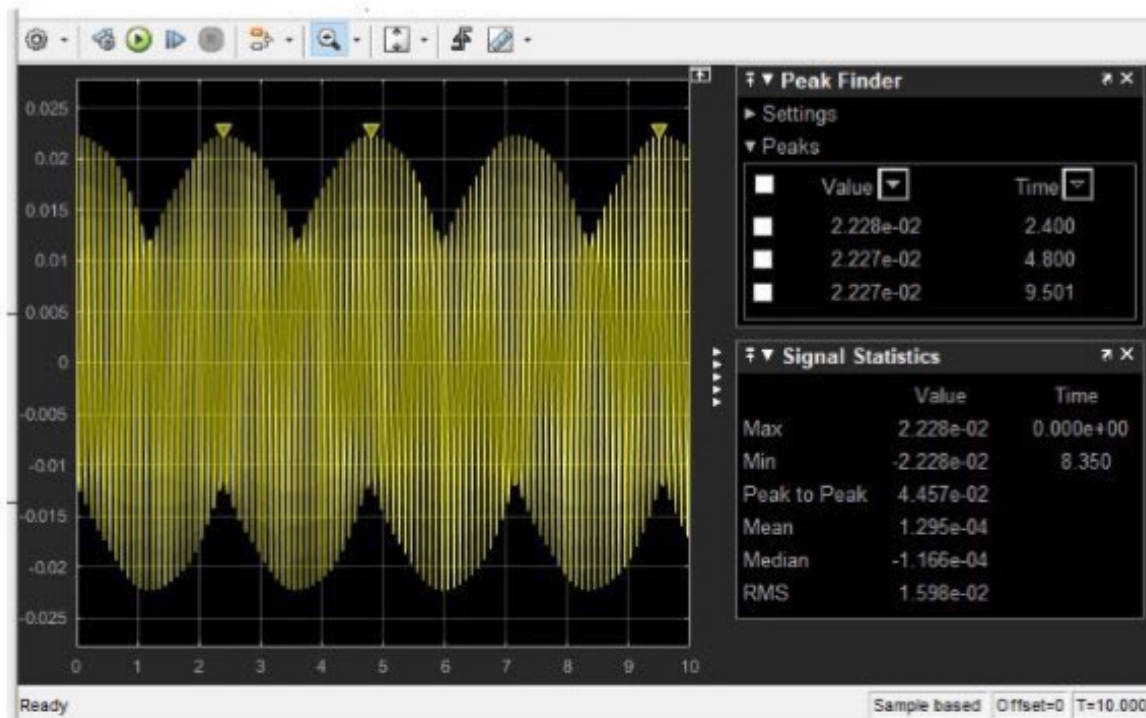
**E. If two signals of 5 K $\Omega$  and 2 K $\Omega$  are pass through the filter at different intervals. Discuss your observation**

When the signal of 5 K $\Omega$  is passed through the filter, the following result is obtained:



**Observations:** It is noticed that when the signal of 5K ohms is passed through the filter, the signal is attenuated to 0.02228 since the input frequency was too high.

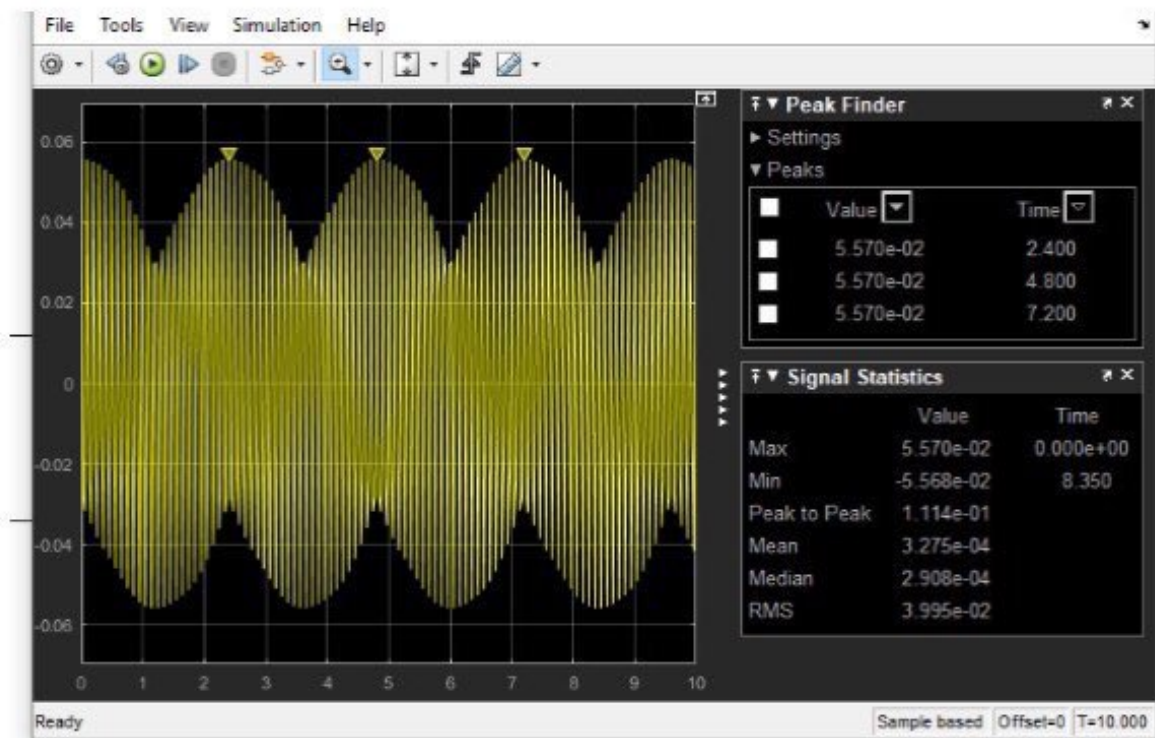**When the signal of 2K ohms is passed through the filter the following results are obtained:**



**Observations:** It is seen that when the signal of 2K ohms is passed through the filter, the signal is attenuated to 0.0557.