


ENG 342 Classwork

Nwadike Reginald-Francis .C

17/ENG02/052

Computer Engineering.


A

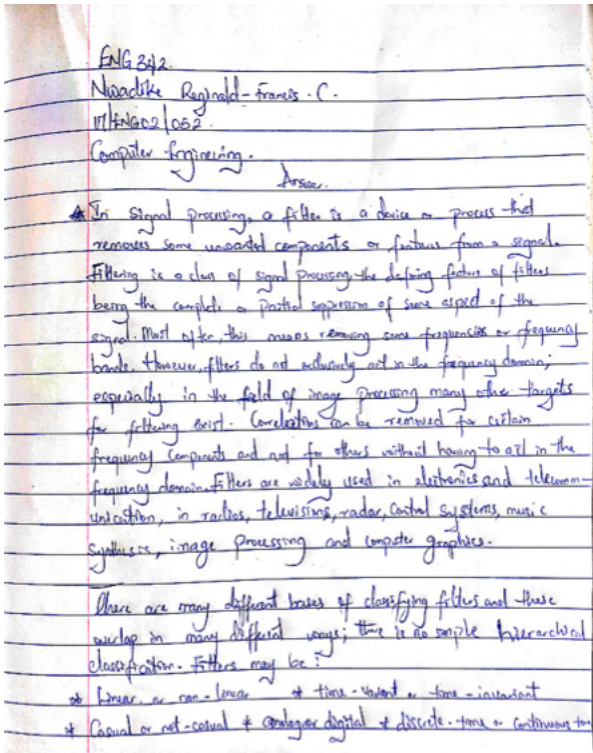


B. A low pass filter of

0.005ohms and 0.01F, with


building blocks

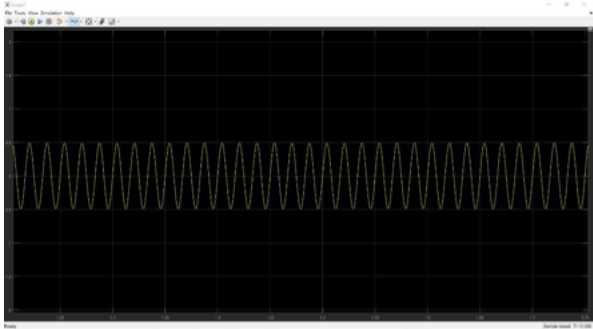

C. The Cut-Off Frequency

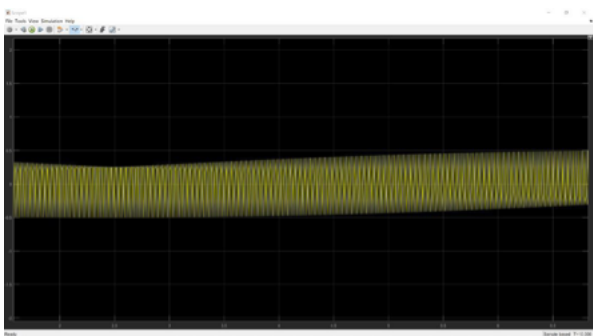

D. The Simulated Design

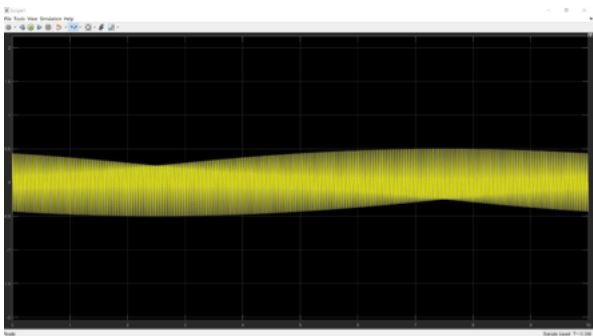

E. When the signal of 2K ohms is passed through the filter, the following will be obtained.

The transfer function

equation for the circuit is given below as


$$(1/RC)/(S + 1/RC)$$

When $R = 2,000\Omega$ and $C = 0.01F$

Transfer Fcn =

$$(1/2000*0.01)/(S + (2000*0.01)) = (0.05)/(s+0.05)$$

therefore:

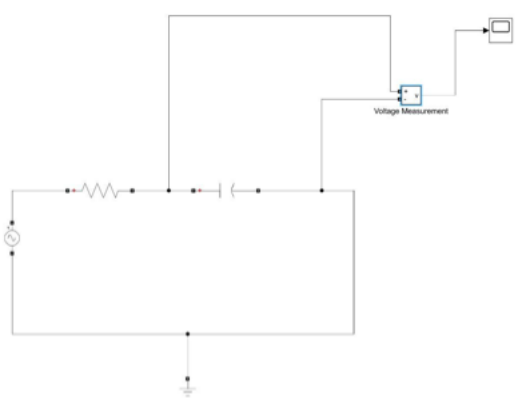

Observations: Attenuation is the reciprocal of gain, and for this particular signal, the signal is attenuated to 9.266 ohms .