

AKUH OJOAJOGU JOSEPH YUSUF

17/ENG06/008

MECHANICAL ENGINEERING

ENG 342 ASSIGNMENT


QUESTION A.

- FILTERS AUTHORIZES RADIO RECEIVERS TO ONLY "SEE" THE DESIRED SIGNAL WHILE REJECTING ALL OTHER SIGNALS (ASSUMING THE OTHER SIGNALS HAVE DIFFERENT FREQUENCY CONTENT).
- FILTERS ARE USED TO ELIMINATE UNDESIRED HIGH FREQUENCIES (I.E., NOISE) THAT ARE PRESENT ON AC INPUT LINES. ADDITIONALLY, FILTERS ARE USED ON A POWER SUPPLY'S OUTPUT TO REDUCE RIPPLE.
- A CROSSOVER NETWORK IS A NETWORK OF FILTERS USED TO CHANNEL LOW-FREQUENCY AUDIO TO WOOFERS, MID-RANGE FREQUENCIES TO MIDRANGE SPEAKERS, AND HIGH-FREQUENCY SOUNDS TO TWEETERS.
- USED IN AUDIO APPLICATIONS FOR EQUALIZATION PURPOSES.
- USED IN RECEIVERS SUCH AS SUPERHETERODYNE ETC FOR EFFICIENT RECEPTION OF THE BASEBAND SIGNALS.

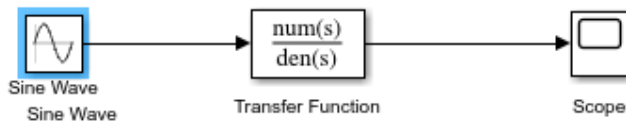QUESTION B.

DESIGNING A LOW-PASS FILTER WITH 0.005Ω RESISTOR AND 0.01F CAPACITOR

A 100V AMPLITUDE WAS SELECTED WITH A FREQUENCY OF 1HZ FOR THE SINE WAVE SOURCE.



QUESTION C.

DETERMINING THE CUT-OFF FREQUENCY

THE CUT-OFF FREQUENCY IS CALCULATED BY $F = \frac{1}{2} * (\pi * R * C)$

WHEN $R = 0.005\Omega$ AND $C = 0.01F$

$$F = 0.5 * \pi * 0.005 * 0.01 = 3189.099 \text{ HZ}$$

QUESTION D.


DESIGN OUTPUT

THE TRANSFER FUNCTION EQUATION FOR THE CIRCUIT IS GIVEN AS

$$(1/RC)/(S + 1/RC)$$

WHEN $R = 0.005\Omega$ AND $C = 0.01F$
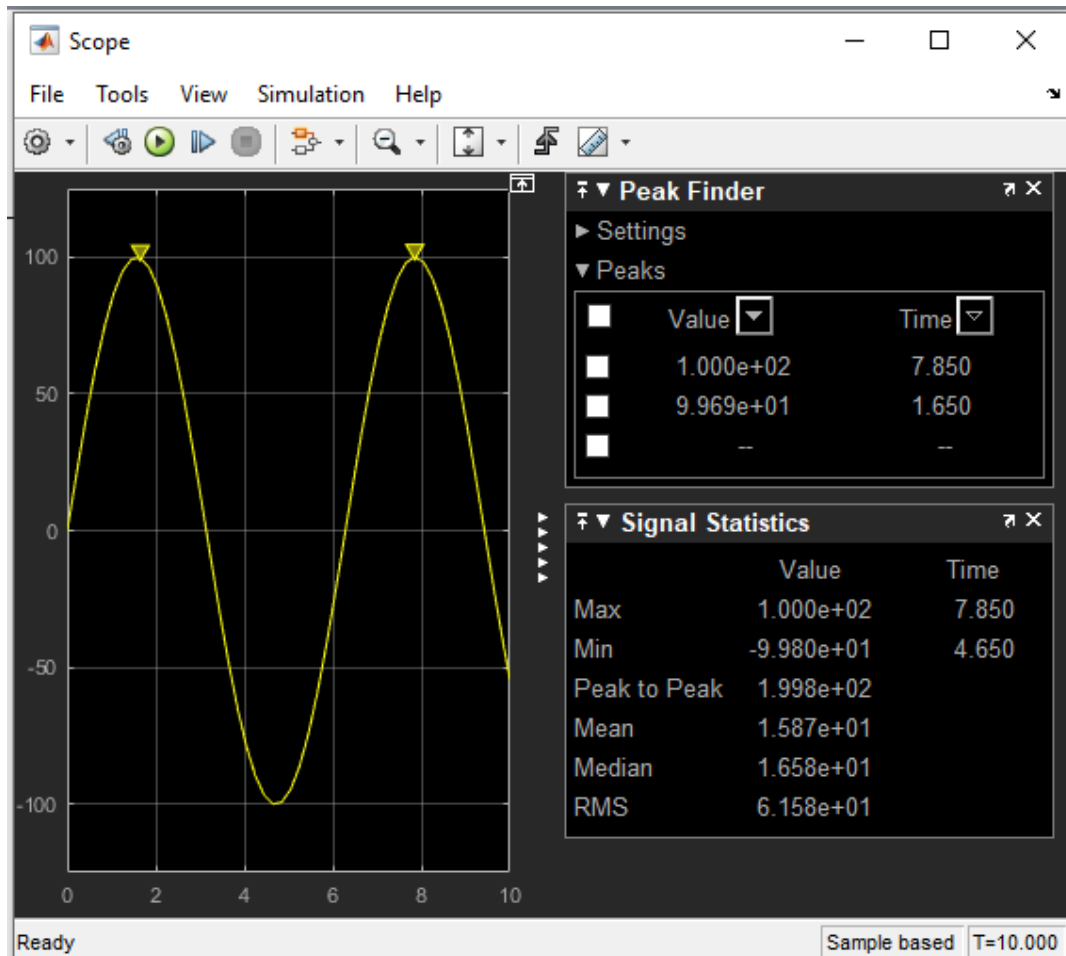
$$\text{TRANSFER FCN} = (1/0.005 * 0.01)/(S + (0.005 * 0.01)) = (20000)/(S + 20000)$$



A. IF TWO SIGNALS OF 5 KΩ AND 2 KΩ ARE PASS THROUGH THE FILTER AT DIFFERENT INTERVALS. DISCUSS YOUR OBSERVATION


WHEN THE SIGNAL OF 5 KΩ IS PASSED THROUGH THE FILTER, THE FOLLOWING RESULT IS OBTAINED:

THE TRANSFER FUNCTION EQUATION FOR THE CIRCUIT IS GIVEN AS

$$(1/RC)/(S + 1/RC)$$

WHEN R= 5000Ω AND C= 0.01F
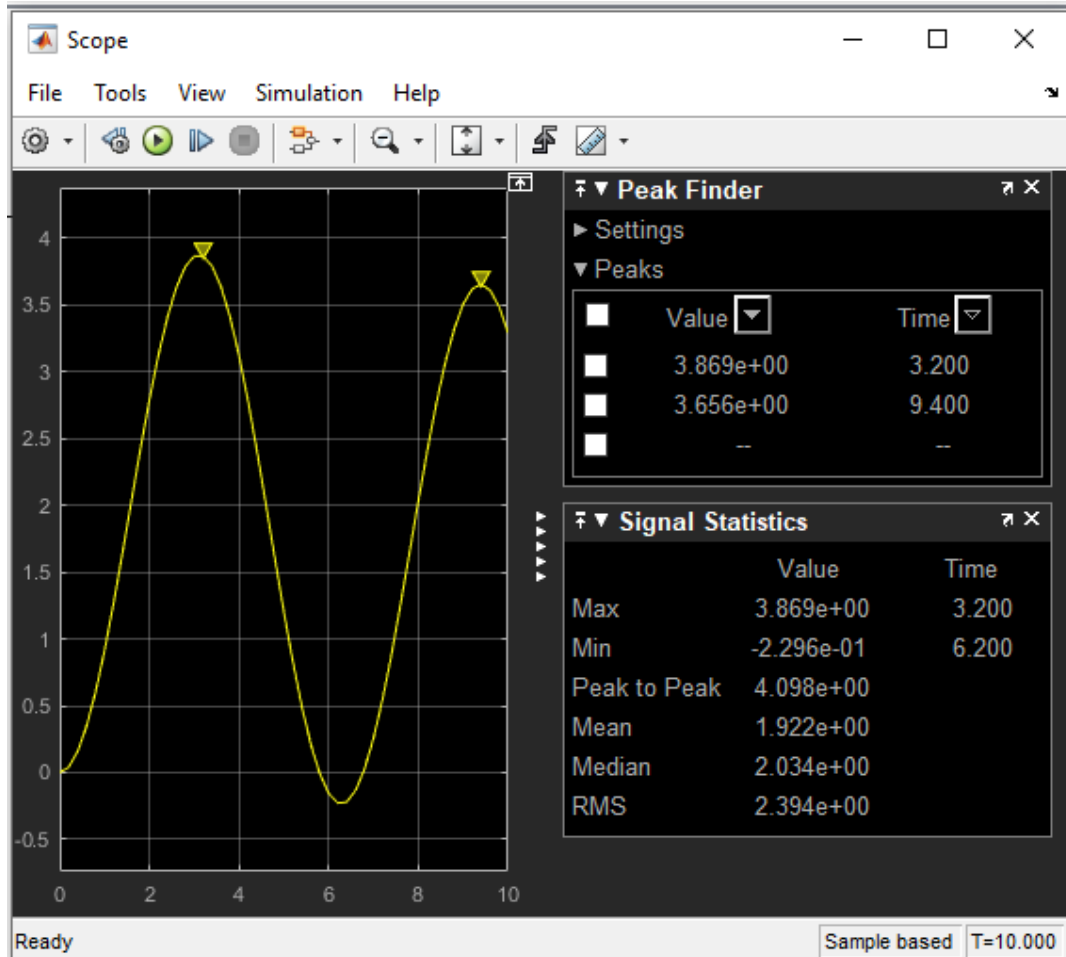
$$\text{TRANSFER FCN}=(1/5000*0.01)/(S + (5000*0.01))= (0.02)/(S+ 0.02)$$




OBSERVATIONS: THE SIGNAL IS ATTENUATED TO 3.869 OHMS

WHEN THE SIGNAL OF 2K OHMS IS PASSED THROUGH THE FILTER THE FOLLOWING RESULTS ARE OBTAINED: THE TRANSFER FUNCTION EQUATION FOR THE CIRCUIT IS GIVEN AS

$$(1/RC)/(S + 1/RC)$$

WHEN R= 2000Ω AND C= 0.01F
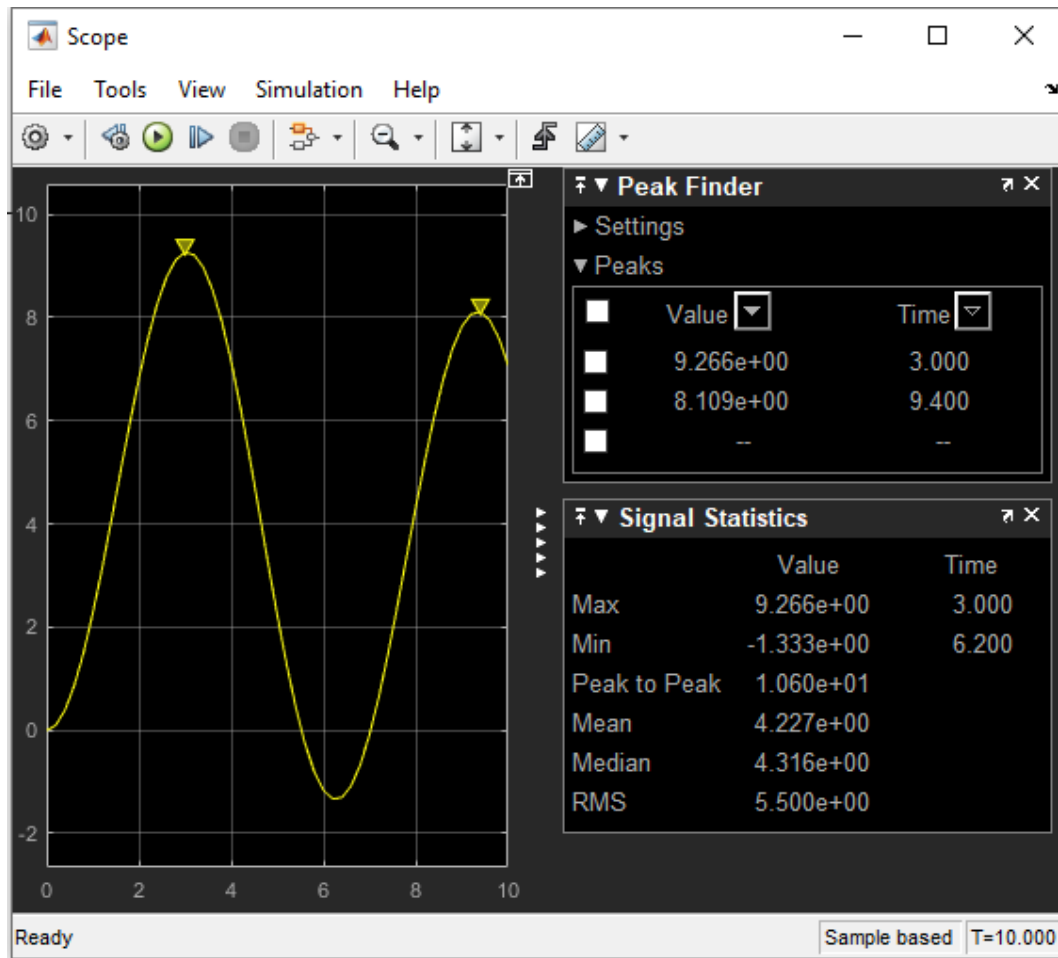
$$\text{TRANSFER FCN} = (1/2000 * 0.01) / (S + (2000 * 0.01)) = (0.05) / (S + 0.05)$$



OBSERVATIONS: THE SIGNAL IS ATTENUATED TO 9.266 OHMS