

NAME : GAIUS DATIABASI IBANGA

MATRIC NUMBER: 17/ENG02/029

DEPARTMENT: COMPUTER ENGINEERING

1. A filter is a circuit capable of passing (or amplifying) certain frequencies while attenuating other frequencies. Thus, a filter can extract important frequencies from signals that also contain undesirable or irrelevant frequencies.

I. Radio communications:

Filters enable radio receivers to only "see" the desired Radio communications: Filters enable radio receivers to only "see" the desired signal while rejecting all other signals (assuming that the other signals have different frequency content).

II. DC power supplies:

Filters are used to eliminate undesired high frequencies (i.e., noise) that are present on AC input lines. Additionally, filters are used on a power supply's output to reduce ripple.

III. Audio electronics:

A crossover network is a network of filters used to channel low-frequency audio to woofers, mid-range frequencies to midrange speakers, and high-frequency sounds to tweeters.

IV. Analog-to-digital conversion:

Filters are placed in front of an ADC input to minimize aliasing

2. Designing a Low-Pass Filter with 0.005Ω resistor and $0.01F$ capacitor


A 100V Amplitude was selected with a frequency of 1Hz for the Sine Wave Source.

3. Determining the Cut-off frequency

The cut-off frequency is calculated by $F = \frac{1}{2} * (\pi * R * C)$

When $R = 0.005\Omega$ and $C = 0.01F$
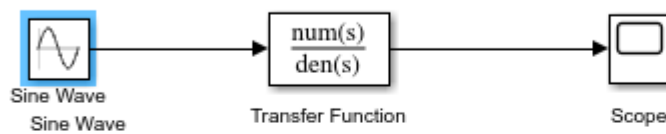
$$F = 0.5 * \pi * 0.005 * 0.01 = 3189.099 \text{ Hz}$$




4. Design Output

The transfer function equation for the circuit is given as

$$(1/RC)/(S + 1/RC)$$

When $R = 0.005\Omega$ and $C = 0.01F$
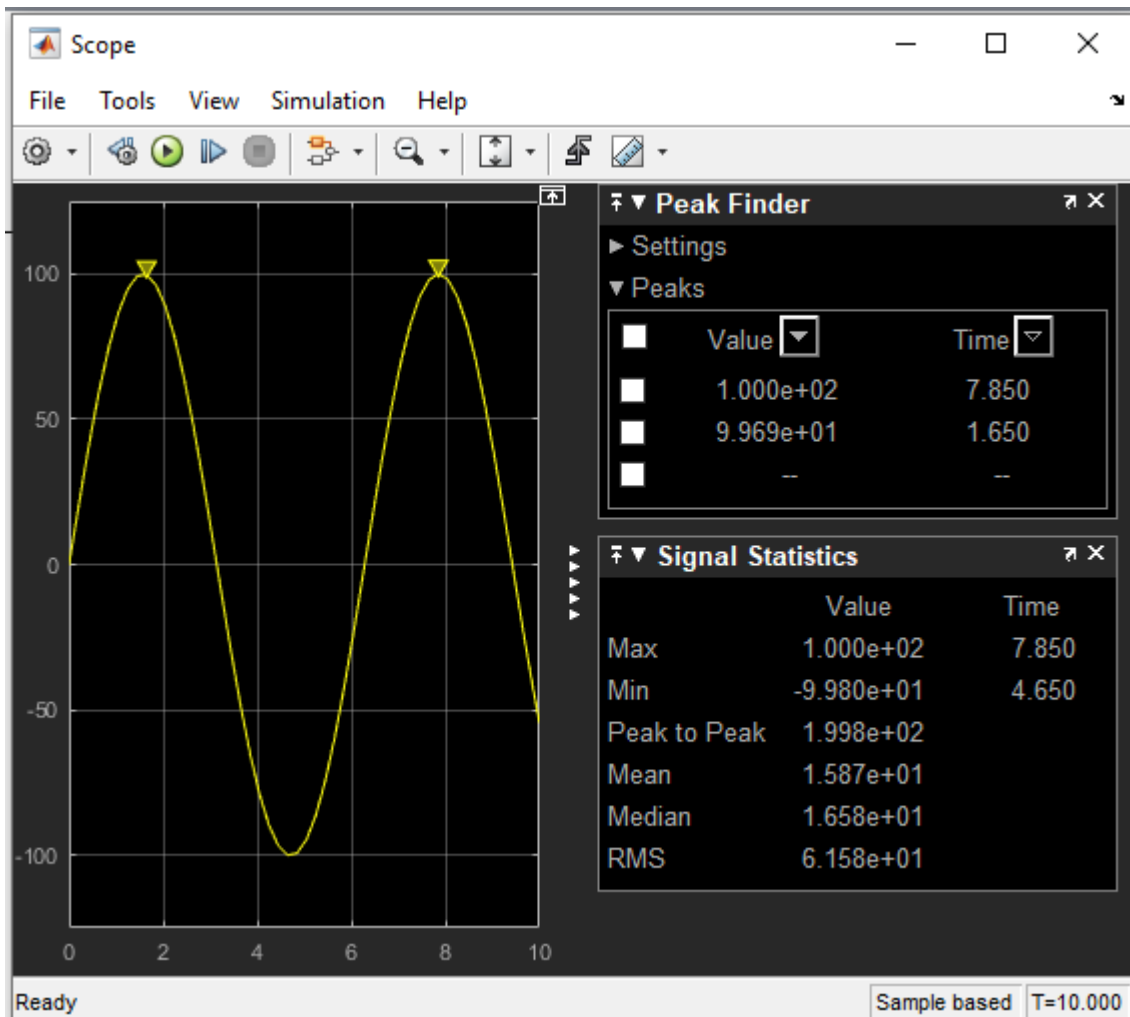
$$\text{Transfer Fcn} = (1/0.005*0.01)/(S + (0.005*0.01)) = (20000)/(s + 20000)$$



A. If two signals of 5 K Ω and 2 K Ω are pass through the filter at different intervals. Discuss your observation


When the signal of 5 K Ω is passed through the filter, the following result is obtained:

The transfer function equation for the circuit is given as

$$(1/RC) / (S + 1/RC)$$

When R= 5000 Ω and C= 0.01F
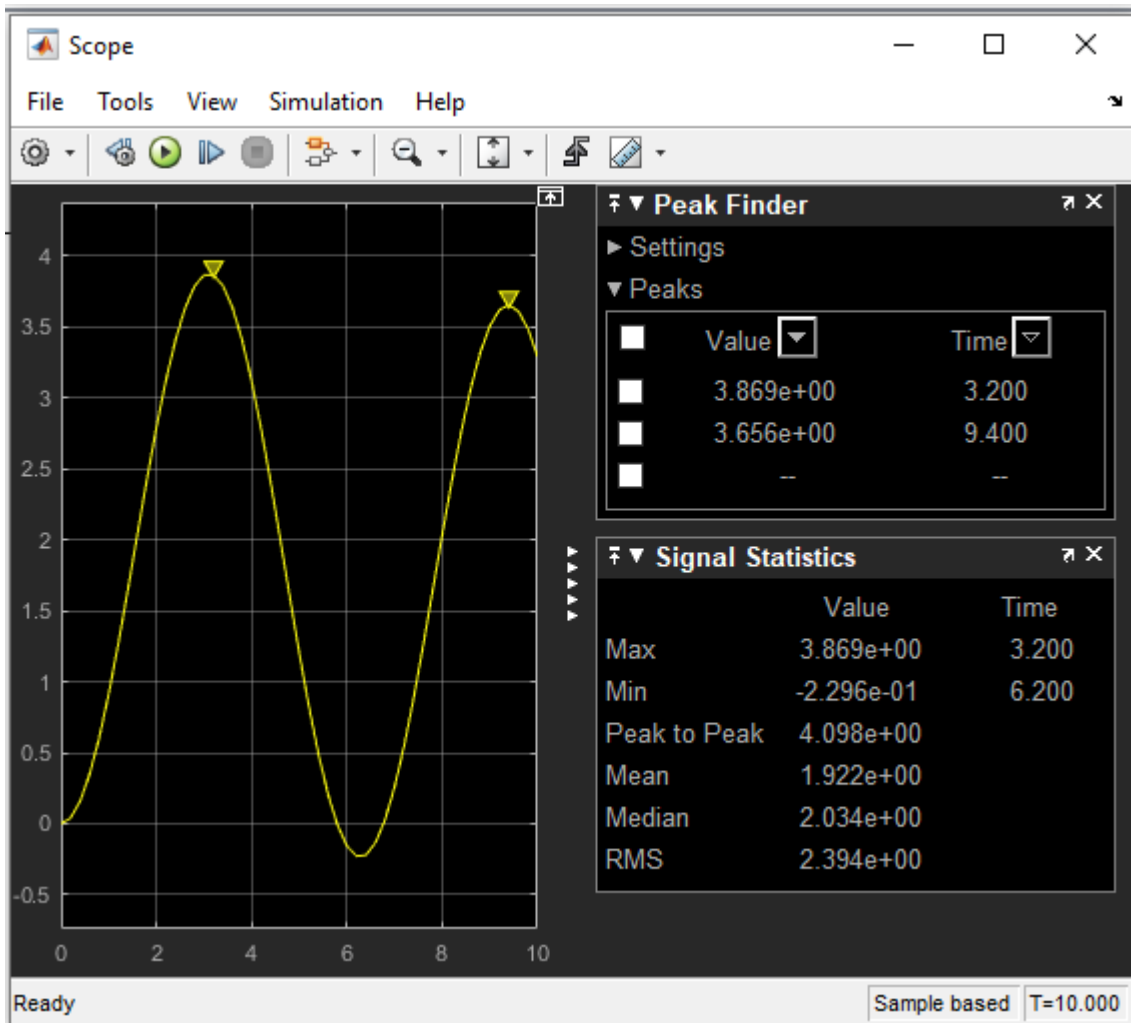
$$\text{Transfer Fcn} = (1/5000 \cdot 0.01) / (S + (5000 \cdot 0.01)) = (0.02) / (s + 0.02)$$




Observation: The signal is attenuated to 3.869 ohms

When the signal of 2K ohms is passed through the filter the following are obtained results: The transfer function equation for the circuit is given as

$$(1/RC) / (S + 1/RC)$$

When $R = 2000\Omega$ and $C = 0.01F$
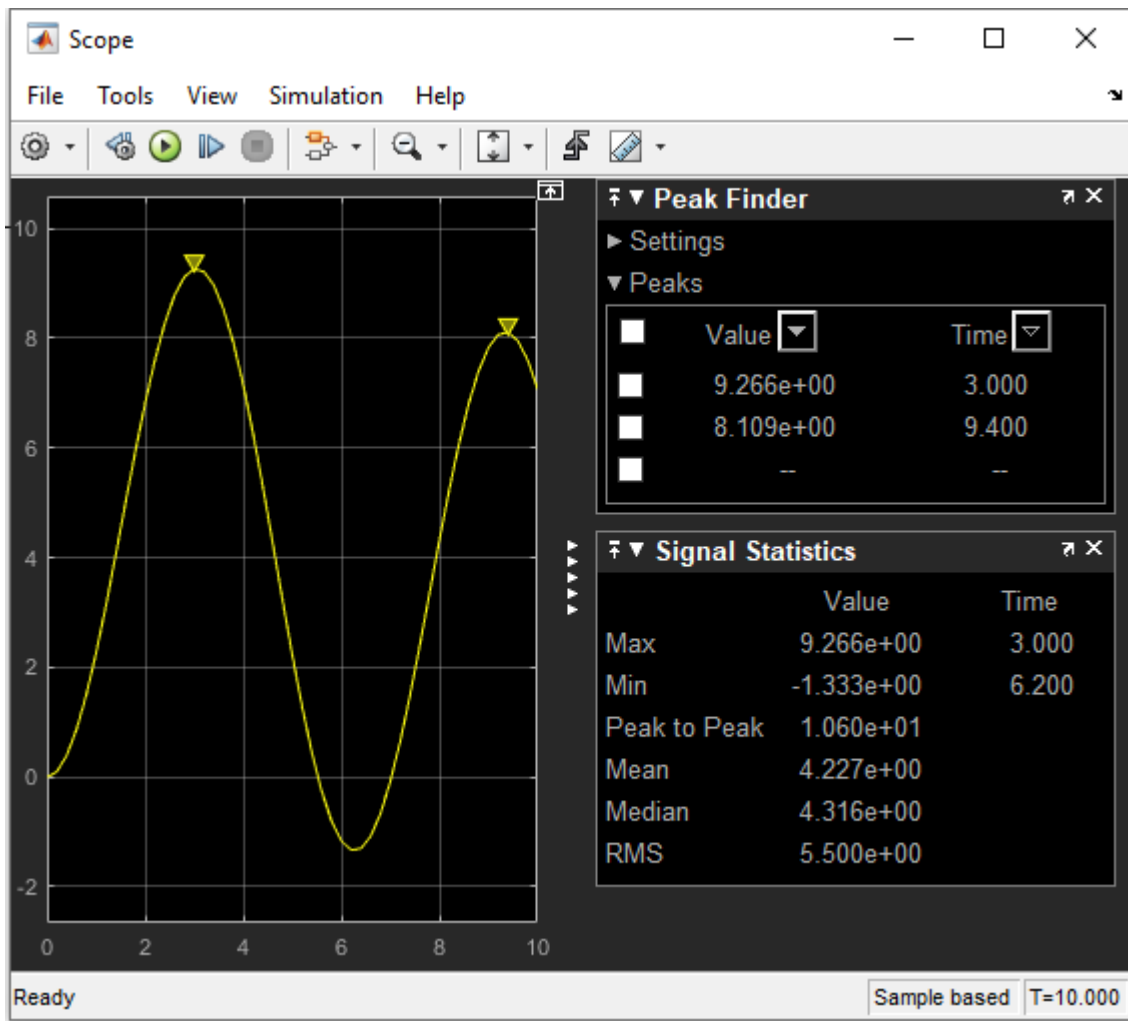
$$\text{Transfer Fcn} = (1/2000 \cdot 0.01) / (S + (2000 \cdot 0.01)) = (0.05) / (s + 0.05)$$



Observation: The signal is attenuated to 9.266 ohms