

## **MECHANICAL ENGINEERING**

### **ENG 342 ASSIGNMENT**


#### **QUESTION A.**

- FILTERS AUTHORIZES RADIO RECEIVERS TO ONLY "SEE" THE DESIRED SIGNAL WHILE REJECTING ALL OTHER SIGNALS (ASSUMING THE OTHER SIGNALS HAVE DIFFERENT FREQUENCY CONTENT).
- FILTERS ARE USED TO ELIMINATE UNDESIRED HIGH FREQUENCIES (I.E., NOISE) THAT ARE PRESENT ON AC INPUT LINES. ADDITIONALLY, FILTERS ARE USED ON A POWER SUPPLY'S OUTPUT TO REDUCE RIPPLE.
- A CROSSOVER NETWORK IS A NETWORK OF FILTERS USED TO CHANNEL LOW-FREQUENCY AUDIO TO WOOFERS, MID-RANGE FREQUENCIES TO MIDRANGE SPEAKERS, AND HIGH-FREQUENCY SOUNDS TO TWEETERS.
- USED IN AUDIO APPLICATIONS FOR EQUALIZATION PURPOSES.
- USED IN RECEIVERS SUCH AS SUPERHETERODYNE ETC FOR EFFICIENT RECEPTION OF THE BASEBAND SIGNALS.

#### **QUESTION B.**

##### **DESIGNING A LOW-PASS FILTER WITH 0.005Ω RESISTOR AND 0.01F CAPACITOR**

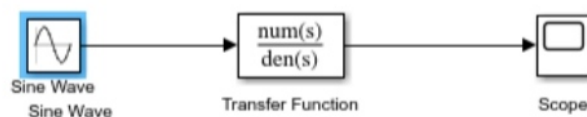**A 100V AMPLITUDE WAS SELECTED WITH A FREQUENCY OF 1HZ FOR THE SINE WAVE SOURCE.**



**QUESTION C.**

**DETERMINING THE CUT-OFF FREQUENCY**

THE CUT-OFF FREQUENCY IS CALCULATED BY  $F = \frac{1}{2}(\pi R C)$

WHEN  $R = 0.005\Omega$  AND  $C = 0.01F$

$$F = 0.5 \cdot \pi \cdot 0.005 \cdot 0.01 = 3189.099 \text{ HZ}$$

**QUESTION D.**


**DESIGN OUTPUT**

THE TRANSFER FUNCTION EQUATION FOR THE CIRCUIT IS GIVEN AS

$$(1/RC)/(S + 1/RC)$$

WHEN  $R = 0.005\Omega$  AND  $C = 0.01F$
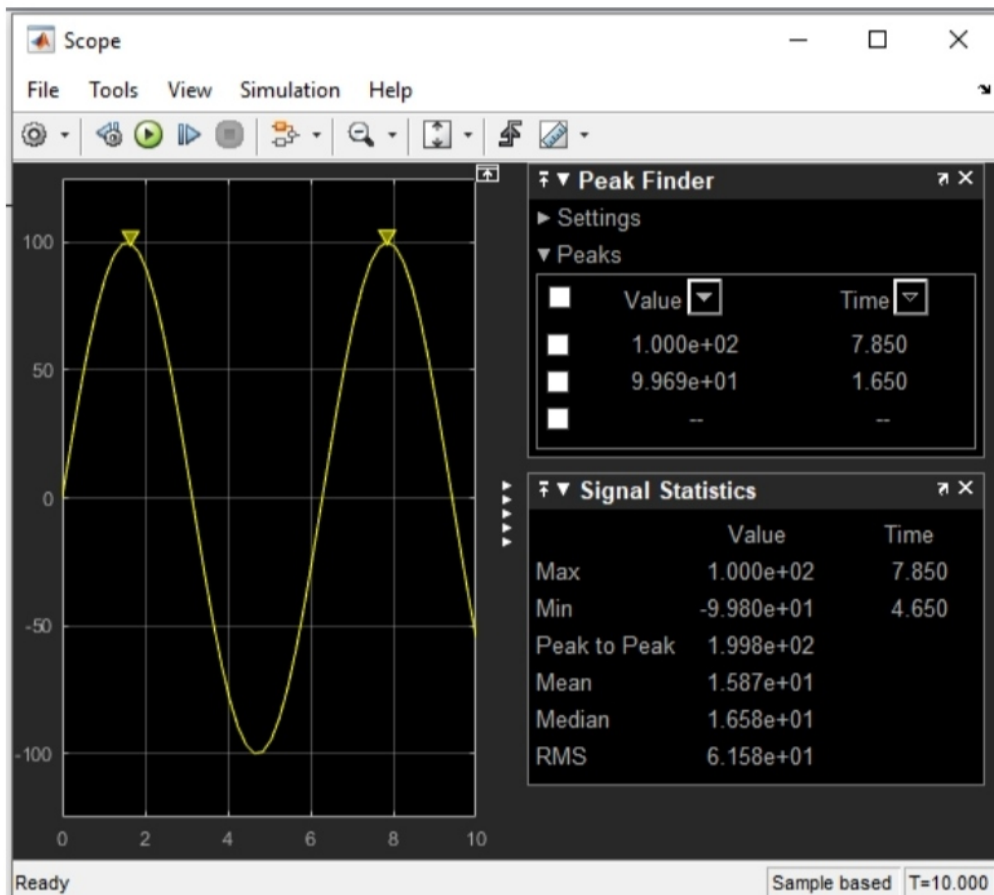
$$\text{TRANSFER FCN} = (1/0.005 \cdot 0.01)/(S + (0.005 \cdot 0.01)) = (20000)/(S + 20000)$$



**A. IF TWO SIGNALS OF 5 KΩ AND 2 KΩ ARE PASS THROUGH THE FILTER AT DIFFERENT INTERVALS. DISCUSS YOUR OBSERVATION**


**WHEN THE SIGNAL OF 5 KΩ IS PASSED THROUGH THE FILTER, THE FOLLOWING RESULT IS OBTAINED:**

THE TRANSFER FUNCTION EQUATION FOR THE CIRCUIT IS GIVEN AS

$$(1/RC)/(S + 1/RC)$$

WHEN R= 5000Ω AND C= 0.01F
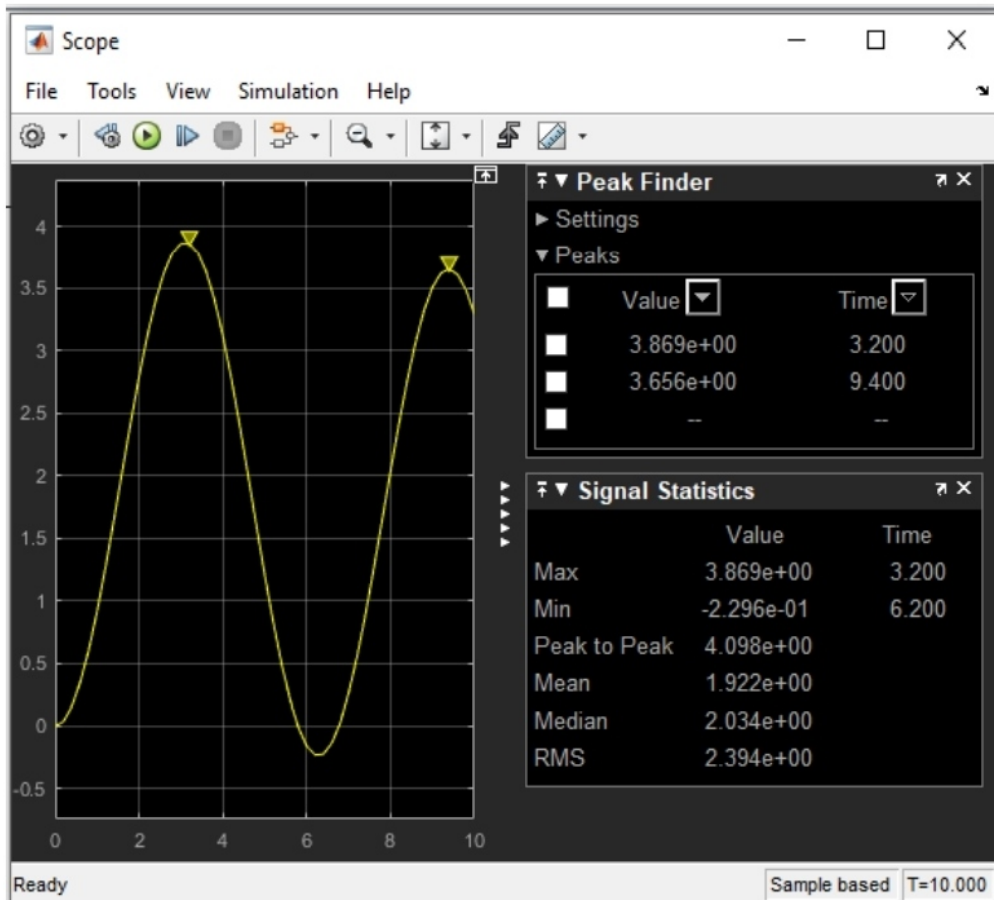
$$\text{TRANSFER FCN}=(1/5000*0.01)/(S + (5000*0.01))= (0.02)/(S+ 0.02)$$




**OBSERVATIONS:** THE SIGNAL IS ATTENUATED TO 3.869 OHMS

**WHEN THE SIGNAL OF 2K OHMS IS PASSED THROUGH THE FILTER THE FOLLOWING RESULTS ARE OBTAINED:** THE TRANSFER FUNCTION EQUATION FOR THE CIRCUIT IS GIVEN AS

$$(1/RC)/(S + 1/RC)$$

WHEN R= 2000Ω AND C= 0.01F

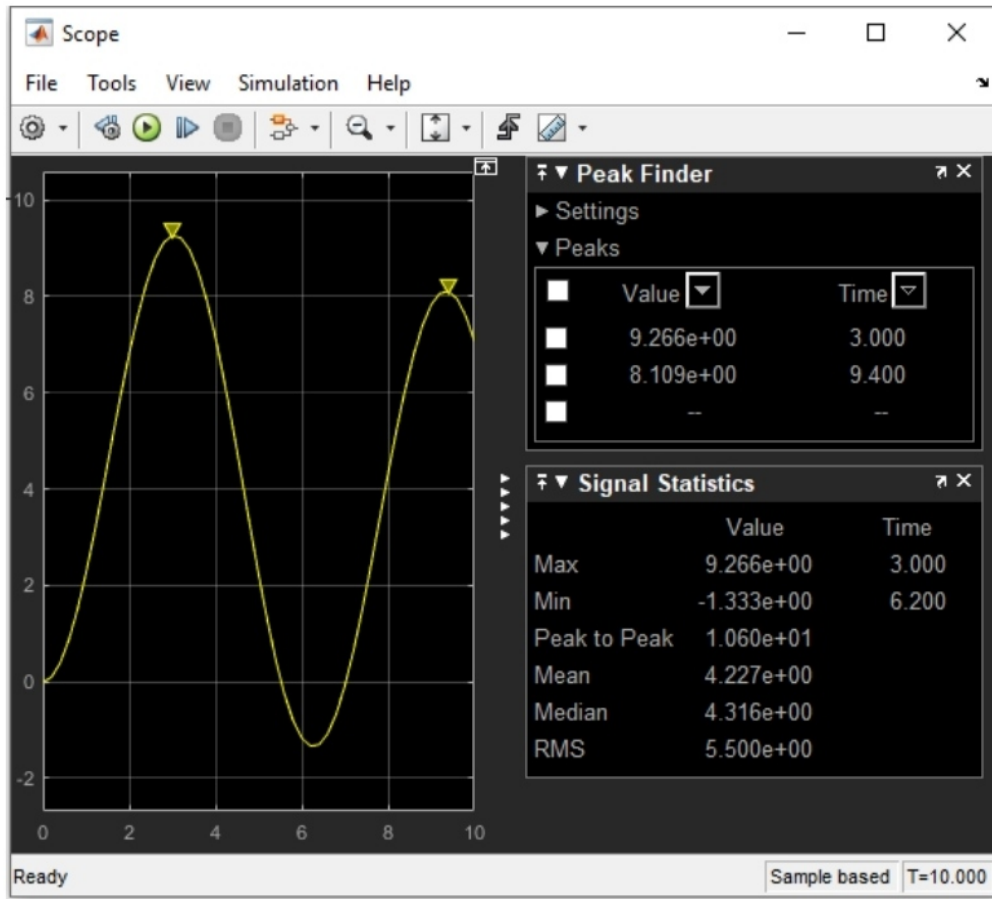TRANSFER FCN=(1/2000\*0.01)/(S + (2000\*0.01))= (0.05)/(S+ 0.05)



**OBSERVATIONS:** THE SIGNAL IS ATTENUATED TO 9.266 OHMS