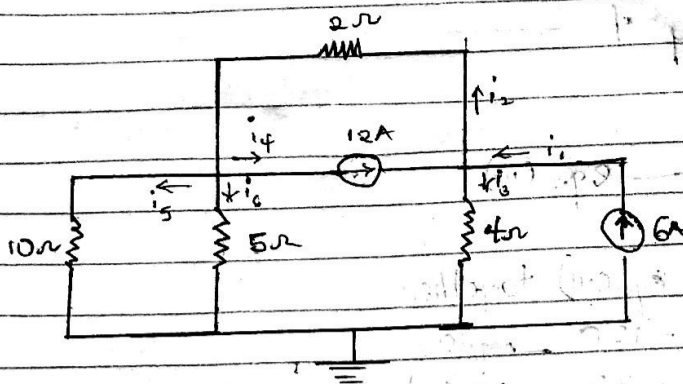


Name: ALEGBELE/E OLUYAFEMI · OLADIPUPO  
 Matric No: 17/ENG04/011  
 Department: ELECT/ELECT

EEE322 ASSIGNMENT SOLUTION



Applying KCL to node 1  
 $i_5 + i_6 + i_4 = i_2$  — eqn (1)  
 $i_5 = \frac{V_2 - 0}{10}$

$i_6 = \frac{V_2 - 0}{5}$

$i_4 = 12$

$i_2 = \frac{V_1 - V_2}{2}$

Substituting into eqn (1)

$\frac{V_2}{10} + \frac{V_2}{5} + 12 = \frac{V_1 - V_2}{2}$

multiply all through by 10

$V_2 + 2V_2 + 120 = 5V_1 - 5V_2$  <collecting like terms>

$V_2 + 2V_2 + 5V_2 - 5V_1 = -120$

$= 8V_2 - 5V_1 = -120$  — eqn (1)

reversing equation

$= 5V_1 - 8V_2 = 120$  — eqn (11)

Applying KCL at node 2

$i_1 + i_4 = i_2 + i_3$

$i_1 = 6A$     $i_4 = 12A$

$i_2 = \frac{V_1 - V_2}{2}$     $i_3 = \frac{V_1 - 0}{4}$

$$6 + 12 = \frac{V_1 - V_2}{2} + \frac{V_1}{4}$$

$$18 = \frac{V_1 - V_2}{2} + \frac{V_1}{4}$$

multiply all through by 4

$$72 = 2V_1 - 2V_2 + V_1$$

collecting like terms

$$72 = 3V_1 - 2V_2 \quad \text{--- eqn (iii)}$$

Putting eqn (ii) and eqn (iii) together

$$5V_1 - 8V_2 = 120 \quad \text{--- eqn (ii)}$$

$$3V_1 - 2V_2 = 72 \quad \text{--- eqn (iii)}$$

Using elimination method:

eqn (iii) is multiplied by 4

$$5V_1 - 8V_2 = 120 \quad \text{--- eqn (iv)}$$

$$12V_1 - 8V_2 = 288 \quad \text{--- eqn (v)}$$

Subtract eqn (iv) from eqn (v)

$$-7V_1 = -168$$

$$V_1 = 24V$$

Substituting  $V_1 = 24V$  into eqn (iv)

$$5(24) - 8V_2 = 120$$

$$120 - 8V_2 = 120$$

$$-8V_2 = 0$$

$$V_2 = 0$$

∴ Current flowing

$$i_1 = 6A$$

$$i_2 = \frac{24 - 0}{2} = 12A$$

$$i_3 = \frac{24 - 0}{4} = 6A$$

$$i_4 = 12A$$

$$i_5 = \frac{24 - 0}{10} = 2.4A$$

$$i_6 = \frac{24 - 0}{5} = 4.8A$$

$$i_1 = 6A$$

$$i_2 = \frac{24 - 0}{2} = 12A$$


$$i_3 = \frac{24 - 0}{4} = 6A$$

$$i_4 = 12A$$

$$i_5 = \frac{10}{10} = 1A$$

$$i_6 = \frac{10}{5} = 2A$$

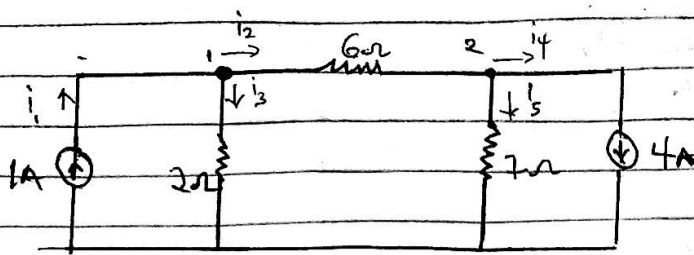$i_1, i_2, i_3, i_4, i_5, i_6$  are 6A, 12A, 6A, 12A, 0, 0 respectively



Applying KCL at node 1

$$i_1 = i_2 + i_3 \quad i_2 = 1A \quad i_3 = \frac{V_1 - V_2}{6} \quad i_5 = \frac{V_1 - 0}{2}$$

Substituting

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

multiply all through by 6

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- eqn (i)}$$

at node 2

$$i_2 = i_4 + i_5 \quad ; \quad i_2 = \frac{V_1 - V_2}{6} \quad i_4 = 4A \quad i_5 = \frac{V_2 - 0}{7}$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

multiply all through by 42

$$7V_1 - 7V_2 = 168 + 6V_2$$

collecting like terms

$$7V_1 - 13V_2 = 168 \quad \text{--- eqn (ii)}$$

bringing eqn (i) and eqn (ii) together

$$4V_1 - V_2 = 6 \quad \text{--- eqn (i)}$$

$$7V_1 - 13V_2 = 168 \quad \text{--- eqn (ii)}$$

multiplying - eqn by 13

$$52V_1 - 13V_2 = 78 \quad \text{--- eqn (iii)}$$

$$7V_1 - 13V_2 = 168 \quad \text{--- eqn (iv)}$$

subtracting eqn (iii) from eqn (iv)

$$45V_1 = -90$$

$$V_1 = -2V$$

substituting  $V_1$  into eqn (i)

$$4(-2) - V_2 = 6$$

$$-8 - V_2 = 6$$

$$-V_2 = 14$$

$$V_2 = -14V$$

to determine currents

$$i_1 = 1A$$

$$i_2 = \frac{12 - (-14)}{2} = \frac{-2 - (-14)}{2} = \frac{12}{2} = 2A$$


$$i_3 = \frac{-2}{2} = -1A$$

$$i_4 = 4A$$

$$i_5 = \frac{-14}{7} = -2A$$

The currents are  $1A, 2A, -1A, 4A, -2A$  are  $i_1, i_2, i_3, i_4, i_5$  respectively.

2.

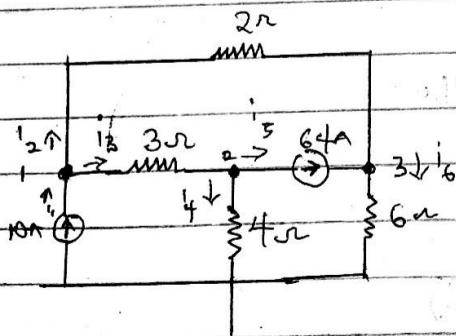

Applying KCL at node 1

$$i_1 = i_2 + i_3 \quad ; \quad i_1 = 10A \quad ; \quad i_2 = \frac{V_1 - V_3}{2} \quad ; \quad i_3 = \frac{V_1 - V_2}{3}$$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3} \quad \leftarrow \text{multiply by 6}$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- eqn (ii)}$$



at node 2

$$i_3 = i_4 + i_5$$

$$\frac{V_1 - V_2}{3} = \frac{V_2 - 0}{4} + 64$$

$$\frac{V_1 - V_2}{3} = \frac{V_2}{4} + 64$$

multiply all through by 12

$$4V_1 - 4V_2 = 3V_2 + 768$$

$$4V_1 - 7V_2 = 768 \quad \text{--- eqn (ii)}$$

at node 3

$$i_6 = i_7 + i_8 + i_9 = i_{10}$$

$$\frac{V_1 - V_3}{2} + 64 = \frac{V_2 - 0}{6}$$

$$\frac{V_1 - V_3}{2} + 64 = \frac{V_2}{6}$$

multiply by 6

$$3V_1 - 3V_3 + 384 = V_2$$

$$3V_1 - 4V_3 = -384$$

reversing equation

$$4V_3 - 3V_1 = 384 \quad \text{--- eqn (iii)}$$

Using matrix rule

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

Using calculator

$$\Delta = -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28) + 2(3072) - 3(2688)$$

$$\Delta_1 = -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45}$$

$$V_1 = 80V$$

$$\Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ 3 & 384 & 4 \end{vmatrix}$$

$$= 5(3072) - 60(16) - 3(3840)$$

$$\Delta_2 = 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & 7 & 768 \\ 3 & 0 & 384 \end{vmatrix}$$

$$= 5(-2688) + 2(3840) - 60(-21)$$

$$\Delta_3 = -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45}$$

$$= 156V$$

Voltages at each node 1, 2, 3

$$V_1 = 80V$$

$$V_2 = -64V$$

$$V_3 = 156V$$