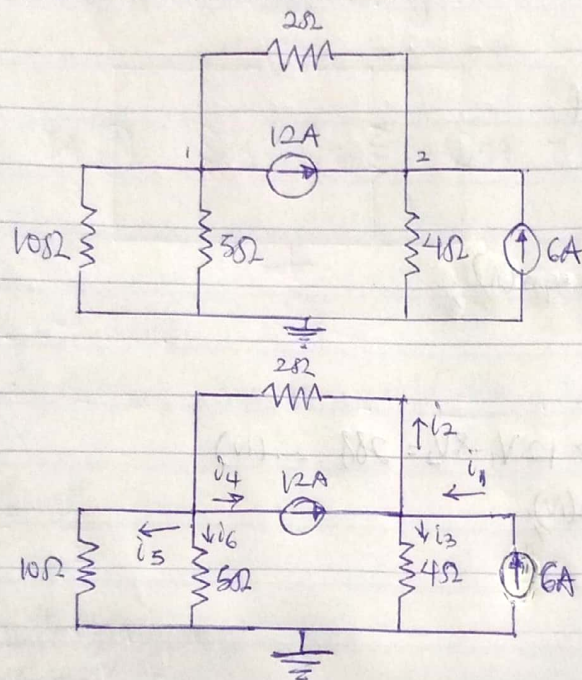


NAME: ODUNFE LEONARD MOTODOREOLUNA

MATRIC NUMBER: 17/ENG02/061

DEPARTMENT: COMPUTER ENGINEERING

① Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below:



Applying KCL to node 1,  $i_5 + i_6 + i_4 = 0$

$$i_5 = \frac{V_2 - 0}{10}, i_6 = \frac{V_2 - 0}{5}, i_4 = 12, i_2 = \frac{V_1 - V_2}{2}$$

$$\frac{V_2}{10} + \frac{V_2}{5} + \frac{12}{1} = \frac{V_1 - V_2}{2} \dots (i)$$

Multiplying eqn (i) through by 10

$$V_2 + 2V_2 + 120 = 5V_1 - 5V_2$$

$$\therefore V_2 + 2V_2 + 8V_2 - 5V_1 = -120$$

$$8V_2 - 5V_1 = -120$$

$$5V_1 - 8V_2 = 120 \dots (ii)$$

Applying KCL at node 2,  $i_1 + i_4 = i_2 + i_3$

$$i_1 = 6A, i_4 = 12, i_2 = \frac{V_1 - V_2}{2}, i_3 = \frac{V_1 - 0}{4}$$

$$6 + 12 = \frac{V_1 - V_2}{2} + \frac{V_1}{4}$$

$$18 = \frac{V_1 - V_2}{2} + \frac{V_1}{4}$$

Multiplying through by 4

$$72 = 2V_1 - 2V_2 + V_1$$

$$72 = 3V_1 - 2V_2 \quad \dots (iii)$$

$$8V_1 - 8V_2 = 120$$

$$3V_1 - 2V_2 = 72$$

Multiplying eqn (iii) by 4  $\rightarrow 12V_1 - 8V_2 = 288 \quad \dots (iv)$

Subtracting eqn (ii) from eqn (iv).

$$12V_1 - 8V_2 = 288$$

$$8V_1 - 8V_2 = 120$$

$$4V_1 = 168$$

$$\therefore V_1 = 24V$$

Substituting  $V_1$  into eqn (iii)

$$3(24) - 2V_2 = 72$$

$$72 - 2V_2 = 72$$

$$72 - 72 = 2V_2$$

$$0 = 2V_2$$

$$\therefore V_2 = 0V$$

The currents flowing through the four resistors, ( $i_2, i_3, i_4$  and  $i_5$ ),

$$i_2 = \frac{V_1 - V_2}{2} = \frac{24 - 0}{2} = \frac{24}{2} = 12A$$


$$i_3 = \frac{V_1}{4} = \frac{24}{4} = 6A$$

$$i_5 = \frac{V_2}{10} = \frac{0}{10} = 0A$$

$$i_6 = \frac{V_2}{6} = \frac{0}{6} = 0 \text{ A}$$

The currents flowing through the four resistors are  $i_2 = 12 \text{ A}$ ,  $i_3 = 8 \text{ A}$ ,  $i_4 = 0 \text{ A}$  and  $i_5 = 0 \text{ A}$ .

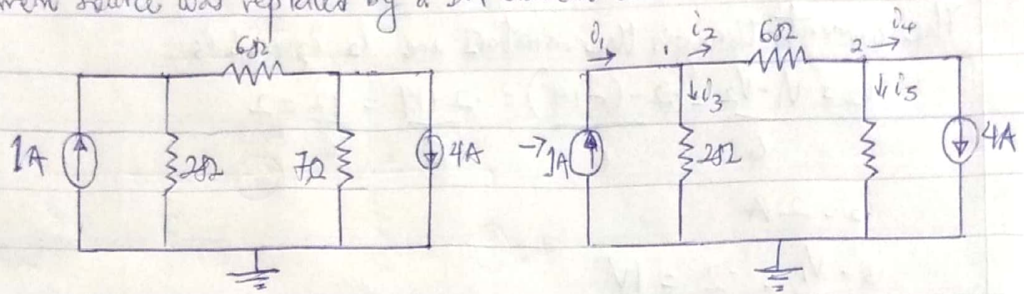(ii) Obtain  $V_1$  and  $V_2$  and the currents through the resistors for the circuit in example (i), if the  $2 \text{ A}$  current source was replaced by a  $1 \text{ A}$  current source



Applying KCL to node 1,

$$i_1 = i_2 + i_3; \quad i_1 = 1 \text{ A}, \quad i_2 = \frac{V_1 - V_2}{6}, \quad i_3 = \frac{V_1}{2}$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

Multiplying through by 6

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \dots (i)$$

Applying KCL to node 2,  $i_2 = i_4 + i_5$

$$i_2 = 4; \quad i_5 = \frac{V_2}{7}$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

Multiplying through by 42

$$7V_1 - 7V_2 = 168 + 6V_2$$

$$7V_1 - 13V_2 = 168 \quad \dots (ii)$$

From eqn (i),  $V_2 = 4V_1 - 6$

Substituting  $V_2$  in eqn (ii)

$$7V_1 - 13(4V_1 - 6) = 168$$

$$7V_1 - 52V_1 + 78 = 168$$

$$-45V_1 = 90$$

$$V_1 = -2V$$

Substituting  $-2V$  for  $V_1$  in eqn (i)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$-V_2 = 14$$

$$V_2 = -14V$$

The currents through the resistors are  $i_2$ ,  $i_3$  and  $i_5$

$$\text{6}\Omega: i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = \frac{-2 + 14}{6} = \frac{12}{6} = 2$$

$$i_2 = 2A$$


$$\text{2}\Omega: i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$i_3 = -1A$$

$$\text{7}\Omega: i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2$$

$$i_5 = -2A$$

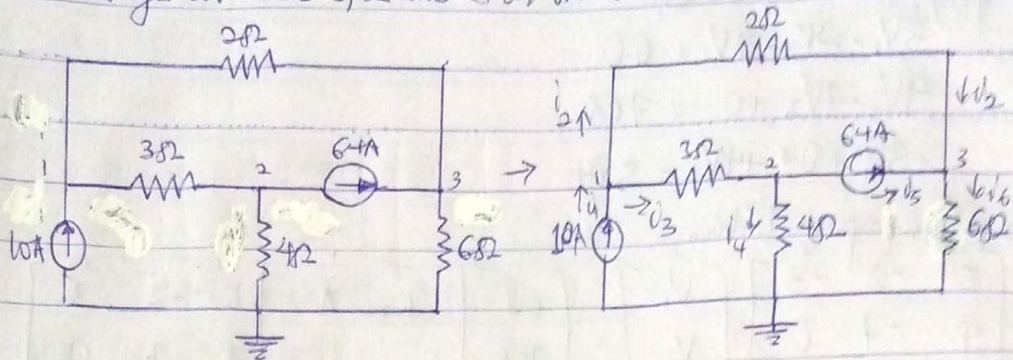② Find the voltages at nodes 1, 2 and 3 in the circuit below:



Applying KCL to node 1,  $i_1 = i_2 + i_3$

$$i_1 = 10A, i_2 = \frac{V_1 - V_3}{2}, i_3 = \frac{V_1 - V_2}{3}, i_4 = \frac{V_2}{4}, i_5 = 6A, i_6 = \frac{V_3}{6}$$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

Multiplying through by 6

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \dots (i)$$

Applying KCL to node 2,  $i_3 = i_4 + i_5$

$$\frac{V_1 - V_2}{3} = \frac{V_2}{4} + \frac{6}{1}$$

Multiplying through by 12

$$4V_1 - 4V_2 = 3V_2 + 768$$

$$4V_1 - 7V_2 = 768 \dots (ii)$$

Applying KCL to node 3,  $i_5 + i_6 = i_2$

$$6 + \frac{V_1 - V_3}{2} = \frac{V_3}{6}$$

Multiplying through by 6

$$38 + 3V_1 - 3V_3 = V_3$$

$$-3V_1 + 4V_3 = 38 \dots (iii)$$

Applying Cramer's Rule,

$$5V_1 - 2V_2 - 3V_3 = 60$$

$$4V_1 - 7V_2 + 0 = 768$$

$$-3V_1 + 0 + 4V_3 = 384$$

In matrix representation,

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix} \text{ where } \Delta = \begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 5 & -7 & 0 & -(-2) & 4 & 0 & -3 & 4 & 0 \\ 0 & 4 & & -3 & 4 & & -3 & 4 & \end{vmatrix} = 5(-28) + 2(16) - 3(-24) \\ = -140 + 32 + 63 = -45$$

$$\Delta = -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix} = 60 \begin{vmatrix} -7 & 0 \\ 0 & 4 \end{vmatrix} + 2 \begin{vmatrix} 768 & 0 \\ 384 & 4 \end{vmatrix} - 3 \begin{vmatrix} 768 & -7 \\ 384 & 0 \end{vmatrix} \\ = 60(-28) + 2(3072) - 3(2688) \\ = -1680 + 6144 - 8064 = -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$V_1 = 80V$$

$$\Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix} = 5 \begin{vmatrix} 768 & 0 \\ 384 & 4 \end{vmatrix} - 60 \begin{vmatrix} 4 & 0 \\ -3 & 4 \end{vmatrix} - 3 \begin{vmatrix} 4 & 768 \\ -3 & 384 \end{vmatrix} \\ = 5(3072) - 60(16) - 3(1536 + 2304) \\ = 15360 - 960 - 3(3840) \\ = 15360 - 960 - 11520 \\ \Delta_2 = 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$V_2 = -64V$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5 \begin{vmatrix} -7 & 768 \\ 0 & 384 \end{vmatrix} + 2 \begin{vmatrix} 4 & 768 \\ -3 & 384 \end{vmatrix} + 60 \begin{vmatrix} 4 & -7 \\ -3 & 0 \end{vmatrix}$$

$$= 5(-2688) + 2(1536 + 2304) + 60(21)$$

$$= -13440 + 2(3840) - 1260$$

$$= -13440 + 7680 - 1260$$

$$\Delta_3 = -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$V_3 = 156V$$

The voltages at the nodes 1, 2 and 3 are

$$V_1 = 80V$$

$$V_2 = -64V$$

$$V_3 = 156V$$