

At Node 1
 $i_1 = i_2 + i_3$
 $1 = \frac{v_1 - v_2}{6} + \frac{v_1}{2}$ (KCL at Node 1)

$6 = v_1 - v_2 + 3v_1$ (KCL at Node 2)
 $6 = 4v_1 - v_2$ (KCL at Node 2)
 $i_2 = i_4 + i_5$ (KCL at Node 2)
 $\frac{v_1 - v_2}{6} = \frac{v_2}{4} + \frac{v_2}{7}$ (KCL at Node 2)

$7(v_1 - v_2) = 168 + 6v_2$ (KCL at Node 2)
 $168 = 7v_1 - 13v_2$ (Equation 1)
 from eqn (1) $v_2 = \frac{7v_1 - 168}{13}$
 Subs $v_2 = \frac{7v_1 - 168}{13}$ in eqn (2)

$168 = 7v_1 - 13 \left(\frac{7v_1 - 168}{13} \right)$
 $168 = 7v_1 - 7v_1 + 168$
 $0 = -13v_2 + 168$
 $v_2 = \frac{168}{13} = 12.92V$
 $v_1 = \frac{168 + 13v_2}{7} = \frac{168 + 13(12.92)}{7} = 40.2V$
 Subs $v_1 = 40.2V$ in eqn (2) $6 = 4(40.2) - v_2$
 $v_2 = 160.8 - 6 = 154.8V$

$v_2 = -8 - 6(0) = -48V$
 $v_1 = 14V$
 current through the resistor
 $i_2 = \frac{v_1 - v_2}{6} = \frac{-2 + 16}{6} = 2A$

$i_3 = \frac{v_1}{2} = \frac{-2}{2} = -1A$
 $i_5 = \frac{v_2}{7} = \frac{-14}{7} = -2A$

$v_1 = 40.2V$
 $v_2 = 154.8V$
 $i_1 = 11.92A$

VA Matrix Representasi E, V, P - 36V

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & 2 & 1 \\ 3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 354 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & 2 & 1 \\ -3 & 0 & 4 \end{vmatrix}$$

$$\Delta = 5(2 \cdot 4 - 0) - 2(16 - 4) - 3(16 - 12)$$

$$= 40 - 2(12) - 3(4) = 40 - 24 - 12 = 4$$

$$\Delta_1 = \begin{vmatrix} 60 & -3 & -3 \\ 768 & 2 & 1 \\ 354 & 0 & 4 \end{vmatrix}$$

$$= 60(2 \cdot 4 - 0) - 3(16 - 4) - 3(3072 - 12)$$

$$= 480 - 3(12) - 3(3060) = 480 - 36 - 9180 = -8736$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-8736}{4} = -2184$$

$$\text{for } V_2: \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 1 \\ -3 & 354 & 4 \end{vmatrix}$$

$$= 5(768 \cdot 4 - 1412) - 60(16 - 4) - 3(2448 - 3)$$

$$= 5(3072 - 1412) - 60(12) - 3(2445) = 5(1660) - 720 - 7335 = 8300 - 720 - 7335 = 245$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{245}{4} = 61.25$$

$$\text{for } V_3: \Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & 2 & 768 \\ -3 & 0 & 354 \end{vmatrix}$$


$$= 5(715.2 - 2592) - 2(7056 - 2148) + 60(12 - 6)$$

$$= 5(456) - 2(4908) + 60(6) = 2280 - 9816 + 360 = -7176$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7176}{4} = -1794$$

$$\therefore V_1 = -2184 \quad V_2 = 61.25 \quad V_3 = -1794$$

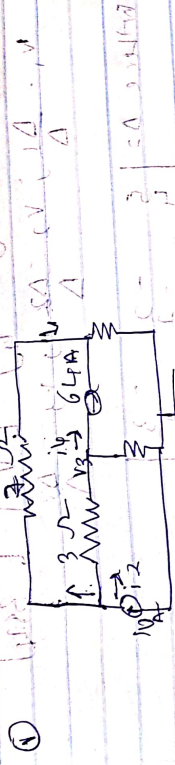Jude - Skema Pénvoutañ
 17 ENG 02 1089
 300L Computer Engineering



At node 1, KCL:
 $3 = 0 + i_1 + i_2 \Rightarrow i_1 + i_2 = 3$

$\Rightarrow 60 = 3CV_1 - V_3 + 2CV_1 - V_2$
 $60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$
 $60 = 5V_1 - 2V_2 - 3V_3 \dots (1)$

At node 2, KCL:
 $i_2 = i_3 + 64 + i_4$
 $64 = i_2 - i_3$
 $64 = \frac{V_1 - V_2}{6} - \frac{V_2 - V_3}{12} \dots (2)$

At node 3, KCL:
 $64 + i_1 = i_5$
 $64 = i_5 - i_1$
 $64 = \frac{V_3 - V_1}{6} - \frac{V_3 - V_4}{6}$
 $64 = \frac{V_3 - V_1}{6} - \frac{V_3 - 0}{6} \dots (3)$

At node 4, KCL:
 $2 = i_4 + i_5$
 $2 = \frac{V_2 - V_3}{12} + \frac{V_3 - V_1}{6}$

Using Cramer's rule:
 $364 = V_1 - 2V_2 - 3V_3 = 768 \dots (1)$
 $4V_1 - 2V_2 - 3V_3 = 768 \dots (2)$
 $4V_1 - 2V_2 - 3V_3 = 768$

100V
 $V_1 = 100$
 $V = 0$

