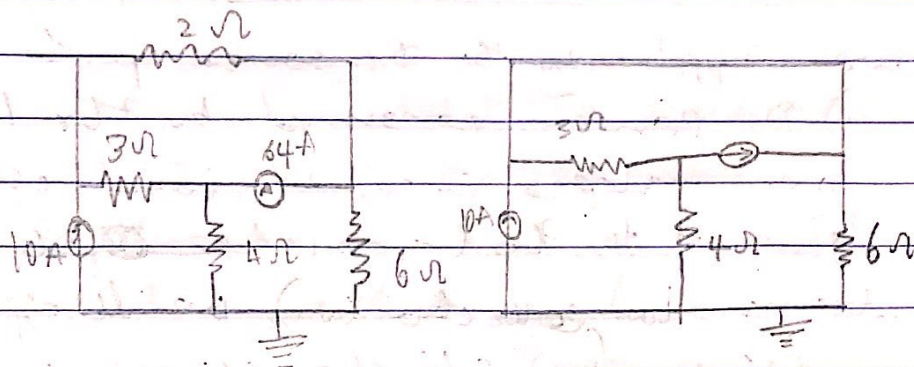


1) Find the voltages at nodes 1, 2 and 3 in the circuit below.



At node 1, KCL:

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{v_1 - v_3}{2} + \frac{v_1 - v_2}{3}$$

$$\Rightarrow 60 = 3(v_1 - v_3) + 2(v_1 - v_2)$$

$$60 = 3v_1 - 3v_3 + 2v_1 - 2v_2$$

$$60 = 5v_1 - 2v_2 - 3v_3 \quad \dots (i)$$

At Node 2, KCL:

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{v_1 - v_2}{3} - \frac{v_2 - 0}{4}$$

$$768 = 4(v_1 - v_2) - 3(v_2 - 0)$$

$$768 = 4v_1 - 4v_2 - 3v_2$$

$$768 = 4v_1 - 7v_2 \quad \dots (ii)$$

At Node 3, KCL:

$$64 + i_1 = i_5$$

$$64 = i_5 - i_1$$

$$64 = \frac{v_3 - 0}{6} - \frac{v_1 - v_3}{2}$$

$$384 = v_3 - 3(v_1 - v_3)$$

$$384 = -3V_1 + 4V_3 \quad \dots \text{(ii)}$$

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \dots \text{(i)}$$

$$4V_1 - 7V_2 = 768 \quad \dots \text{(ii)}$$

$$-3V_1 + 4V_3 = 384 \quad \dots \text{(iii)}$$

In Matrix

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & 7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & 7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-28-6) + 2(16+6) - 3(6-21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & 7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28-6) - 768(-8-6) + 384(0-21)$$

$$= 1680 + 6144 - 8064$$

$$= -3600$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80 \text{ V}$$

$$\text{for } V_2: \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(768 \times 4 - 0) - 4(60 \times 4 - (384 \times 3))$$

$$- 3(0 - (768 \times 3))$$

$$= 2880$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$\text{for } V_3; \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ 3 & 6 & 384 \end{vmatrix}$$


$$= 5((-7 \times 384) - 6) - 4((-2 \times 384 - 6)) - 3((-2 \times 768) - (4 \times 60))$$

$$= -7020$$

$$\therefore V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$\text{Hence } V_1 = 80V, V_2 = -64V, V_3 = 156V$$

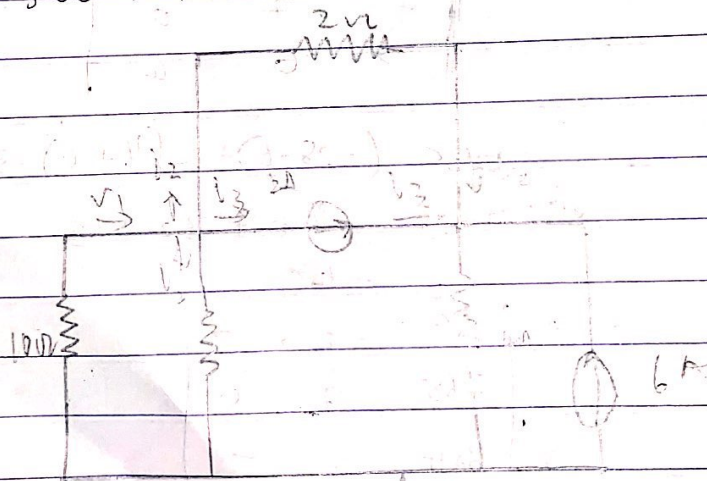2) Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below.




At Node 1, KCL

$$0 = i_1 = 4i_2 + i_4$$

$$0 - V_1 = \frac{V_1 - V_2}{2} + \frac{V_1 - 0}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

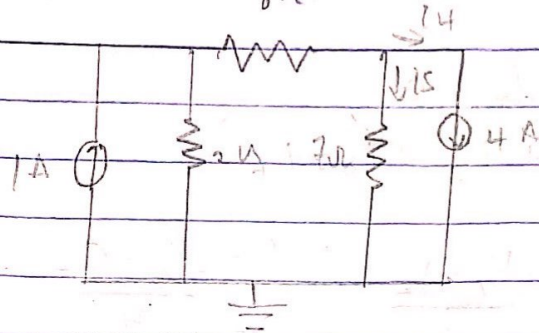obtain v_1 and v_2 and the currents through the resistor in the circuit in example (ii)
 If the 2A current source and replaced by a 1A current source,



At Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{v_1 - v_2}{6} + \frac{v_1}{7}$$

$$6 = v_1 - v_2 + 3v_1$$

$$6 = 4v_1 - v_2 \quad \dots (i)$$

At Node 2

$$i_2 = i_4 + i_3$$

$$\frac{v_1 - v_2}{6} = 4 + \frac{v_2}{7}$$

$$7(v_1 - v_2) = 168 + 6v_2$$

$$168 = 7v_1 - 13v_2 \quad \dots (ii)$$

From equation (i) $v_2 = 4v_1 - 6$

sub $(v_2 = 4v_1 - 6)$ in eqn (ii)

$$168 = 7v_1 - 13(4v_1 - 6)$$

$$168 = 7v_1 - 52v_1 + 78$$

$$90 = -45v_1$$

$$v_1 = \frac{90}{-45}$$

$$v_1 = -2V$$

sub $v_1 = -2$ in eqn (i)

$$6 = 4(-2) - v_2$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

At Node 2

$$i_3 + i_2 + i_5 = i_6$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 20(V_2)$$

$$144 + 4V_1 - 4V_2 = 20V_2$$

$$144 = -4V_1 + 24V_2 \quad \text{--- (ii)}$$

Using Elimination Method

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)} \times -4$$

$$144 = -4V_1 + 24V_2 \quad \text{--- (ii)} \times -8$$

$$-480 = 32V_1 - 20V_2 \quad \text{--- (iii)}$$

$$-152 = 32V_1 - 48V_2 \quad \text{--- (iv)}$$

Subtract eqn (iii) from eqn (iv)

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$V_2 = 24 \text{ V}$$

Subs $V_2 = 24$ in eqn (ii)

$$144 = -4V_1 + 24V_2$$

$$V_1 = \frac{144 - 24V_2}{-4}$$

$$V_1 = 0$$

$$V_1 = 0 \text{ V}, V_2 = 24 \text{ V}$$

$$6 = -8 - v_2$$

$$v_2 = -8 - 6$$

$$v_2 = -14V$$

$$\therefore v_1 = -2V, v_2 = -14V$$

Current through resistors

$$i_2 = \frac{v_1 - v_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{v_1}{2} = \frac{-2}{2} = -1A$$

$$i_5 = \frac{v_2}{7} = \frac{-14}{7} = -2A$$