


KOLAWOLE JOSEPH O.

17/06/2024/038

Elect/Elect.

ENG 322 Assignment

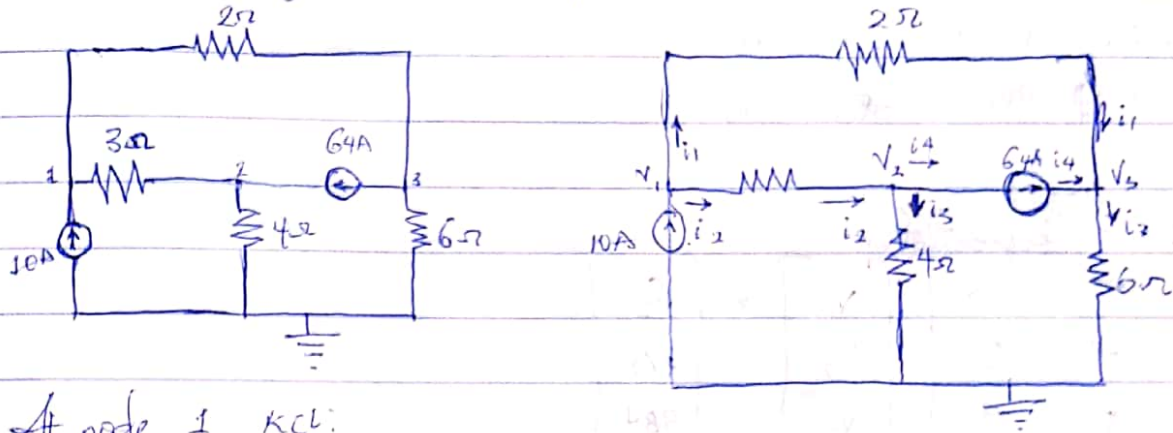1) Find the voltages at nodes 1, 2, 3 in the circuit below



At node 1, KCL:

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{v_1 - v_3}{2} + \frac{v_1 - v_2}{3}$$

$$60 = 3(v_1 - v_3) + 2(v_1 - v_2)$$

$$60 = 3v_1 - 3v_3 + 2v_1 - 2v_2$$

$$60 = 5v_1 - 2v_2 - 3v_3 \dots (i)$$

At node 2, KCL

$$i_2 = i_3 + 64$$

$$i_2 - i_3 = 64$$

$$\frac{v_1 - v_2}{3} - \frac{v_2 - 0}{4} = 64$$

$$4(v_1 - v_2) - 3(v_2 - 0) = 768$$

$$4v_1 - 4v_2 - 3v_2 = 768$$

$$4v_1 - 7v_2 = 768 \dots (ii)$$

At node 3, KCL

$$64 + i_1 = i_5$$

$$64 = i_5 - i_1$$

$$64 = \frac{v_3 - 0}{6} - \frac{v_1 - v_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \quad \dots \quad (iii)$$

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \dots \quad (i)$$

$$4V_1 - 7V_2 - 0 = 768 \quad \dots \quad (ii)$$

$$-3V_1 + 0 + 4V_3 = 384 \quad \dots \quad (iii)$$

In Matrix Representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ 3 & 0 & 4 \end{vmatrix}$$

$$= 5(-28-0) + 2(16+0) - 3(0-21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28-0) - 768(-8-0) - 384(0-21)$$

$$= -1680 + 6144 - 804$$

$$= \frac{-3600}{-45}$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

For V_2 :

Δ_2	5	60	-3
	4	768	0
	-3	384	4

$$= 5[(768 \times 4) - 0] - 4[(60 \times 4) - (384 \times 3)] - 3[0 - (768 \times 3)]$$

$$= 2880$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

For V_3 :

	5	-2	60
	4	-7	768
	-3	0	384


$$= 5[(-7 \times 384) - 0] - 4[(-2 \times 384) - 0] - 3[(-2 \times 768) - (-7 \times 60)]$$

$$= -7020$$

$$\therefore V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

Hence $V_1 = 80V$; $V_2 = -64V$; $V_3 = 156V$

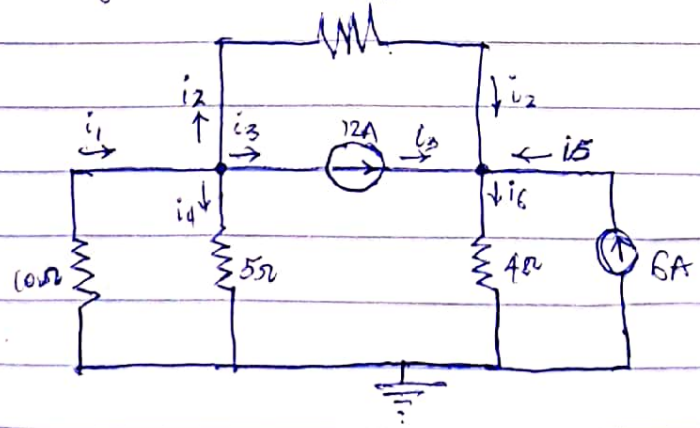2) Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below.



At Node 1, KCL
 $i_1 = i_2 + i_3 + i_4$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_0}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots (i)$$

At Node 2 ; KCL

$$i_8 + i_5 = i_6$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$98 + 4(V_1 - V_2) + 48 = 2V_2$$

$$144 + 4V_1 = 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \dots (ii)$$

Using elimination method ;

$$120 = -8V_1 + 5V_2 \quad \text{--- (i) } \times -4$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii) } \times -8$$

$$-480 = 32V_1 - 20V_2 \quad \text{--- (iii)}$$

$$-1152 = 32V_1 - 48V_2 \quad \text{--- (iv)}$$

Subtract eqn (iii) from (iv)

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$V_2 = \frac{24V}{2}$$

Put $V_2 = 24V$ in eqn (ii)

$$144 = -4V_1 + 6V_2$$

$$144 = -4V_1 + 6(24)$$


$$V_1 = \frac{144 - 6(24)}{4}$$

$$V_1 = \frac{0}{4} = 0$$

$V_1 = 0V$; $V_2 = 24V$

$i_1 = 0A$; $i_2 = 0A$; $i_3 = 6A$; $i_4 = -12A$

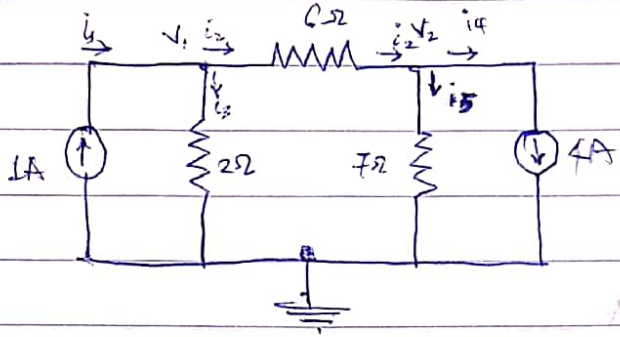ii) Obtain V_1 and V_2 and the currents through the resistors for the circuit in example (i) if the 2A current source was replaced by a 1A current source.



At node 1; KCL

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \dots \quad (i)$$

At node 2; KCL

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 28 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \dots \quad (ii)$$

From eqn (i), $V_2 = 4V_1 - 6$

Put $V_2 = 4V_1 - 6$ in eqn (ii)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45} = -2V$$

Put $V_1 = -2$ in eqn (1)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$

$$\underline{V_2 = -14V}$$


$$\therefore \underline{V_1 = -2V, V_2 = -14V}$$

Current through the resistors:-

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = \underline{2A}$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = \underline{-1A}$$
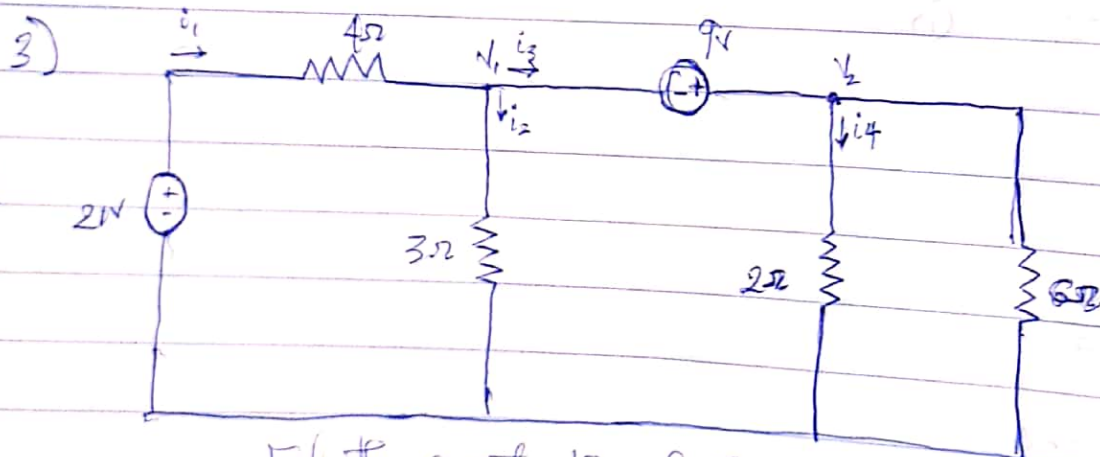
$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = \underline{-2A}$$



Find the current through the 3Ω and 2Ω resistors by using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 2}{4} + \frac{V_1}{2} + \frac{V_2}{6} + \frac{V_2}{2} = 0$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (1)}$$


Using KVL for Loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \dots (ii)$$

$$7V_1 + 8V_2 = 63 \dots (iii)$$

$$-V_1 + V_2 = 9 \dots (iv)$$

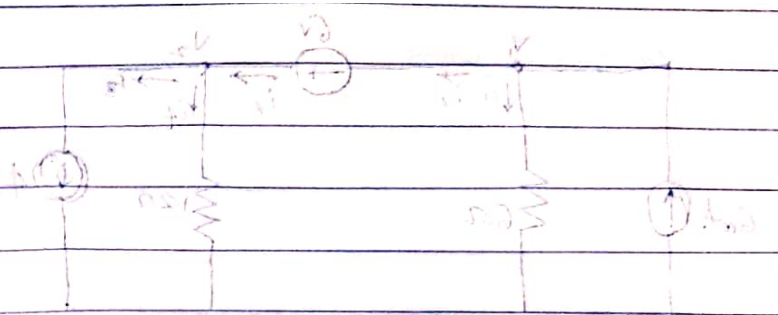

from (iv) let $V_2 = 9 + V_1$

Put V_2 in eqn (iii)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

Put $V_1 = -0.6V$ in eqn (iv)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = \frac{9 - 0.6}{1} = 8.4V$$

$$V_2 = 8.4V$$

$\therefore V_1 = -0.6V$ and $V_2 = 8.4V$


Current through the 3Ω resistor;

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the 2Ω resistor

$$i_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1A$$

4)

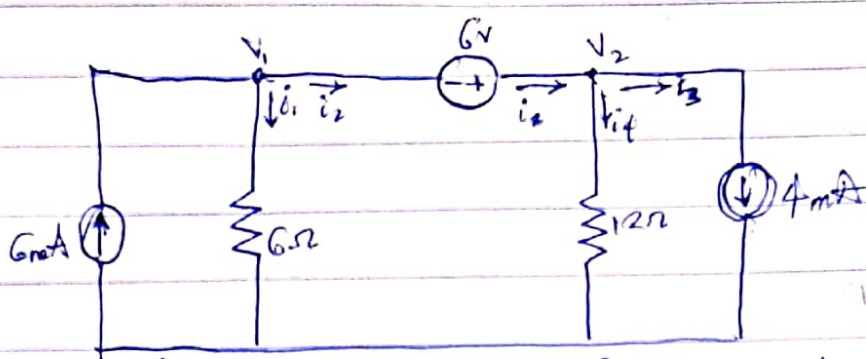

Find the node voltages and the currents through the 6Ω and 12Ω resistors.

Solu

Assuming that $V_1 - V_2 = 6V \Rightarrow i_2$

At node 1; using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = 7V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \dots (i)$$

At node 2

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4mA + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \dots (ii)$$

Using elimination method.

$$36 = 7V_1 - 6V_2 \quad \dots \times 12$$

$$- 48 = 12V_1 - 13V_2 \quad \dots \times 7$$

$$432 = 84V_1 - 72V_2$$

$$- 336 = 84V_1 - 91V_2$$

$$\underline{- 96 = 19V_2}$$

$$V_2 = \frac{96}{19}$$

$$V_2 = 5.1V$$

Putting $V_2 = 5.1V$ in eqn (i)

$$36 = 7V_1 - 6(5.1)$$

$$36 = 7V_1 - 30.6$$

$$7V_1 = 66.6$$

$$V_1 = \frac{66.6}{7}$$

$$V_1 = 9.5V$$

$\therefore V_1 = 9.5V$ and $V_2 = 5.1V$

\therefore Current through the 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

Current through the 12Ω resistor

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A$$

$$\therefore V_1 = 9.5V \quad ; \quad V_2 = 5.1V$$

$$i_1 = 1.58A \quad ; \quad i_4 = 0.43A$$