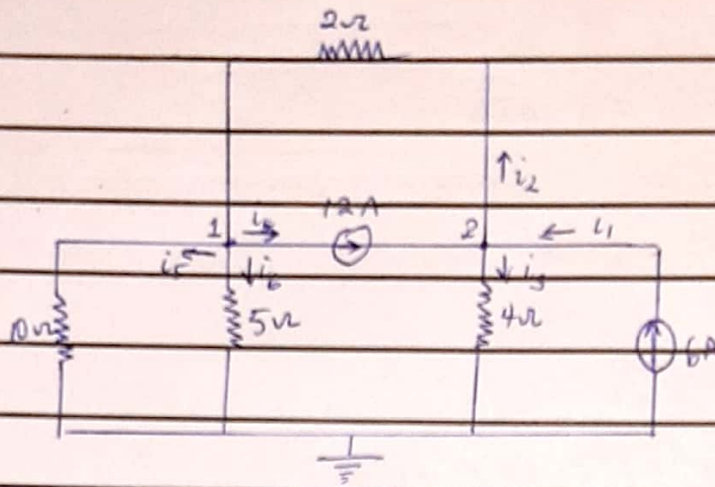


(1) (i)



Applying KCL to node 1

$$i_5 + i_6 + i_4 - i_2 = 0$$

$$i_5 = \frac{V_1 - 0}{10}$$

$$i_6 = \frac{V_1 - 0}{5}$$

$$i_4 = 12$$

$$i_2 = \frac{V_2 - V_1}{2}$$

Substituting in equation 1

$$\frac{V_1}{10} + \frac{V_1}{5} + 12 = \frac{V_2 - V_1}{2}$$

eliminating the fractions multiplying through by 20

$$2V_1 + 4V_1 + 240 = 10V_2 - 10V_1$$

$$16V_1 + 240 = 10V_2 - 10V_1$$

$$26V_1 - 10V_2 = -240$$

$$5V_1 - 2V_2 = -24 \quad \text{--- (1)}$$

Applying KCL to node 2

$$i_1 + i_4 = i_2 + i_3$$

$$i_1 = 6A$$

$$i_4 = 12A$$



$$i_1 = \frac{V_1 - 0}{4} \quad i_2 = \frac{V_1 - V_2}{2}$$

$$6 + 12 = \frac{V_1 - V_2}{2} + \frac{V_1}{4}$$

$$18 = \frac{V_1 - V_2}{2} + \frac{V_1}{4}$$

multiplying through by 4

$$72 = 2V_1 - 2V_2 + V_1$$

$$72 = 3V_1 - 2V_2$$

$$3V_1 - 2V_2 = 72 \quad \text{--- (ii)}$$

Solving eqn (i) and (ii) simultaneously

$$5V_1 - 8V_2 = 120 \quad \text{--- (i)}$$

$$3V_1 - 2V_2 = 72 \quad \text{--- (ii)}$$

Using elimination method

multiply (ii) by 4

$$5V_1 - 8V_2 = 120 \quad \text{--- (i)}$$

$$12V_1 - 8V_2 = 288 \quad \text{--- (iii)}$$

subtract (i) from (iii)

$$-7V_1 = -168$$

$$V_1 = 24V$$

Substituting  $V_1$  in eqn (i)

$$5(24) - 8V_2 = 120$$

$$120 - 8V_2 = 120$$

$$8V_2 = 0$$

$$V_2 = 0$$



∴ Currents flowing

$$i_1 = 6A$$


$$i_2 = \frac{V_1 - V_2}{2} = \frac{24 - 0}{2} = 12A$$

$$i_3 = \frac{V_1 - 0}{4} = \frac{24}{4} = 6A$$

$$i_4 = 12A$$

$$i_5 = \frac{V_2 - 0}{10} = \frac{0 - 0}{10} = 0A$$
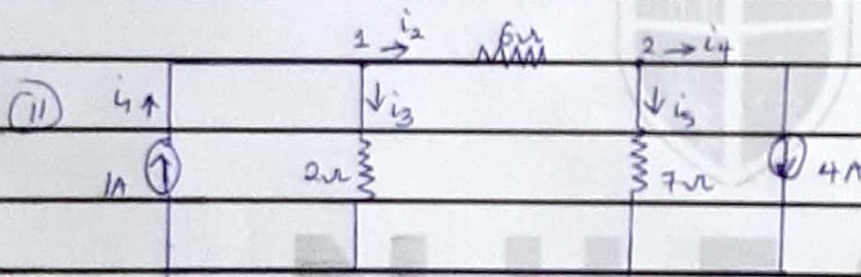
$$i_6 = \frac{V_2 - 0}{5} = \frac{0 - 0}{5} = 0A$$



Applying KCL at node 1

$$i_1 = i_2 + i_3 \quad i_1 = 1A$$

$$i_2 = \frac{V_1 - V_2}{6} \quad i_3 = \frac{V_1 - 0}{2}$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

multiplying through by 6

$$6 = V_1 - V_2 + 3V_1 \quad \text{--- (1)}$$

$$4V_1 - V_2 = 6 \quad \text{--- (2)}$$

Applying KCL at node 2

$$i_2 = i_4 + i_5$$

$$i_2 = 4A \quad i_2 = \frac{V_1 - V_2}{6} \quad i_5 = \frac{V_2 - 0}{7}$$



$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

multiplying through by 42

$$7V_1 - 7V_2 = 168 + 6V_2$$

$$7V_1 - 7V_2 - 6V_2 = 168$$

$$7V_1 - 13V_2 = 168 \quad \text{--- (i)}$$

solving (i) and (ii) simultaneously

$$4V_1 - V_2 = 6 \quad \text{--- (ii)}$$

$$7V_1 - 13V_2 = 168 \quad \text{--- (i)}$$

from (ii)

$$4V_1 - 6 = V_2 \quad \text{--- (iii)}$$

$$7V_1 - 13(4V_1 - 6) = 168$$

$$7V_1 - 52V_1 + 78 = 168$$

$$-45V_1 = 90$$

$$V_1 = \frac{90}{-45} = -2V$$

Putting  $V_1$  in (iii)

$$4(-2) - 6 = V_2$$

$$V_2 = -8 - 6 = -14V$$

$\therefore$  The currents flowing

$$i_1 = 1A$$


$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = \frac{12}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$i_4 = 4A$$

$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$

2)

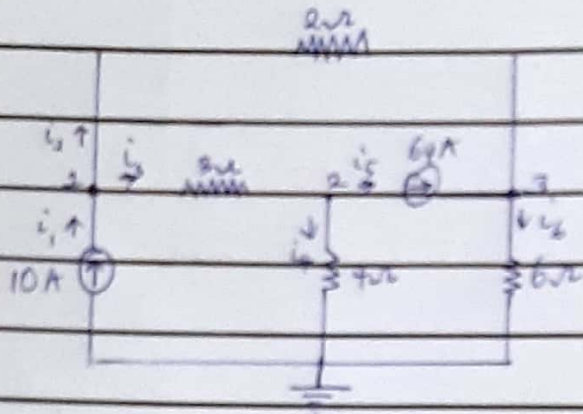

Applying KCL at node 1

$$i_1 = i_2 + i_3$$

$$i_1 = 10A \quad i_2 = \frac{V_1 - V_3}{2} \quad i_3 = \frac{V_1 - V_2}{3}$$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

multiplying through by 6

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (i)}$$

at node 2

$$i_3 = i_4 + i_5$$

$$i_3 = 6A \quad i_3 = \frac{V_1 - V_2}{3} \quad i_4 = \frac{V_2 - 0}{4}$$

$$\frac{V_1 - V_2}{3} = \frac{V_2}{4} + 6$$

multiplying through by 12

$$4V_1 - 4V_2 = 3V_2 + 72$$

$$4V_1 - 7V_2 = 72 \quad \text{--- (ii)}$$

at node 3

$$i_6 = i_2 + i_5$$

$$i_6 = 6A$$



$$i_2 = \frac{V_1 - V_3}{2} \quad i_3 = \frac{V_3 - 0}{6}$$

$$\frac{V_3}{6} = \frac{V_1 - V_3}{2} + 6.4$$

multiplying through by 6

$$V_3 = 3V_1 - 3V_3 + 384$$

$$3V_1 - 4V_3 = -384$$

$$4V_3 - 3V_1 = 384 \quad \text{--- (ii)}$$

solving eqn (i) (ii) and (iii) simultaneously

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (i)}$$

$$4V_1 - 7V_2 = 768 \quad \text{--- (ii)}$$

$$-3V_1 + 4V_3 = 384 \quad \text{--- (iii)}$$

Using Matrix Rule

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & 7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$\Delta = 5 \begin{vmatrix} 7 & 0 \\ 0 & 4 \end{vmatrix} - (-2) \begin{vmatrix} 4 & 0 \\ -3 & 4 \end{vmatrix} - 3 \begin{vmatrix} 4 & 7 \\ -3 & 0 \end{vmatrix}$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & 7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28) + 2(3072) - 3(2688)$$

$$\Delta_1 = -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$



$$\Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ 3 & 384 & 4 \end{vmatrix}$$

$$= 5(3072) - 60(16) - 3(3840)$$

$$\Delta_2 = 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & 7 & 768 \\ 3 & 0 & 384 \end{vmatrix}$$

$$= 5(-2688) + 2(3840) - 60(-21)$$

$$\Delta_3 = -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = \underline{\underline{156V}}$$

$$V_1 = 80V$$

$$V_2 = -64V$$

$$V_3 = 156V$$