

Applying KCL to node 1

$$i_1 + i_2 + i_3 + i_4 + i_5 + i_6 = 0$$

$$i_1 = i_2 + i_3 + i_4 + i_5 + i_6$$

$$12 + \frac{V_1}{5} + \frac{V_1}{10} + \frac{V_1}{2} - V_2 = 0$$

$$\left(\frac{V_1}{5} + \frac{V_1}{10} + \frac{V_1}{2} \right) - \frac{V_2}{2} = -12$$

$$\left(\frac{1}{5} + \frac{1}{10} + \frac{1}{2} \right) V_1 - \left(\frac{1}{2} \right) V_2 = -12$$

$$0.8 V_1 - 0.5 V_2 = -12 \quad \text{eqn (1)}$$

Applying KCL to node 2

$$i_2 + i_6 = i_1 + i_3 + i_5$$

$$12 + 6 = \frac{V_1 - V_2}{2} + \frac{V_2}{4}$$

$$18 = \left(\frac{-1}{2} \right) V_1 + \left(\frac{1}{4} + \frac{1}{2} \right) V_2$$

$$-0.5 V_1 + 0.75 V_2 = 18 \quad \text{eqn (2)}$$

Solving eqn 1 & 2 simultaneously by elimination method

$$0.8 V_1 - 0.5 V_2 = -12 \times 6$$

$$-0.5 V_1 + 0.75 V_2 = 18 \times 4$$

$$0.8 \times 4.8 V_1 - 3 = -72$$

$$-2 V_1 + 3 = 72$$

$$-2 V_1 = 0$$

$$V_1 = 0$$

for V_2 we substitute value of V_1 into eqn ①

$$\therefore 0.8(0) - 0.5V_2 = -12$$

$$-0.5V_2 = -12$$

$$V_2 = \frac{-12}{-0.5}$$

$$V_2 = 24V$$

$$i_4 = \frac{V_1}{10} = \frac{0}{10} = 0$$


$$i_2 = 12$$

$$i_3 = \frac{V_1}{5} = \frac{0}{5} = 0$$

$$i_4 \times i_1 = \frac{V_1 - V_2}{2} = \frac{0 - 24}{2} = -12A$$

$$i_5 = \frac{V_2}{4} = \frac{24}{4} = 6A$$

$$i_6 = 6A$$

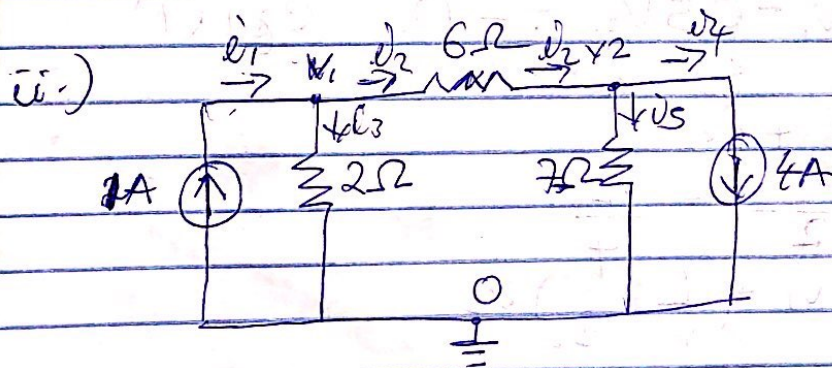

Applying KCL to node 1

$$i_1 = i_2 + i_3 \Rightarrow 1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- eqn ①}$$

Applying KCL to node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7V_1 - 7V_2 = 168 + 6V_2$$

$$7V_1 - 13V_2 = 168 \quad \text{--- eqn (2)}$$

from eqn (1) $V_2 = 4V_1 - 6$
 Substitute $V_2 = 4V_1 - 6$ for V_2 in eqn (2)

$$7V_1 - 13(4V_1 - 6) = 168$$

$$7V_1 - 52V_1 + 78 = 168$$

$$-45V_1 = 90$$

$$V_1 = -2 \text{ V}$$

for V_2 , substitute $V_1 = -2$ into eqn (1)

$$V_2 = 4(-2) - 6$$

$$V_2 = -8 - 6$$

$$V_2 = -14 \text{ V}$$

$$i_1 = 1 \text{ A}$$


$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = \frac{12}{6} = 2 \text{ A}$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1 \text{ A}$$

$$i_4 = 4 \text{ A}$$

$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2 \text{ A}$$

2.)

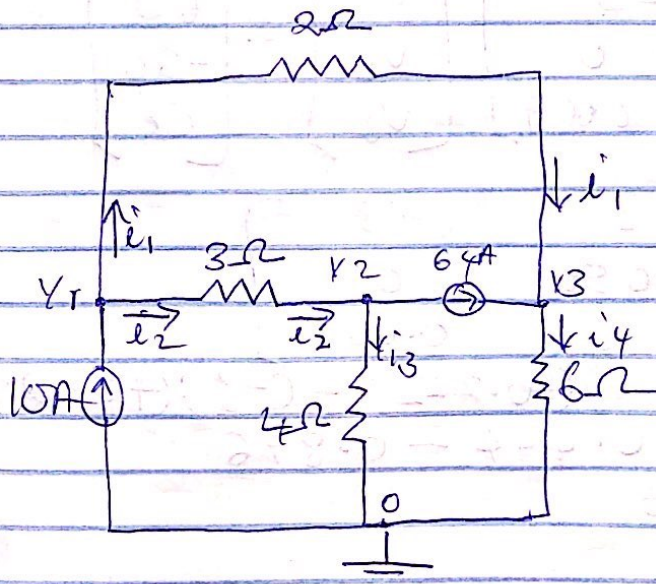

at node 1

$$-10 + i_1 + i_2 = 0$$

$$-10 + \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3} = 0$$

$$5V_1 - 2V_2 - 3V_3 = 60 \text{ --- eqn (1)}$$

Applying KCL at node 2

$$i_3 + 64 + \frac{V_2 - V_1}{3} = 0$$

$$i_3 + 64 + i_2 = 0$$

$$\frac{64}{4} + \frac{V_2 - V_1}{3} = -64$$

$$\left(\frac{1}{4} + \frac{1}{3} \right) V_2 - \frac{1}{3} V_1 = -64 \text{ --- eqn (2)}$$

Applying KCL to node 3

$$i_4 + i_3 - 64 = 0$$

$$\frac{V_3}{6} + \frac{V_3 - V_1}{2} - 64 = 0$$

$$\left(\frac{1}{6} + \frac{1}{2} \right) V_3 - \frac{1}{2} V_1 = 64 \text{ --- eqn (3)}$$

Using Cramer's rule

set the augmented matrix

$$\begin{bmatrix} V_1 & V_2 \\ 5 & -2 & -3 \\ -0.333 & -0.583 & 0 \\ -0.5 & 0 & 0.667 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ -64 \\ 64 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 5 & -2 & -3 \\ -0.333 & -0.583 & 0 \\ -0.5 & 0 & 0.667 \end{bmatrix}$$

$$= 5(0.889) - (-2)(-0.222) + (-3)(+0.292)$$

$$= 1.945 - 0.444 - 0.876$$

$$\Delta = 0.625$$

$$\Delta_1 = \begin{bmatrix} 60 & -2 & -3 \\ -64 & 0.583 & 0 \\ 64 & 0 & 0.667 \end{bmatrix}$$

$$\begin{aligned} &= 60(0.389) - (-2)(-42.688) + (-3)(0 - 37.31) \\ &= 23.34 - 85.376 + 111.936 \\ &= 49.9 \approx 50 \end{aligned}$$

$$\Delta_2 = \begin{bmatrix} 5 & 60 & -3 \\ -0.333 & -64 & 0 \\ -0.5 & 64 & 0.667 \end{bmatrix}$$

$$\begin{aligned} &= 5(-42.688) - 60(-0.222) + (-3)(-21312 - 32) \\ &= -213.44 + 13.32 + 32 \times 3 + 159.94 \\ &= -40.18 \end{aligned}$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{50}{0.625} = 80 \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-40 \cdot 18}{0.625} = -64 \cdot 3 \approx -64$$

For V_3 substitute V_1 & V_2 into eqn ①

$$5(80) - 2(-64) - 3V_3 = 60$$

$$400 + 128 - 60 = 3V_3$$

$$468 = 3V_3$$

$$V_3 = \frac{468}{3}$$

$$V_3 = 156 \text{ V}$$