

EZEGBIDI CLEMENTINA ONYINYECHUKWU


17/ENG 04/027

11-may-2020

ELECTRICAL AND ELECTRONICS ENGINEERING

Circuit Theory II Assignment FTI

Question 1

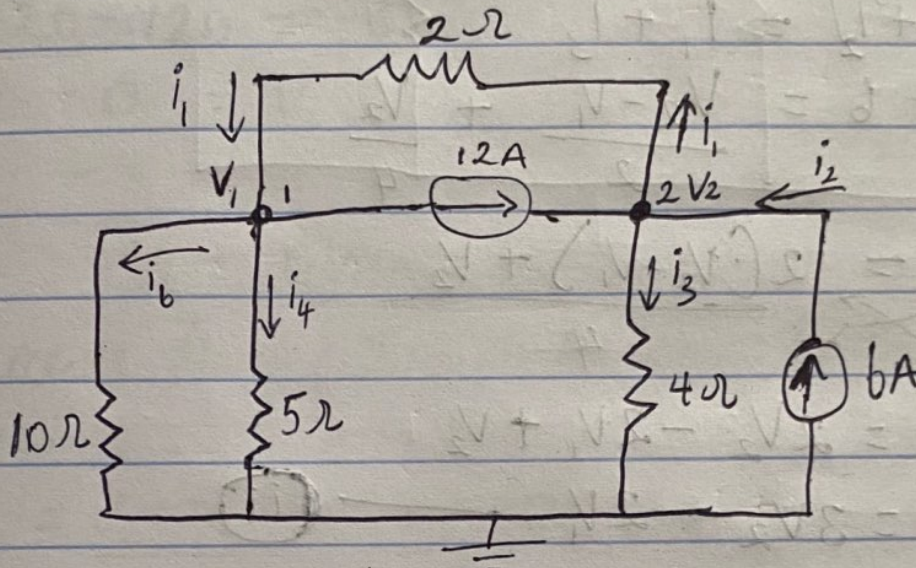

Soln

Applying KCL at node 1

$$i_1 = i_b + i_4 + 12$$

$$\frac{V_2 - V_1}{2} = \frac{V_1}{10} + \frac{V_1}{5} + 12$$

$$\frac{V_2 - V_1}{2} = \frac{V_1 + 2V_1 + 120}{10}$$

$$\frac{5(V_2 - V_1)}{10} = \frac{V_1 + 2V_1 + 120}{10}$$

$$5V_2 - 5V_1 = V_1 + 2V_1 + 120$$

$$5V_2 - 5V_1 - V_1 - 2V_1 = 120$$

$$5V_2 - 8V_1 = 120 \quad \text{--- (i)}$$

Applying KCL at node 2

$$12 + \bar{i}_2 = \bar{i}_1 + \bar{i}_3$$

$$12 + 6 = \frac{V_2 - V_1}{2} + \frac{V_2}{4}$$

$$18 = \frac{2(V_2 - V_1) + V_2}{4}$$

$$72 = 2V_2 - 2V_1 + V_2$$

$$72 = 3V_2 - 2V_1 \quad \text{--- (ii)}$$

recalling:

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

$$72 = -2V_1 + 3V_2 \quad \text{--- (ii)}$$

Applying elimination method

→ multiplying eqn (ii) by (4)

$$120 = -8V_1 + 5V_2$$

$$288 = -8V_1 + 12V_2$$

$$\frac{-168}{-7} = \frac{-7V_2}{-7}$$

$$V_2 = \underline{\underline{24 \text{ Volts}}}$$

Substituting the values of $V_2 = 24 \text{ Volt}$ into eqn (1)

$$120 = -8V_1 + 5(24)$$

$$120 - 120 = -8V_1$$

$$\frac{0}{-8} = V_1$$

$$V_1 = \underline{\underline{0 \text{ Volts}}}$$

⇒ The Currents flowing through Resistors: $6\Omega, 2\Omega, 5\Omega, 4\Omega$ are:


$$i_1 = \frac{V_2 - V_1}{2} = \frac{24 - 0}{2} = 12 \text{ A}$$

$$i_6 = \frac{V_1}{10} = \frac{0}{10} = 0 \text{ A}$$

$$i_4 = \frac{V_1}{5} = \frac{0}{5} = 0 \text{ A}$$

$$i_3 = \frac{V_2}{4} = \frac{24}{4} = 6 \text{ A}$$

Question 2

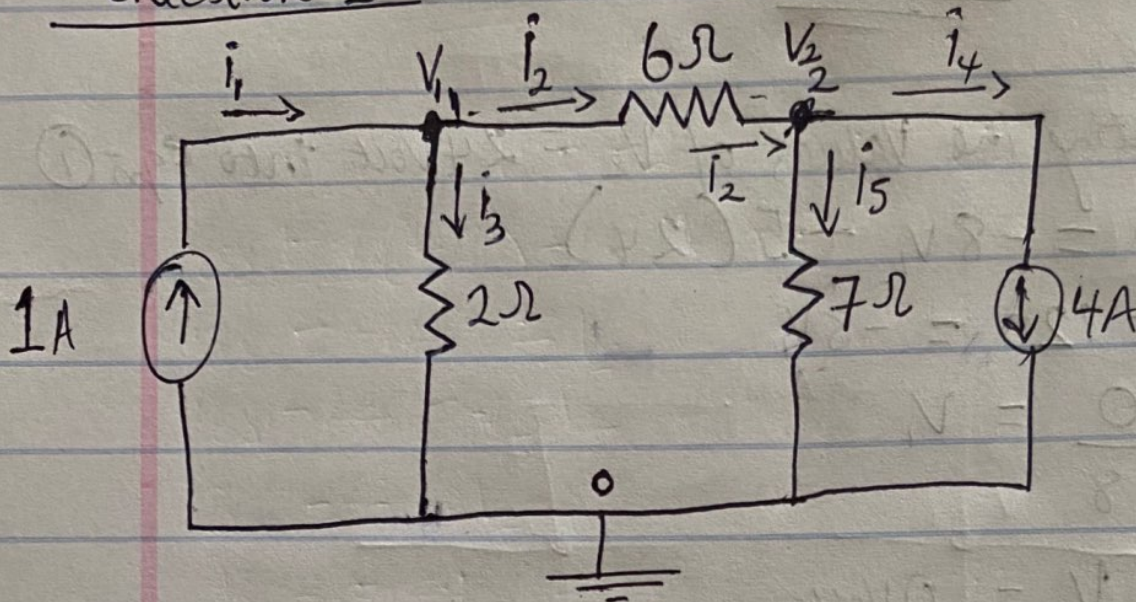

Soln

Applying KCL at node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$1 = \frac{V_1 - V_2 + 3V_1}{6}$$

$$6 = 4V_1 - V_2$$

Applying KCL at node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = \frac{4}{1} + \frac{V_2}{7}$$

$$\frac{V_1 - V_2}{6} = \frac{28 + V_2}{7}$$

$$\underline{7(V_1 - V_2) = 6(28 + V_2)}$$

$$\underline{(7V_1 - 7V_2 = 168 + 6V_2)} \times \cancel{42} \text{ (multiply Through)}$$

$\cancel{42}$ by 42

$$7V_1 - 7V_2 = 168 + 6V_2$$

$$7V_1 - 7V_2 - 6V_2 = 168$$

$$7V_1 - 13V_2 = 168 \quad \text{--- (2)}$$

recalling

$$6 = 4V_1 - V_2 \quad \text{--- (1)}$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (2)}$$

from eqn (1)

$$-V_2 = 6 - 4V_1$$

$$\therefore V_2 = -6 + 4V_1 \quad \text{--- (*)}$$

Putting eqn (*) into eqn (2)

$$168 = 7V_1 - 13(-6 + 4V_1)$$

$$168 = 7V_1 + 78 - 52V_1$$

$$168 - 78 = -45V_1$$

$$90 = -45V_1$$

$$V_1 = \underline{\underline{-2 \text{ Volt}}}$$

Substituting $V_1 = -2$ into eqn (1)

$$168 = 7(-2) - 13(V_2)$$

$$168 = -14 - 13V_2$$

$$168 + 14 = -13V_2$$

$$182 = -13V_2$$

$$V_2 = \underline{\underline{-14 \text{ Volts}}}$$


→ The currents flowing through resistors: 6Ω , 7Ω & 2Ω includes

$$I_3 = \frac{V_1}{2} = \frac{-2}{2} = -1 \text{ A}$$

$$I_2 = \frac{V_1 - V_2}{6} = 2 \text{ A}$$

$$I_5 = \frac{V_2}{7} = -2 \text{ A}$$

Question 3

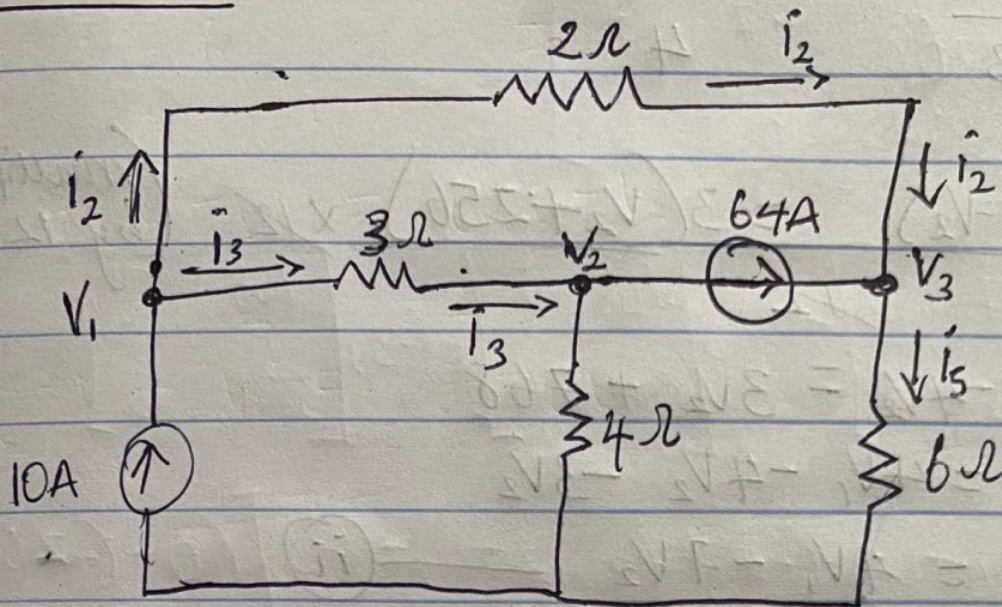

Soln

Applying KCL at node 1

$$i_1 = i_2 + i_3$$

$$10A = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$10 = \frac{3(V_1 - V_3) + 2(V_1 - V_2)}{6}$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (i)}$$

Applying KCL at node 2

$$i_3 = i_4 + 64A$$

$$\frac{V_1 - V_2}{3} = \frac{V_2}{4} + \frac{64}{1}$$

$$\frac{V_1 - V_2}{3} = \frac{V_2 - 256}{4}$$

$$\frac{4(V_1 - V_2)}{12} = \frac{3(V_2 + 256)}{12} \quad \text{(multiplying through by 12)}$$

$$4V_1 - 4V_2 = 3V_2 + 768$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (ii)}$$

Applying KCL at node (3)

$$64 + i_2 = i_5$$

$$\frac{64}{1} + \frac{V_1 - V_3}{2} = \frac{V_3}{6}$$

$$\frac{128 + V_1 - V_3}{2} = \frac{V_3}{6}$$

$$\frac{3(128 + V_1 - V_3)}{6} = \frac{V_3}{6} \quad \times 6$$

$$384 + 3V_1 - 3V_3 = V_3$$

$$384 = V_3 + 3V_3 - 3V_1$$

$$384 = 4V_3 - 3V_1 \quad \text{--- (iii)}$$

recalling:

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (i)}$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (ii)}$$

$$384 = -3V_1 + 4V_3 \quad \text{--- (iii)}$$

Expressing the above in matrix form

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$\text{recall: } V_1 = \frac{\Delta_1}{\Delta}; \quad V_2 = \frac{\Delta_2}{\Delta}; \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$\Delta = 5(-28 - 0) - (-2)(16 - 0) + (-3)(0 - 21)$$

$$\Delta = -140 + 32 + 63$$

$$\Delta = -45$$

$$\Delta_1 = \begin{bmatrix} + & - & + \\ 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{bmatrix}$$

$$\Delta_1 = 60 \begin{bmatrix} -7 & 0 \\ 0 & 4 \end{bmatrix} - (-2) \begin{bmatrix} 768 & 0 \\ 384 & 4 \end{bmatrix} + (-3) \begin{bmatrix} 768 & -7 \\ 384 & 0 \end{bmatrix}$$

$$\Delta_1 = 60(-28 - 0) - (-2)(3072 - 0) + (-3)(0 - (-2688))$$

$$\Delta_1 = -1680 + 6144 - 8064$$

$$\Delta_1 = -3600$$

$$\text{Hence; } V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80 \text{ Volts}$$

Recalling eqn (iii), substitute $V_1 = 80$ volts into eqn (iii)

$$384 = -3(80) + 4V_3$$

$$384 = -240 + 4V_3$$

$$384 + 240 = 4V_3$$

$$624 = 4V_3$$

$$V_3 = \underline{\underline{156 \text{ Volts}}}$$

Substituting the values of V_1 & V_3 into Eqn (i)

$$60 = (80)5 - 2(V_2) - 3(156)$$

$$60 = 400 - 2V_2 - 468$$

$$60 - 400 + 468 = -2V_2$$

$$\frac{128}{-2} = \frac{-2V_2}{-2}$$

$$V_2 = \underline{\underline{-64 \text{ Volts}}}$$