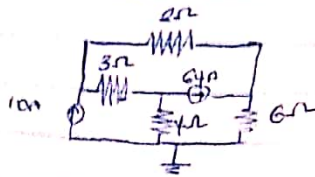


ARON TECHNICAL
 12/ENGG04/012
 ELECTRICAL / ELECTRONICS ENGINEERING
 EEE 824 Assignment

1) Find the Voltages at nodes 1, 2 and 3 in the circuit below



At node 1, KCL

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \dots (1)$$

at node 2, KCL:

$$i_2 = i_3 + 6$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \quad \dots (2)$$

at node 3, KCL:

$$64 + i_1 = i_3$$

$$64 = i_3 - i_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \quad \dots (3)$$

Using Cramer's Rule

$$\begin{aligned} 5V_1 - 2V_2 - 3V_3 &= 60 \quad \text{(i)} \\ 4V_1 - 7V_2 &= 768 \quad \text{(ii)} \\ -3V_1 + 4V_3 &= 384 \quad \text{(iii)} \end{aligned}$$

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\begin{aligned} \text{where } \Delta &= \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix} \\ &= 5(-28-0) + 12(16+0) - 3(0-21) \\ &= 140 + 32 + 63 \\ &= -45 \end{aligned}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix} = 60(-28-0) - 768(-8-0) - 384(0-21) = -1680 + 6144 - 8064 = -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$


$$\begin{aligned} \text{For } \Delta_2 &= \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix} = 5(768 \times 4 - 0) - 4(60 \times 4) \\ &\quad - (384 \times 3) - 3(0 - (768 \times 3)) \\ &= 2880 \end{aligned}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$\begin{aligned} \text{For } V_3, \Delta_3 &= \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ 3 & 0 & 384 \end{vmatrix} \\ &= 5((-4 \times 384) - 0) - 4(-2 \times 384 - 0) - 3(-2 \times 768) - (-4 \times 60) \\ &= -7020 \end{aligned}$$

$$V_0 = \frac{\Delta u}{\Delta} = \frac{-7020}{-45} = 156 \text{ V}$$

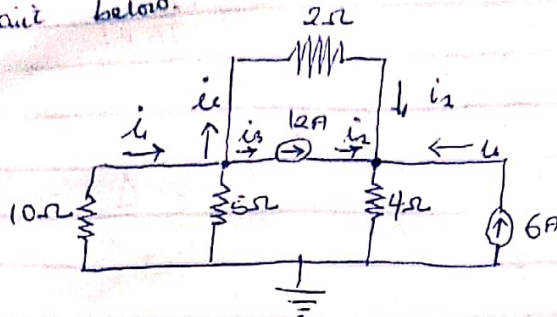e) Find the Voltages at node 1 and 2 and determine the currents flowing through the four resistors in the circuit below.



At node 1, KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_2}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 20V_1$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 20V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

At node 2

$$i_3 + i_5 + i_6 = 12$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2$$

Using Elimination method

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)} \times -4$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii)} \times -8$$

$$480 = 52V_1 - 20V_2 \quad \text{--- (iii)}$$

$$-1152 = 32V_1 - 48V_2 \quad \text{--- (iv)}$$

Subtract eqn (iii) from (iv)

$$V_2 = \frac{-672}{-2} = 336$$

$$V_2 = 24 \text{ V}$$

$$\text{subs } V_2 = 24 \text{ in eqn (1)}$$


$$V_1 = \frac{144 - 6V_2}{-4}$$

$$V_1 = 0$$

$$V_1 = 0 \text{ V}, \quad V_2 = 24 \text{ V}$$

$$i_1 = 0 \text{ A}, \quad i_2 = 0 \text{ A}, \quad i_3 = 0 \text{ A}, \quad i_4 = -12 \text{ A}$$

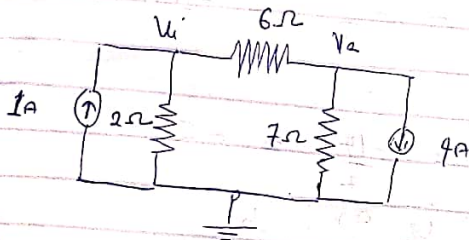iii) Obtain V_1 and V_2 and the currents through the resistors the circuit in example (ii) if the 2A source was replaced by a 1A current source.



At node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \dots (1)$$

At node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \dots (2)$$

from eqn (1), $V_2 = 4V_1 - 6$

$$\text{Subs } V_0 = 4V_1 - 6 \text{ in eqn (2)}$$

$$10x = 7V_1 - 13(4V_1 - 6)$$

$$10x = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = 90 / -45$$

$$V_1 = -2V$$

$$\text{Subs } V_1 = -2 \text{ in eqn (1)}$$

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$V_1 = -2V, \quad V_2 = -14V$$

Current through the resistors

$$I_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = 2A$$

$$I_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
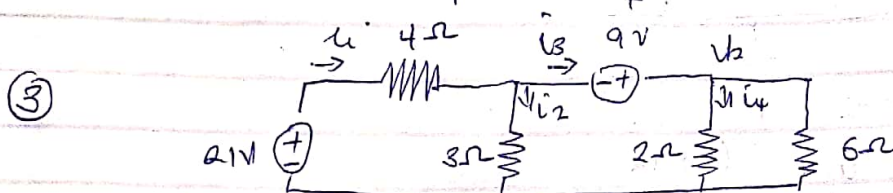
$$I_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the 3Ω and 2Ω resistors

Using KCL at node 1

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1 - 2}{4} + \frac{V_1}{3} + \frac{V_2}{2} + \frac{V_3}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (i)}$$

Using KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (i)}$$


$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

Let $V_2 = 9 + V_1$
 Sub $V_2 = 9 + V_1$ in eqn (1)
 $7V_1 + 8(9 + V_1) = 63$
 $7V_1 + 72 + 8V_1 = 63$
 $15V_1 = -9$

Sub $V_1 = 0.6$
 $V_2 = 9 + 0.6 = 9.6$
 $-(-0.6) + V_2 = 9$
 $0.6 + V_2 = 9$

$V_1 = -0.6$ V and $V_2 = 8.4$ V

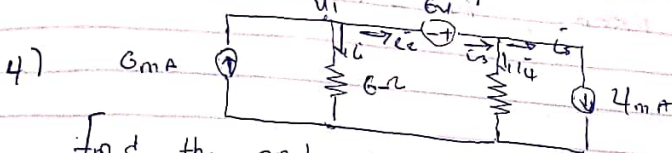Current through the 2Ω resistor
 $I = \frac{V_2}{4} = \frac{8.4}{4} = 2.1$ A



Find the node voltage and the current through the 6Ω and 12Ω resistor

Let Assume that $V_1 - V_2 = 6V \Rightarrow I_1$

At node 1, using KCL

$$6mA = I_1 + I_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \text{--- (1)}$$

At node 2

$$I_2 = I_3 + I_4$$

$$V_1 - V_2 = 4mA + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \text{--- (2)}$$

Solving V_1 and V_2 Simultaneously by using
 $V_1 = 9.5 \text{ V}$ and $V_2 = 5.1 \text{ V}$

Current through the 6Ω resistor
 $i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58 \text{ A}$, $i_2 = V_1 - V_2$
 $= 9.5 - 5.1 = 4.4 \text{ A}$

Current through the 12Ω resistor
 $i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43 \text{ A}$

$V_1 = 9.5 \text{ V}$, $V_2 = 5.1 \text{ V}$
 $i_1 = 1.58 \text{ A}$, $i_4 = 0.43 \text{ A}$