



Q. For node 1

$$i_1 = i_2 + i_3 + i_4$$

$$12A = \frac{v_1 - 0}{5} + \frac{v_1 - 0}{10} + \frac{v_1 - v_2}{2}$$

$$120A = 2v_1 + v_1 + 5(v_1 - v_2)$$

$$120 = 8v_1 - 5v_2 \quad \dots \text{--- (1)}$$

For node 2

$$i_1 = i_3 + i_4$$

$$12A = \frac{v_2 - 0}{4} + (-6A) + \frac{v_2 - v_1}{2}$$

$$18A = \frac{v_2}{4} + \frac{v_2 - v_1}{2}$$

$$72 = V_2 + 2V_2 - 2V_1$$

$$72 = 3V_2 - 2V_1 \quad \text{--- (ii)}$$

$$72 = 3V_2 - 2V_1 \quad \text{--- (i)}$$

$$120 = -5V_2 + 8V_1$$

$$V_1 = \frac{360}{7} = 51.43 \text{ V}$$

$$V_2 = \frac{408}{7} = 58.29 \text{ V}$$

∴ For Node 1

$$i_1 = 12 \text{ A} \quad i_2 = \frac{51.43}{5} = 10.29 \text{ A}$$

$$i_3 = \frac{51.43}{10} = 5.143 \text{ A}$$

$$i_4 = \frac{51.43 - 58.29}{2}$$

$$= \frac{-6.86}{2} = -3.43 \text{ A}$$

For Node 2

$$i_1 = 12 \text{ A}$$

$$i_2 = \frac{5V_2}{4} = 14.57 \text{ A}$$

$$i_3 = -6 \text{ A}$$

$$i_4 = \frac{V_2 - V_1}{2}$$

$$= \underline{3.43 \text{ A}}$$

Q2 For Node 1

$$i_1 = i_2 + i_3 + i_4$$

$$1 \text{ A} = \frac{V_1}{5} + \frac{V_1}{10} + \frac{V_1 - V_2}{2}$$

$$10 \text{ A} = 2V_1 + V_1 + 5V_1 - 5V_2$$

$$10 \text{ A} = 8V_1 - 5V_2$$

①

For Node 2

$$i_2 = i_3 + i_4$$

$$1 \text{ A} = \frac{V_2}{4} - 6 \text{ A} + \frac{V_2 - V_1}{2}$$

Source to nodes

$$V_1 = 12.14 \text{ V}$$

$$V_2 = 17.43 \text{ V}$$

For Node 1

$$i_1 = 1 \text{ A} \quad i_2 = \frac{12.14}{5} = 2.43 \text{ A}$$

$$i_3 = \frac{12.14}{10} = 1.21 \text{ A}$$

$$i_4 = \frac{12.14 - 17.43}{2} = \frac{-5.29}{2} = -2.65 \text{ A}$$

For Node 2

$$i_1 = 1 \text{ A}, \quad i_2 = \frac{17.43}{4} = 4.36 \text{ A}$$

$$i_3 = -1 \text{ A}$$

$$i_4 = \frac{V_2 - V_1}{2} = \frac{5.29}{2} = 2.65 \text{ A}$$