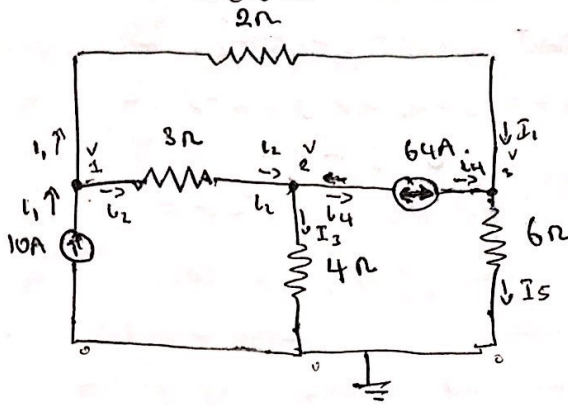


Obot Mkpouts Obot
 17/12/2024/046
 Elect / Elect
 Circuit theory assignment

1) Find the voltages at node 1, 2 and 3 in
 The circuit below



At node 1 using kcl

$$10A = i_1 + i_2$$

$$10A = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

multiply by 6

$$60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (1)}$$

At Node 2, using kcl

$$i_2 = i_3 + i_4$$

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

multiply by 12

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2 + 0$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (2)}$$

At Node 3 kcl

$$64 = -I_1 + I_5$$

$$64 = I_5 - I_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

Multiply 6

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = V_3 - 3V_1 + 3V_3$$

$$384 = -3V_1 + 4V_3 \quad \text{--- (3)}$$

Using Cramer's rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$4V_1 - 7V_2 = 768 \quad \text{--- (2)}$$

$$-3V_1 + 0 + 4V_3 = 384 \quad \text{--- (3)}$$

matrix :

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

where

Where Δ

$$\begin{vmatrix} 8 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 8((-7 \times 4) - (0)) - (2)((4 \times 4) - (0 \times -3)) - 3((4 \times 0) - (-7 \times -3)) \\ &= 8(-28) + 2(16) - 3(-21) \\ &= -140 + 32 + 63 \\ &= -45 \end{aligned}$$

Δ_1

$$\begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 60((-7 \times 4) - (0)) - (-2)(768 \times 4) - (384 \times 0) \\ &= 60((-28) - 0) + 768(-8) - 384(0) \\ &= 60(-28) - 768(-8) + 384(0) \\ &= 60(-28) + 6144 - 0 \\ &= -1680 + 6144 - 0 \\ &= 4464 \end{aligned}$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

Δ_2

$$\begin{vmatrix} 8 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 8(60 \times 4 - (-3 \times 0)) - 60(4 \times 4 - (-3 \times -3)) + 384(4 \times 0 - (-3 \times -3))$$

Since $V_1 = 80V$

value we have: from eq (1) and (2)

$$-5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$-3V_1 + 4V_3 = 384 \quad \text{--- (2)}$$

replacing V_1 with 80

$$-5(80) - 2V_2 - 3V_3 = 60 \quad \text{--- (1')}$$

$$-3(80) + 4V_3 = 384 \quad \text{--- (2')}$$

$$-400 - 2V_2 - 3V_3 = 60 \quad \text{--- (1'')}$$

$$-240 + 4V_3 = 384 \quad \text{--- (2'')}$$

$$2V_2 - 3V_3 = -340 \quad \text{--- (3)}$$

$$4V_3 = 624 \quad \text{--- (4)}$$

using (4) to find for V_3

$$V_3 = \frac{624}{4}$$

$$V_3 = 156V //$$

putting V_3 in (3)

$$-2V_2 - 3(156) = -340$$

$$-2V_2 - 468 = -340$$

$$-2V_2 = 128$$

$$-V_2 = 64$$

$$V_2 = -64V //$$


$$V_2 = -64V //$$

Voltages are


$$V_1 = 80V //$$

$$V_2 = -64V //$$

$$V_3 = 156V //$$

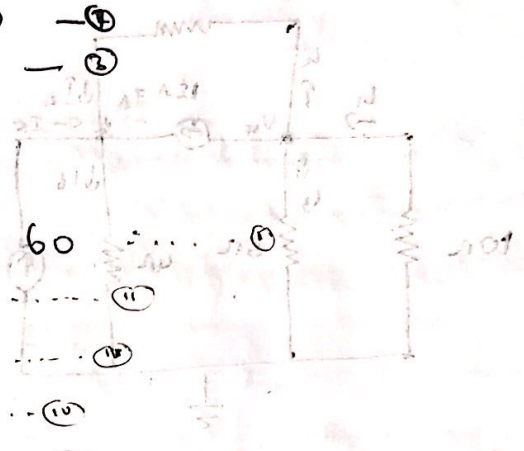

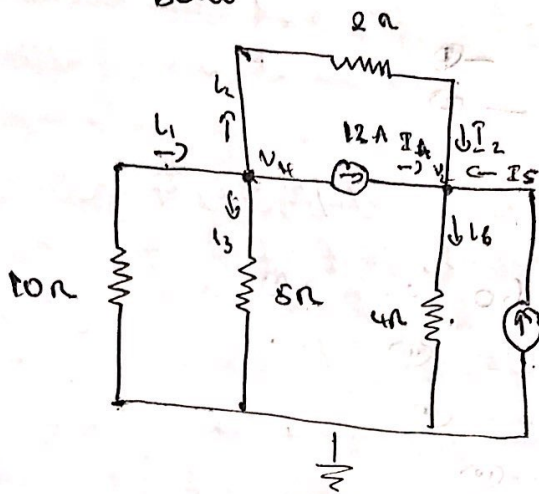2). Find the voltages at node 1 and 2 and determine the currents flowing through the four resistors in circuit below



At Node 1 with KCL

$$I_1 = I_2 + I_3 + I_4$$

$$I_1 = \frac{V_1 - V_2}{2}$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + \frac{V_1 - V_0}{5} + 12A$$

Multiply through by 10

$$V_0 - V_1 = 5(V_1 - V_2) + 2(V_1 - V_0) + 120$$

$$V_0 - V_1 = 5V_1 - 5V_2 + 2V_1 - 2V_0 + 120$$

$$0 = 6V_1 - 5V_2 + 2V_1 + 120$$

$$0 = 8V_1 - 5V_2 + 120$$

$$-8V_1 + 5V_2 = 120 \quad \text{--- (1)}$$

At Node 2

$$I_A = -I_2 - I_S + I_6$$

$$I_6 = I_4 + I_2 + I_5$$

$$\frac{V_2 - V_0}{4} = 12 + \frac{V_1 - V_2}{2} + 6V$$

multiply by 4


$$V_2 - V_0 = 48 + 2(V_1 - V_2) + 24$$

$$V_2 = 48 + 2V_1 - 2V_2 + 24$$

$$V_2 = 72 + 2V_1 - 2V_2$$

$$0 = 72 + 2V_1 - 3V_2$$

$$-2V_1 + 3V_2 = 72$$

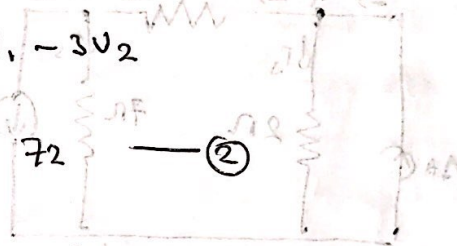

Using elimination method

$$-8V_1 + 5V_2 = 120 \quad \text{--- (1)}$$

$$-2V_1 + 3V_2 = 72 \quad \text{--- (2)}$$

$$+32V_1 - 20V_2 = -480 \quad \text{--- (1)}$$

$$+10V_1 - 24V_2 = -576 \quad \text{--- (2)}$$

$$+2V_1 + 4V_2 = 96$$

$$+16V_1 + 10V_2 = -240$$

$$+16V_1 - 24V_2 = -576$$

$$0 + 14V_2 = 336$$

$$V_2 = 24V$$

Sub 24V in equation (1)

$$-8V_1 + 5(24) = 120$$


$$-8V_1 + 120 = 120$$

$$-8V_1 = 0$$

$$V_1 = 0V, V_2 = 24V$$

$$I_1 = 0A, I_2 = 0A, I_3 = 6A, I_4 = 12A$$

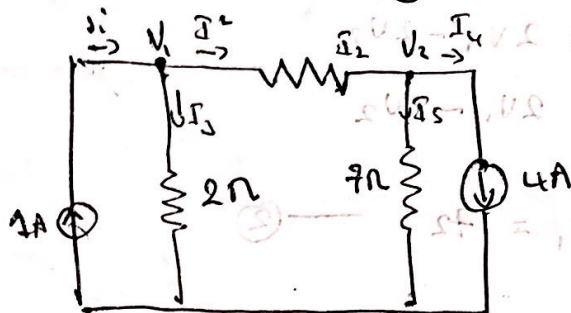III) Obtain V_1 and V_2 (and) the currents through the resistors for the circuit in example (iv) if the 2A current source was replaced by 4A current source



At Node 1

$$I_1 = I_2 + I_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (1)}$$

At Node 2

$$I_2 = I_3 + I_4$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (2)}$$

from eq (1) $V_2 = 4V_1 - 6$

Subs $V_2 = 4V_1 - 6$ in eqn ①

$$168 = 7V_1 - 15(4V_1 - 6)$$

$$168 = 7V_1 - 60V_1 + 90$$

$$90 = -45V_1$$

$$V_1 = 90 / -45$$

$$V_1 = -2V$$

Subs $V_1 = -2$ in eqn ①

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$


$$V_2 = -14V$$

Current through the resistors

$$I_1 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$I_2 = \frac{V_1}{3} = \frac{-2}{3} = -\frac{2}{3}A$$
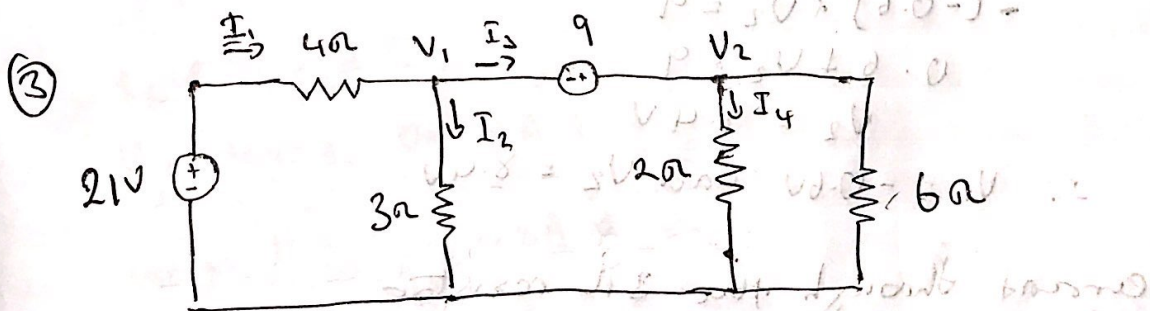
$$I_3 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the 3Ω and 2Ω resistor

Using KCL at Node 1

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1 = 24}{4} + \frac{V_1}{5} + \frac{V_2}{6} \left(1 + \frac{V_2}{2}\right) = 10 + 24 = 34$$

$$7V_1 + 8V_2 - 63 = 0 \dots (i)$$

Apply KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \dots (ii)$$

$$7V_1 + 8V_2 = 63 \dots (i)$$

$$V_1 + V_2 = 9 \dots (ii)$$

but $V_2 = 9 + V_1$

Sub $V_2 = 9 + V_1$ in eqn (i)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

Sub $V_1 = -0.6$ in eqn (ii)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = 8.4V$$


$\therefore V_1 = -0.6V$ and $V_2 = 8.4V$

Current through the 3Ω resistor

$$I_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the 2Ω resistor
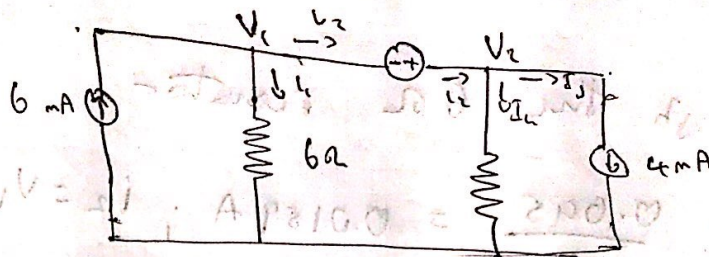
$$I_1 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1A$$



Find the node voltage and the currents through the 6 ohm and 12 ohm resistors.

Let assume that $V_1 - V_2 = 6V \Rightarrow I_2$

At node 1 using KCL

$$6mA = 0.06A$$

$$0.06A = I_1 + I_2$$

$$0.06A = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$0.36 = V_1 + 6(V_1 - V_2)$$

$$0.36 = V_1 + 6V_1 - 6V_2$$

$$0.36 = 7V_1 - 6V_2 \quad \text{--- (i)}$$

At node 2

$$I_2 = I_3 + I_4$$

$$V_1 - V_2 = 0.04A + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 0.48A + V_2$$

$$0.48A = 12V_1 - 12V_2 - V_2$$

$$0.48A = 12V_1 - 13V_2 \quad \text{--- (ii)}$$

Solving V_1 and V_2 simultaneously, we get:

$$V_1 = 0.05V \quad V_2 = 0.095V$$

Current through the 6Ω resistor

$$I_1 = \frac{V_1}{6} = \frac{0.095}{6} = 0.0159 \text{ A}; \quad i_2 = V_1 - V_2$$

~~9.5 - 5.1 = 4.4A~~ 0.095 - 0.051V = 0.044A

Current through the 12Ω resistor

$$I_2 = \frac{V_2}{12} = \frac{0.051}{12} = 0.00425 \text{ A}$$

$V_1 = 0.095$ $V_2 = 0.051 \text{ V}$

$I_4 = 0.00425$ $I_1 = 0.0159 \text{ A}$

$(2V - 1V) + \frac{0 - V}{2} = 100.0$
 $(2V - 1V) + 1V = 20.0$
 $500 - 100 + 100 = 20.0$
 $500 - 100 = 20.0$

$\frac{0 - 5V}{5} + 100.0 = 5V - 1V$
 $500 + 100.0 = (5V - 1V) \cdot 11$

$500 - 500 - 100 = 100.0$
 $(ii) \quad 500 - 500 - 100 = 100.0$