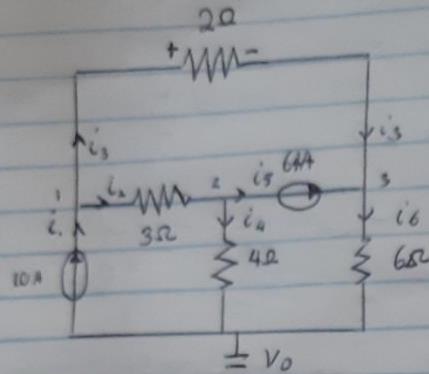


BRIGGS FRANCO SOIBI

17/ENGO41015

ELECT/ELECT



$$i_1 = i_2 + i_3 \text{ (I)}; \quad i_2 = i_5 + i_4 \text{ (II)}; \quad i_5 + i_6 = i_6 \text{ (III)}$$

$$i_1 = 10A \quad i_6 = 64A \quad V_0 = 0$$

from I

$$10 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{2} \quad \text{--- IV}$$

from II

$$\frac{V_1 - V_2}{3} = 64 + \frac{V_2 - V_0}{4} \quad \text{--- V}$$

from III

$$\frac{V_3 - V_0}{6} = 64 + \frac{V_1 - V_3}{2} \quad \text{--- VI}$$

hence equations become

$$10 = \frac{5}{6}V_1 - \frac{1}{3}V_2 - \frac{1}{2}V_3 \quad \text{from IV}$$

$$64 = \frac{1}{3}V_1 - \frac{7}{12}V_2 + 0V_3 \quad \text{from V}$$

$$64 = -\frac{1}{2}V_1 + 0V_2 + \frac{2}{3}V_3 \quad \text{from VI}$$

in matrix form

$$\begin{bmatrix} 10 \\ 64 \\ 64 \end{bmatrix} = \begin{bmatrix} \frac{5}{6} & -\frac{1}{3} & -\frac{1}{2} \\ \frac{1}{3} & -\frac{7}{12} & 0 \\ -\frac{1}{2} & 0 & \frac{2}{3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$b = AX$$

$$X = A^{-1}b$$


$$X = A^{-1} b = \begin{bmatrix} 3.73 & -2.13 & 2.8 \\ 2.13 & -2.93 & 1.6 \\ 2.8 & -1.6 & 3.6 \end{bmatrix} \begin{bmatrix} 10 \\ 64 \\ 64 \end{bmatrix}$$

$$X = \begin{bmatrix} 80 \\ -64 \\ 156 \end{bmatrix}$$

$$V_1 = 80$$

$$V_2 = -64$$

$$V_3 = 156$$

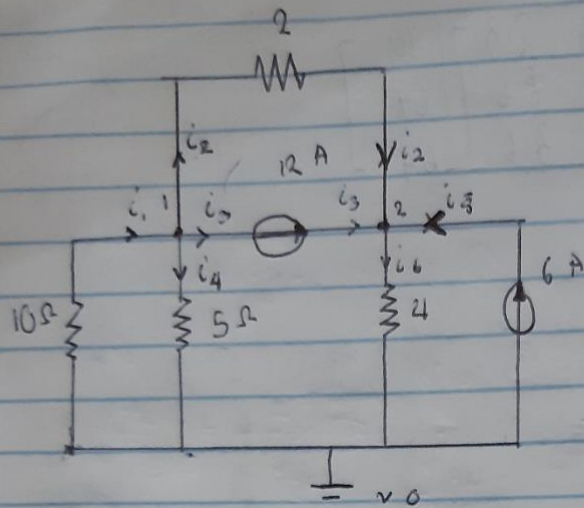

$$i_1 = i_2 + i_3 + i_4$$

$$i_3 = 12$$

$$i_3 + i_5 = -i_5 + i_6$$

$$i_5 = 6A$$

$$V_0 = 0$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_0}{5} \quad - (i)$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - V_0}{4} \quad - (ii)$$

from (i)

$$12 = \frac{-V_1}{10} - \frac{V_1}{2} + \frac{V_2}{2} - \frac{V_1}{5} \Rightarrow \left[\frac{-1}{10} - \frac{1}{2} \right] V_1 + \left[\frac{1}{2} - \frac{1}{5} \right] V_2 =$$

from (ii)

$$-0.6V_1 + 0.3V_2 =$$

$$18 = \frac{V_2}{2} + \frac{V_2}{2} - \frac{V_1}{5}$$

$$V_2 = \frac{12 + 0.6V_1}{0.3}$$

$$\cancel{V_2 = 18V}$$

$$12 = \begin{bmatrix} -1 & -1 & -1 \\ 10 & 2 & 5 \end{bmatrix} V_1 + \frac{1}{2} V_2$$

$$12 = -0.8V_1 + 0.5V_2 \quad \text{--- (ii)}$$

from (i)

$$18 = \frac{V_2}{4} + \frac{V_2}{2} - \frac{V_1}{2}$$

$$18 = 0.75V_2 - 0.5V_1 \quad \text{--- (iv)}$$

$$0.75V_2 = 18 + 0.5V_1 \Rightarrow V_2 = \frac{18 + 0.5V_1}{0.75}$$

$$12 = -0.8V_1 + \frac{0.5(18 + 0.5V_1)}{0.75}$$


$$\cancel{12} = -0.8V_1 \quad \cancel{12} + 0.3V_1$$

$$0 = -0.8V_1 + 0.3V_1$$

$$V_1 = 0V$$

hence

$$V_2 = \frac{18}{0.75} = 24V$$

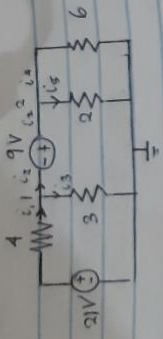

3)

node 1 $-i_1 = i_2 + i_3 + i_4$
 $V_1 - 2 + V_2 + V_3 + V_4 = 0$
 $\frac{V_1 - 2}{3} + \frac{V_2}{2} + \frac{V_3}{6} = 0$ — (1)

using KVL for Loop 1
 $-V_1 - 9 + V_2 = 0$
 $-V_1 + V_2 = 9$ — (2)

$V_2 = 9 + V_1$

$7V_1 + 8(9 + V_1) = 63$


$7V_1 + 72 + 8V_1 = 63$
 $15V_1 = -9$

$V_1 = -0.6V$

hence $V_2 = 8.4V$

$i_3 = \frac{V_1}{3} = \frac{-0.6V}{3} = -0.2A$

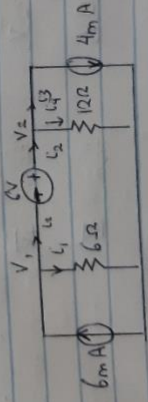$i = \frac{V_2}{4} = \frac{8.4}{4} = 2.1A$



4)

$V_1 - V_2 = 6V \Rightarrow V_2$

at node 1: using KCL

$6 \times 10^{-3} = i_1 + i_2$

$6 \times 10^{-3} = \frac{V_1}{6} + V_1 - V_2$

$36 \times 10^{-3} = V_1 + 6V_1 - 6V_2$

$36 \times 10^{-3} = 7V_1 - 6V_2$ — (1)

at node 2

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4 \times 10^{-3} + \frac{V_2}{12}$$

$$12V_1 - 12V_2 = 4 \times 10^{-3} + V_2$$

$$48 \times 10^{-3} = 12V_1 - 12V_2 - V_2$$

$$48 \times 10^{-3} = 12V_1 - 13V_2 \quad \dots \dots (1)$$

$$V_1 = 9.5V \quad \text{and} \quad V_2 = 51V$$

$$i_3 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

$$i_4 = \frac{V_2 - V_1}{12} = \frac{51 - 9.5}{12} = 4.4A$$

$$i_4 = \frac{V_2}{12} = \frac{51}{12} = 0.43A$$

$$V_1 = 9.5V \quad ; \quad V_2 = 51V$$

$$i_3 = 1.58A \quad ; \quad i_4 = 0.43A$$