
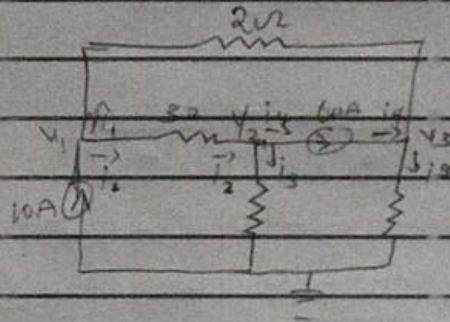

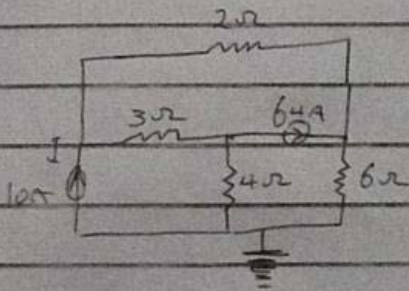
## Circuit Theory Answers

① Find the Voltages at nodes 1, 2, and 3 in the circuit below.



~~At~~ Node 1 KCL

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3}$$

Multiply through by 6

$$60 = 3[V_1 - V_2] + 2[V_1 - V_2]$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_2$$

~~$$60 = 5V_1 - 5V_2$$~~

$$60 = 5V_1 - 3V_2 - 2V_2 = 0$$

At Node 2 KCL

$$i_2 = i_3 + 6A$$

$$6A = i_2 - i_3$$

$$6 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

Multiply through by 7

$$768 = 4(2V_1 - V_2) - 3(2V_2 - 0)$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (2)}$$

Make 3 ucu

$$64 = i_5 = i_4$$

$$64 = i_5 = i_4$$

$$64 = \frac{V_3 - 0}{6} = \frac{V_1 - V_2}{2}$$

$$384 = V_3 - 3(V_1 - V_2)$$

$$384 = -3V_1 + 4V_3 \quad \text{--- (3)}$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$4V_1 - 7V_2 + 0V_3 = 768 \quad \text{--- (2)}$$

$$-3V_1 + 0V_2 + 4V_3 = 384 \quad \text{--- (3)}$$

Matrix Rep.

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5[-28-0] + 2[16+0] - 3[0-21]$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60[-28-0] - 768[-8-0] - 384[0-21]$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$V_2 = \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5[768 \times 4] - 0 - 4[384 \times 4] - [384 \times 5] - 3[0 - 1768 - 3]$$

$$= 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$


$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{45}$$

$$V_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5[-7 \times 384 - 0] - 4[-2 \times 384 - 0] - 3[-2 \times 768] - [-7 \times 60] \\ = -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{45} = 156V$$
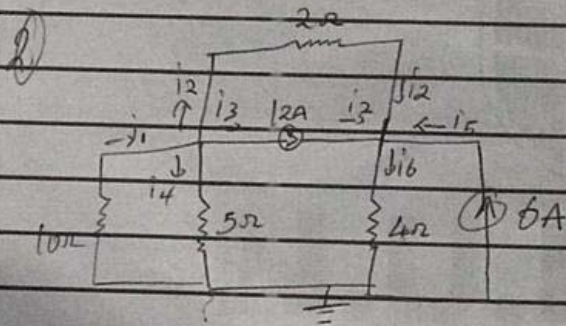
$$\therefore V_1 = 80V \quad V_2 = -64V \quad V_3 = 156V$$



Nodal KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_2 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_2}{5}$$

$$0 - V_1 = 5[V_1 - V_2] + 120 + 2[V_1 - V_2]$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (1)}$$

Node a.

$$I_3 + I_2 + i_5 = 16$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2}{4} = 0$$

$$96 + 4[V_1 - V_2] + 48 = 2[V_2]$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (2)}$$

Using Elimination method

$$120 = -8V_1 + 5V_2 \quad \text{--- (1)} \quad \times 4$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (2)} \quad \times 8$$

$$-480 = 32V_1 - 20V_2 \quad \text{--- (3)}$$

$$-1152 = 32V_1 - 48V_2 \quad \text{--- (4)}$$

Subtract eqn 3 from 4

$$-672 = 0 - 28V_2$$

$$-672 = -28V_2$$

$$V_2 = \frac{+672}{+28}$$

$$V_2 = 24V$$

Sub  $V_2$  into eqn (1)

$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6[24]}{-4}$$

$$V_1 = \frac{144 - 144}{-4} \quad V_1 = 0V$$


$$V_1 = 0V \quad V_2 = 24V$$

$$i_1 = 0A, \quad i_2 = 0A, \quad i_3 = 6A, \quad i_4 = -12A$$

② Obtain  $V_1$  and  $V_2$  and the currents through the resistors

Classmate

②

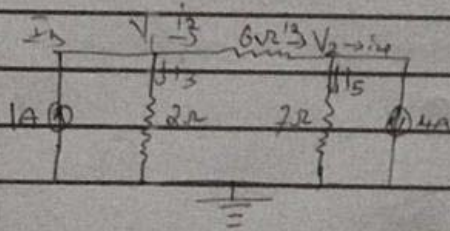

Node 1

$$\sum I = i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (1)}$$

Node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7[V_1 - V_2] = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (2)}$$

From equation (1)

$$V_2 = 4V_1 - 6$$

Sub  $V_2 = 4V_1 - 6$  into eqn (2)

$$168 = 7V_1 - 13[4V_1 - 6]$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = 90 / -45$$

$$V_1 = -2V$$

Subs  $V_1 = -2$  into eqn 1

$$6 = 4[-2] - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$V_1 = -2V, V_2 = -14V$$

Currents through the resistors:

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
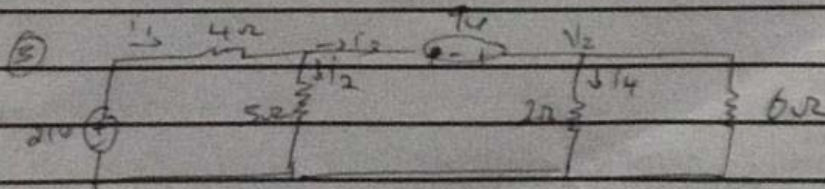
$$i_4 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the ~~the~~ Current through the ~~the~~ 2-ohm resistor

Using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (i)}$$

Using KVL for LOOP 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (i)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$\begin{array}{r} 7V_1 + 8V_2 = 63 \\ + \quad -7V_1 + 7V_2 = 63 \\ \hline 15V_2 = 126 \end{array}$$

From eqn 2:  $-V_1 + V_2 = 9$

$$V_2 = 9 + V_1 \quad \text{Put into eqn 1}$$

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = 63 - 72$$

$$15V_1 = -9$$

$$V_1 = -9/15$$

$$V_1 = -0.6V$$

Sub  $V_1 = -0.6V$  in eqn 1



$$-[-0.67 + V_2] = 9$$

$$0.6 + V_2 = 9$$


$$V_2 = 9 - 0.6 = 8.4 \text{ V}$$

$$V_1 = -0.6 \text{ V} \quad V_2 = 8.4 \text{ V}$$

Current through  $3\Omega$  and  $2\Omega$ .

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2 \text{ A} \quad \text{at } 3\Omega$$
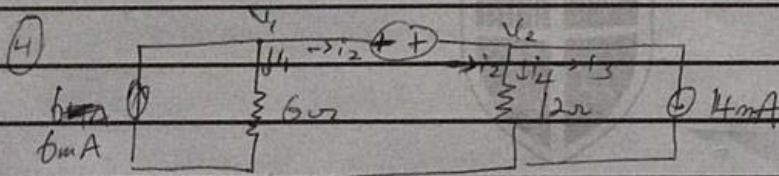
$$i_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1 \text{ A} \quad \text{at } 2\Omega$$



Find the nodes at the voltages and the currents through the  $6\Omega$  and  $12\Omega$  resistor.

$$\text{Take } V_1 - V_2 = 6 \text{ V} \Rightarrow i_2$$

At node 1, using KCL

$$6 \text{ mA} = i_1 + i_2$$

$$6 \text{ mA} = \frac{V_1 - 0}{6} + [V_1 - V_2]$$

$$36 = V_1 + 6[V_1 - V_2]$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \text{--- (1)}$$

At Node 2.

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4 \text{ mA} + \frac{V_2 - 0}{12}$$

$$12[V_1 - V_2] = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \text{--- (2)}$$

Solving  $V_1$  and  $V_2$  Simultaneously we have

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

Current through the  $6\Omega$  resistor:

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58 \text{ A}$$

$$i_2 = \frac{V_1 - V_2}{12} = \frac{9.5 - 5.1}{12} = 0.36 \text{ A}$$

Current through  $12\Omega$

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43 \text{ A}$$

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

$$i_1 = 1.58 \text{ A}$$

$$i_4 = 0.43 \text{ A}$$