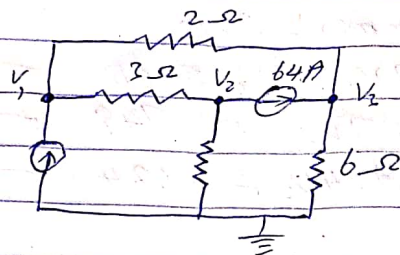


Elenwoke Chukwuebuka Joshua  
 17/ENG04/020  
 Electrical/Electronics

1.) Find the Voltages at nodes 1, 2 and 3 in the circuit below.



At node 1, KCL

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 + V_2}{2} + \frac{V_1 + V_3}{3}$$

$$60 = 3(V_1 - V_2) + 2(V_1 - V_3)$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_3$$

$$60 = 5V_1 - 3V_2 - 2V_3 \quad \text{--- (i)}$$

At node 2, KCL

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2 - 0$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (ii)}$$

At node 3, KCL

$$64 + i_3 = i_5$$

$$64 = i_5 - i_3$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_2 - 3(V_1 - V_2)$$

$$384 = -3V_1 + 4V_2 \quad \text{--- (iii)}$$

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (i)}$$

$$4V_1 - 7V_2 = 748 \quad \text{--- (ii)}$$

$$-3V_1 + 4V_2 = 384 \quad \text{--- (iii)}$$

In Matrix Representation

$$\begin{pmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 60 \\ 748 \\ 384 \end{pmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-28-0) + 2(16+0) - 3(0-21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 748 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28-0) - 768(-8-0) - 384(0)$$

$$= -1680 + 6144 - 8064$$

$$\Delta_1 = -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$



$$V_2 = \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(768 - 0) - 4(240 + 1152) - 3(0 + 2244)$$

$$= 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$V_3 = \Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$


$$= -5((-7 \times 384) - 0) - 4((-2 \times 384) - 0) - 3((-2 \times 768) - (-7 \times 60))$$

$$= -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$\therefore V_1 = 80V, V_2 = -64V, V_3 = 156V$$

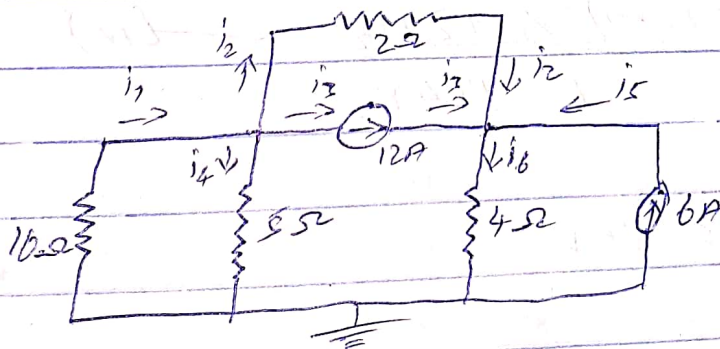2. Find the voltage at nodes 1 and 2 and determine the current flowing through the four resistances in the circuit below



At node 1, KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_1 - 0}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_2}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

At node 2, KCL

$$i_3 + i_2 + i_5 = i_6$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii)}$$

Using Elimination Method

$$120 = -8V_1 + 5V_2 \quad \times 2$$

$$144 = -4V_1 + 6V_2 \quad \times 4$$

$$240 = -16V_1 + 10V_2 \quad \text{--- (iii)}$$

$$576 = -16V_1 + 24V_2 \quad \text{--- (iv)}$$

$$816 \quad 0 \quad +14V_2$$

$$V_2 = 24V$$

Sub  $V_2$  in eqn (iii)

$$240 = -16V_1 + 240$$

$$V_1 = 0$$


$$\therefore V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A; i_2 = 0A; i_3 = 6A; i_4 = 12A$$

2ii. Obtain  $V_1$   
resistor  
2A cur  
2A.



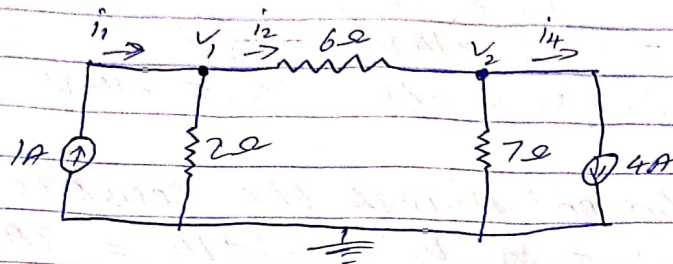2ii. Obtain  $V_1$  and  $V_2$  and the current through the resistors for the circuit in example (ii) at the 2A current source was replaced by a 1A current source.



Solution

At node 1, KCL

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = (V_1 - V_2) + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (i)}$$

At node 2, KCL

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (ii)}$$

From eqn (i),  $V_2 = 4V_1 - 6$

Sub  $V_2$  in eqn (ii)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$168 - 78 = 7V_1 - 52V_1$$

$$90 = -45V_1$$

$$V_1 = -2V_1$$

$$\text{Sub } V_1 = -2 \text{ into eqn (1)}$$

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$= -14V$$


$$\therefore V_1 = -2V, \quad V_2 = -14V$$

Current through the resistors

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{V_1}{3} = \frac{-2}{3} = -1A$$
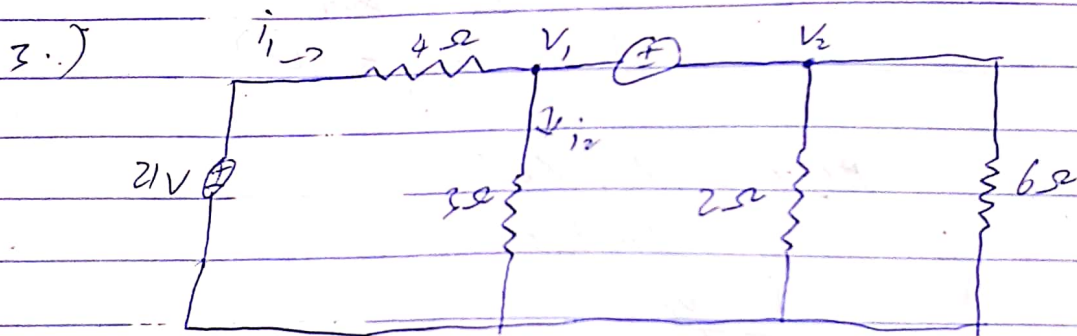
$$i_4 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the  $3\Omega$  and  $2\Omega$  resistors

Solution

Using KCL at node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (1)}$$



Using KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- } \times 1$$

$$-V_1 + V_2 = 9 \quad \text{--- } \times 7$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (iii)}$$

$$\underline{-7V_1 + 7V_2 = 63 \quad \text{--- (iv)}}$$

$$0 + 15V_2 = 126$$

$$V_2 = \frac{126}{15} = 8.4V$$

Sub  $V_2$  into eqn (iv)

$$-7V_1 + 7 \times (8.4) = 63$$

$$-7V_1 = 63 - 58.8$$

$$-7V_1 = 4.2$$

$$V_1 = -0.6V$$


Current through the  $2\Omega$  resistor

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the  $2\Omega$  resistor

$$i_4 = \frac{V_2}{4} = \frac{8.4}{4} = 4.2A$$

4.)

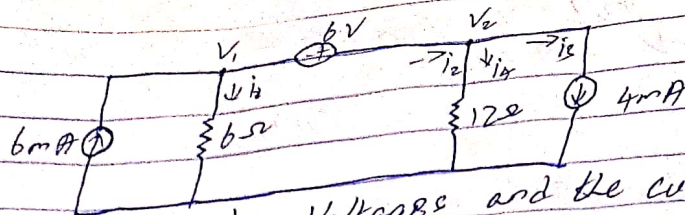

Find the node voltages and the current through the  $6\Omega$  and  $12\Omega$  resistor

solution

$$\text{let say } V_1 - V_2 = 6V \rightarrow i_2$$

At node 1, using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1}{6} + (V_1 - V_2)$$

$$0.036 = V_1 + 6(V_1 - V_2)$$

$$0.036 = V_1 + 6V_1 - 6V_2$$

$$0.036 = 7V_1 - 6V_2 \quad \text{--- (i)}$$

At node 2

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4mA + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 0.048 + V_2$$

$$0.048 = 12V_1 - 12V_2 - V_2$$

$$0.048 = 12V_1 - 13V_2 \quad \text{--- (ii)}$$

$$7V_1 - 6V_2 = 0.036 \times 12$$

$$12V_1 - 13V_2 = 0.048 \times 7$$

$$84V_1 - 72V_2 = 0.432 \quad \text{--- (iii)}$$

$$84V_1 - 91V_2 = 0.336 \quad \text{--- (iv)}$$

$$0 + 19V_2 = 0.096$$



$$V_2 = 5.053 \times 10^{-3} \text{ V}$$

sub  $V_2$  in eqn (IV)

$$84V_1 - 0.4598 = 0.336$$

$$84V_1 = 0.336 + 0.4598$$

$$V_1 = \frac{0.7958}{84} = 9.474 \times 10^{-3} \text{ V}$$

$\therefore$  Current through the  $6 \Omega$  resistor

$$i_1 = \frac{V_1}{6} = \frac{9.474 \times 10^{-3}}{6} = 1.579 \times 10^{-3} \text{ A}$$

Current through the  $12 \Omega$  resistor

$$i_4 = \frac{V_2}{12} = \frac{5.053 \times 10^{-3}}{12} = 4.212 \times 10^{-4} \text{ A}$$

$$V_1 = 9.474 \times 10^{-3} \text{ V}$$

$$V_2 = 5.053 \times 10^{-3} \text{ V}$$

$$i_1 = 1.579 \times 10^{-3} \text{ A}$$

$$i_4 = 4.212 \times 10^{-4} \text{ A}$$