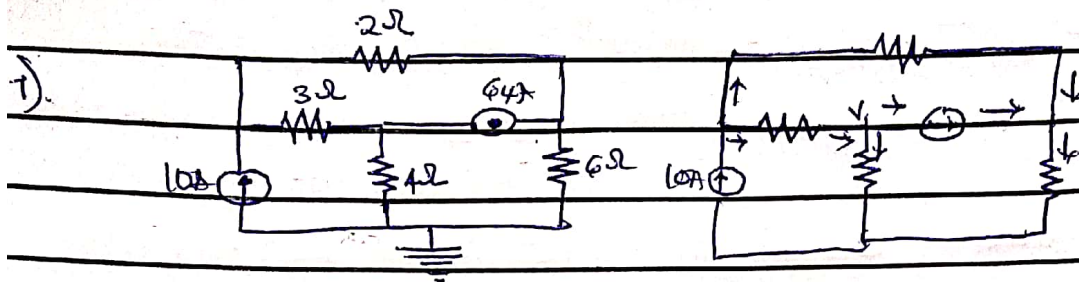


Michael Effiong Eke

ENGG04/079

ELE/ELE

EEE 322



At node 1, KCL

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3}$$

$$\Rightarrow 60 = 3(V_1 - V_2) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \dots \dots \textcircled{1}$$

At Node 2, KCL

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \dots \dots \textcircled{ii}$$

At Node 3, KCL

$$64 + i_4 = i_5$$

$$64 = i_5 - i_4$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_2}{2}$$

$$384 = V_3 - 3(V_1 - V_2)$$

$$384 = -3V_1 + 4V_2 \dots \dots \textcircled{iii}$$

Using Cramer's Rules

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (i)}$$

$$4V_1 - 7V_2 = 768 \quad \text{--- (ii)}$$

$$-3V_1 + 4V_3 = 384 \quad \text{--- (iii)}$$

In matrix representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$\Delta_1 = \frac{\Delta_1}{\Delta} \quad \Delta_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

Where  $\Delta_1 = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix} \begin{matrix} + & - & + \\ - & + & - \\ + & - & + \end{matrix}$

$$= 5(-28-0) + 2(16+0) - 3(0-21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_2 = + \begin{vmatrix} 60 & -2 & -3 \\ -768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix} = 60(-28-0) - 768(-8-0) - 364(0-21)$$
$$= -1680 + 6144 - 8064$$
$$= -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

For  $V_2$ :  $\Delta_2 = + \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$

$$= 5((768 \times 4) - 0) - 4((60 \times 4) - (384 \times -3)) - 3(0 - (768 \times -3))$$

$$= 2880$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$




$$\text{For } V_3: \begin{vmatrix} + & 5 & -2 & 60 \\ - & 4 & -7 & 765 \\ + & -3 & 0 & 384 \end{vmatrix}$$

$$= 5 [(-7 \times 384) - 0] - 4 [(-2 \times 384) - 0] - 3 [(-2 \times 765) - (-7 \times 60)]$$

$$\therefore V_3 = \frac{\Delta_3}{\Delta} = \frac{7020}{-45} = 156 \text{ V}$$

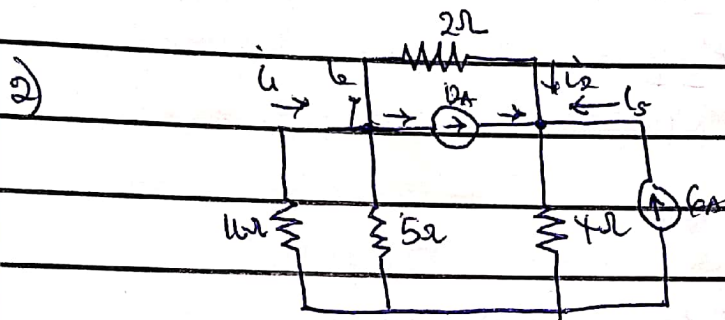Hence  $V_2 = 80$ ,  $V_2 = -64 \text{ V}$ ,  $V_3 = 156 \text{ V}$



At Node 1; KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{20} = \frac{V_1 - V_2}{5} + 12 + \frac{V_1 - V_0}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (i)}$$

At Node 2

$$i_3 + i_2 + i_5 = i_4$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii)}$$

Using Elimination method.



$$120 = -8V_1 + 5V_2 \quad \text{--- (i) } \times -4$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (ii) } \times -8$$

$$-480 = 32V_1 - 20V_2 \quad \text{--- (iii)}$$

$$-1152 = 32V_1 - 28V_2 \quad \text{--- (iv)}$$

Subtract eqn (iii) from

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$V_2 = 24V$$

Subs  $V_2 = 24V$  in eqn (i)

$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6V_2}{-4}$$

$$-4$$


$$V_1 = \frac{144 - 6V_2}{-4}$$

$$-4$$

$$V_1 = 0$$

$$\therefore V_1 = 0V \quad V_2 = 24V$$
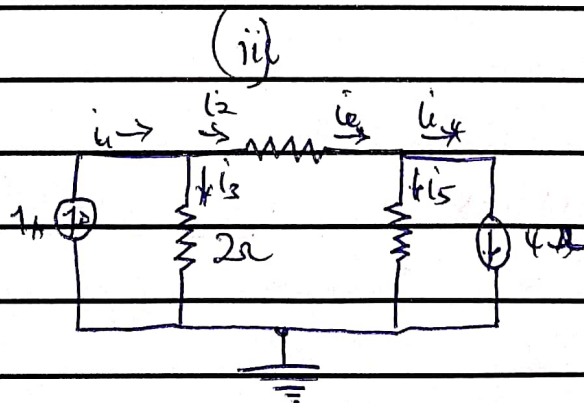
$$i_1 = 0A \quad i_2 = 20A \quad i_3 = 6A \quad i_4 = 12A$$



At Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{2} + \frac{V_1}{4}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \text{ --- (i)}$$

At Node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \text{ --- (ii)}$$

from eqn (i);  $V_2 = 4V_1 - 6$

Sub  $V_2 = 4V_1 - 6$  in eqn (ii)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = 90 / -45$$

$$V_1 = -2V$$

Sub  $V_1 = -2$  in eqn (i)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$

$$\therefore V_1 = -2V, V_2 = -14V$$


Current through the resistors

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6}$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
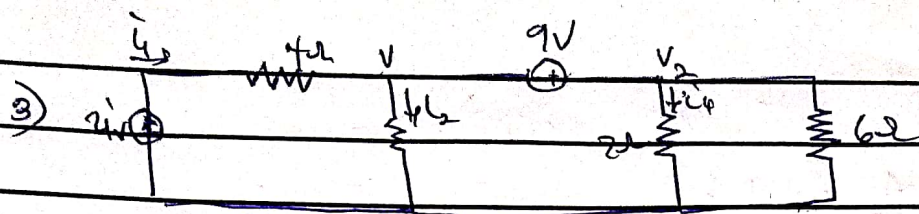
$$i_3 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$





find the current through the 3Ω and 2Ω resistor  
using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 2i}{4} + \frac{V_1}{3} + \frac{V_2}{2} + \frac{V_2}{6} = 0$$

$$7V_1 + 8V_2 - 63 = 0$$

using KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (i)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (ii)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (iii)}$$

$$\text{let } V_2 = 9 + V_1 \quad \text{--- (iv)}$$

Sub. eqn (iv) in (ii)

$$7V_1 = 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

Sub  $V_1 = -0.6$  in eqn (iii)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = 8.4V$$

$$\therefore V_1 = -0.6V \text{ and } V_2 = 8.4V$$


Current through the 3Ω resistor

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$



Current through the  $2\Omega$  resistor

$$I_4 = \frac{V_2}{2} = 8.4 = 4.2A$$

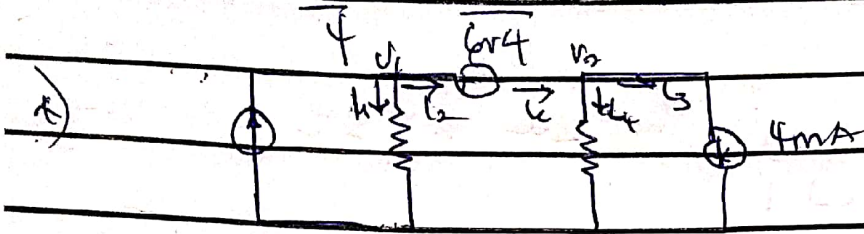

① Node (i) using KCL

$$6mA = I_1 + I_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 + V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \text{--- (i)}$$

② Node (ii)

$$I_2 = I_3 + I_4$$

$$V_1 - V_2 = 4mA + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \text{--- (ii)}$$

Solving  $V_1$  and  $V_2$  simultaneously we have

$$V_1 = 9.5V \text{ and } V_2 = 5.1V$$

∴ Current through  $6\Omega$  resistor

$$I_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A; \quad I_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4A$$

Current through  $12\Omega$  resistor

$$I_3 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A; \quad \therefore V_1 = 9.5V, V_2 = 5.1V$$

$$I_1 = 1.58A, I_4 = 0.43A$$