


Name: Mba Jonah Abali

Matric Number: 17/mt501/187

Department: Computer Engineering

Quiz

1 Solution

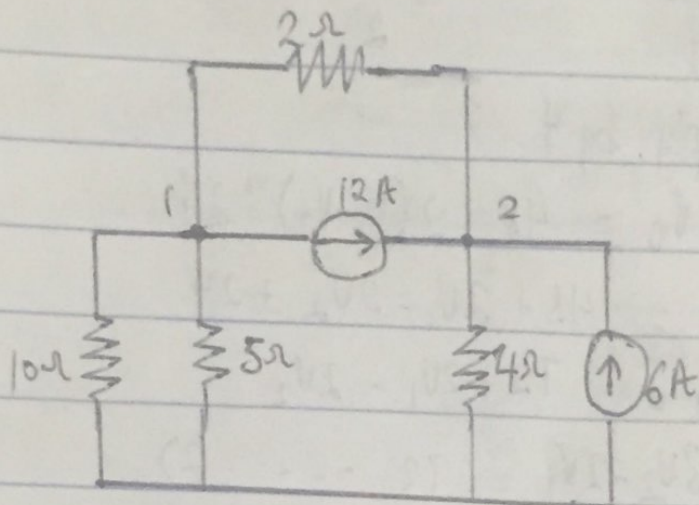

At node 1 with KCL

$$I_1 = I_2 + I_3 + I_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + \frac{V_1 - V_0}{5} + 12A$$

multiply through by 10

$$V_0 - V_1 = 5(V_1 - V_2) + 2(V_1 - V_0) + 120$$

$$V_0 - V_1 = 5V_1 - 5V_2 + 2V_1 - V_0 + 120$$

$$V_0 - V_1 = 7V_1 - 5V_2 + V_0 + 120$$

$$-V_1 = 7V_1 - 5V_2 + V_0 - V_0 + 120$$

$$-V_1 = 7V_1 - 5V_2 + 120$$

$$-8V_1 + 5V_2 = 120 \quad \dots (1)$$

At node 2

$$I_4 = -I_2 - I_5 + I_6$$

$$I_6 = I_4 + I_2 + I_5$$

$$\frac{V_2 - V_0}{4} = 12 + \frac{V_1 - V_2}{2} + 6V$$

multiply by 4

$$V_2 - V_0 = 48 + 2(V_1 - V_2) + 24$$

$$V_2 = 48 + 2V_1 - 2V_2 + 24$$

$$V_2 = 72 + 2V_1 - 2V_2$$

$$3V_2 - 2V_1 = 72 \quad \dots \quad (2)$$

Applying elimination method

$$5V_2 - 8V_1 = 120 \quad \dots \quad (1)$$

$$3V_2 - 2V_1 = 72 \quad \dots \quad (2)$$

$$10V_2 - 16V_1 = 240$$

$$+ \underline{24V_2 - 16V_1 = 576}$$

$$34V_2 = 816$$

$$V_2 = 24V$$

Putting the value of V_2 in eqn (1)

$$5(24) - 8V_1 = 120$$


$$-8V_1 = 120 - 120$$

$$-8V_1 = 0$$

$$V_1 = 0$$

$$I_1 = 0A, I_2 = 0A, I_3 = 6A, I_4 = 12A$$

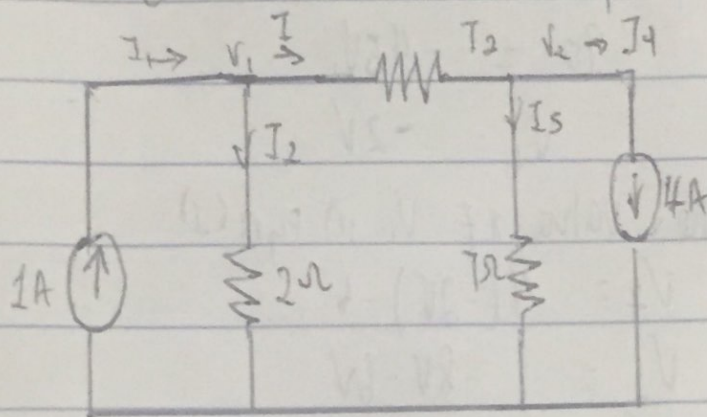ii) Obtain V_1 and V_2 and the currents through these resistors if the 2A current source was replaced by a 1A current source



At node 1

$$I_1 = I_2 + I_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \text{ ----- (1)}$$

At node 2

$$I_2 = I_3 + I_4$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{2}$$

$$7(V_1 - V_2) = 6(28 + V_2)$$

$$7V_1 - 7V_2 = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \dots (2)$$

From eqn(1) $V_2 = 4V_1 - 6$

put eqn(1) in eqn(2)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = -2V$$

put the value of V_1 in eqn(1)

$$V_2 = 4(-2V) - 6$$

$$V_2 = -8V - 6V$$

$$V_2 = -14V$$


Current ~~follow~~ flowing through the resistor

$$I_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = 2A$$

$$I_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$I_6 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$

2

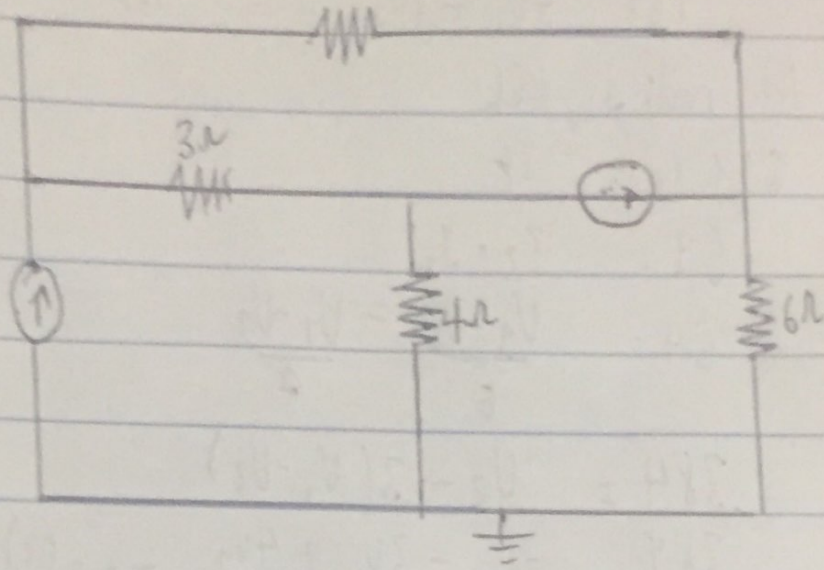

At node 1 using KCL

$$10A = i_1 + i_2$$

$$10A = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

multiply through by 6

$$60A = 3(V_1 - V_2) + 2(V_1 - V_3)$$

$$60A = 3V_1 - 3V_2 + 2V_1 - 2V_3$$

$$60 = 5V_1 - 3V_2 - 2V_3$$

At node 2 using KCL

$$i_2 = I_3 + 6A$$

$$6A = i_2 - I_3$$

$$6A = \frac{V_1 - V_2}{2} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 2(V_2)$$

$$768 = 4V_1 - 7V_2 \quad \dots (ii)$$

At node 3, KCL

$$64 + i_1 = I_3$$

$$64 = I_3 - I_1$$

$$64 = \frac{V_3 - V_0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \quad \dots (iii)$$

in matrix form

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix}$$

$$= 5(-28) + 2(16+0) - 3(0-21)$$

$$\Delta = -45$$

$$\Delta_1 = \begin{bmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{bmatrix}$$

$$= 60(-28) + 2(3072) - 3(0 + 2688)$$

$$= -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$\Delta_2 = \begin{bmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{bmatrix}$$

$$= 5(3072) - 60(16) - 3(1536 + 2304)$$

$$= 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$


$$\Delta_3 = \begin{bmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{bmatrix}$$

$$= 5(-2688) + 2(1536 + 2304) + 60(21)$$

$$= -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$V_1 = 80V, V_2 = -64V, V_3 = 156V$$

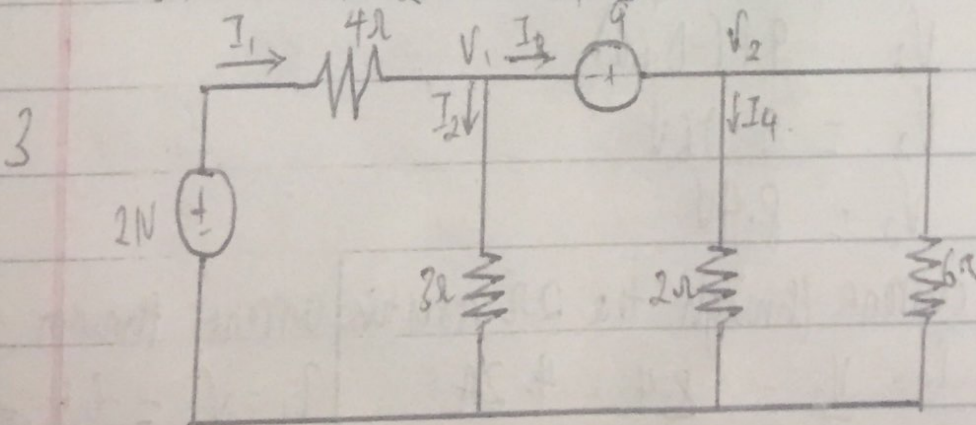

Using KCL at nodal

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1 - 2V}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (i)}$$

Using KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (i)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$V_2 = 9 + V_1$$

Sub $V_2 = 9 + V_1$ in eqn (i)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

Put the value of V_1

$$V_2 = 9 + (-0.6V)$$

$$V_2 = 9 - 0.6V$$

$$V_2 = 8.4V$$


Current through the 2Ω resistor

$$I_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1A$$

Current through the 3Ω resistor

$$I_1 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

4

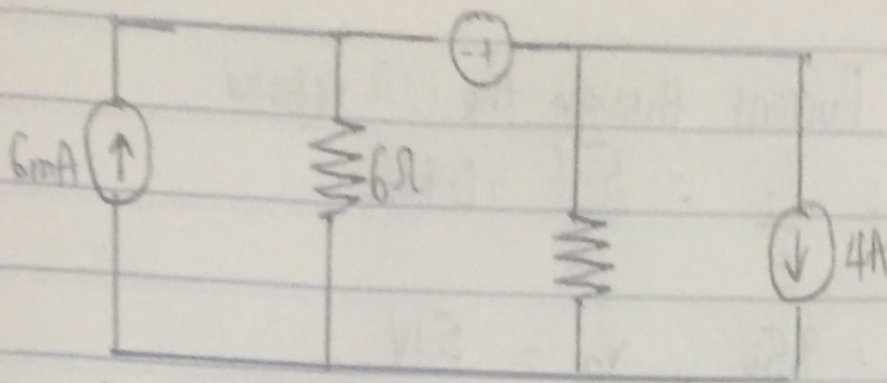

At node 1, using KCL

$$6\text{mA} = I_1 + I_2$$

$$6\text{mA} = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \dots (i)$$

At node 2

$$i_2 = I_2 + I_4$$

$$V_1 - V_2 = 4\text{mA} + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \dots (ii)$$

Solving V_1 and V_2 simultaneously,

$$V_1 = 9.5\text{V} \text{ and } V_2 = 5.1\text{V}$$

Current through the 6Ω resistor

$$I_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58\text{A}, \quad I_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4\text{A}$$

Current through the 12Ω resistor

$$I_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A$$

$$V_1 = 9.5V, \quad V_2 = 5.1V$$

$$I_2 = 1.58A, \quad I_4 = 0.43A$$