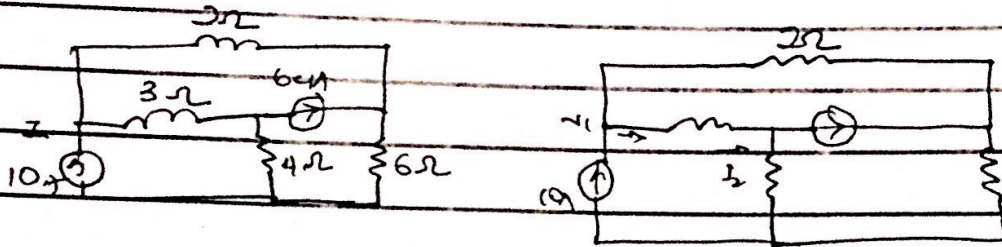


Ejike David Chinyere
 18 / ENGO4 / 078
 Elect / Elect

(1) Find the voltage at node 1, 2 & 3 in the circuit below



Node 1 KCL

$$10 = i_1 + i_2 \rightarrow 10 = \frac{v_1 - v_2}{2} + \frac{v_1 - v_2}{3}$$

$$60 = 3[v_1 - v_2] + 2[v_1 - v_2]$$

$$60 = 3v_1 - 3v_2 + 2v_1 - 2v_2$$

$$60 = 5v_1 - 3v_2 - 2v_2 - 0$$

At Node 2 KCL

$$I_2 = i_2 + 6A$$

$$6A = i_2 - i_3$$

$$6A = \frac{v_1 - v_2}{3} = \frac{v_2 - 0}{4}$$

$$768 = 4[v_1 - v_2] - 3[v_2 - 0]$$

$$768 = 4v_1 - 7v_2 \quad \text{--- (2)}$$

Node 3 KCL

$$6A + i_1 = 15$$

$$6A = 15 - i_1$$

$$6A = \frac{v_3 - 0}{6} - \frac{v_1 - v_3}{2}$$

$$384 = V_3 - 3[V_1 - V_2]$$

$$384 = -3V_1 + 4V_3 \quad \dots$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \dots$$

$$4V_1 - 7V_2 + 10V_3 = 768 \quad \dots$$

$$-3V_3 + 1274 + 1442 + 2584$$

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5[-28-0] + 2(16-0) - 3(0-28)$$

$$= -140 + 32 + 84$$

$$= -44$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60[-28-0] - 768[-8-0] - 384[0-28]$$

$$= 7680 + 6144 - 10752$$

$$= -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = \frac{80V}{2}$$

$$V_2 = \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ 0 & 384 & 4 \end{vmatrix}$$

$$= 5[(768 \times 4) - 0] - 4[(60 \times 4) - [384 \times 3]] - 3[0 - (768 \times 3)]$$

$$= 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$


$$V_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5[(-7 \times 384) - 0] - 4[(-2 \times 384) - 0] - 3[(-2 \times 768) - [-7 \times 60]]$$

$$= -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{45} = 156V$$
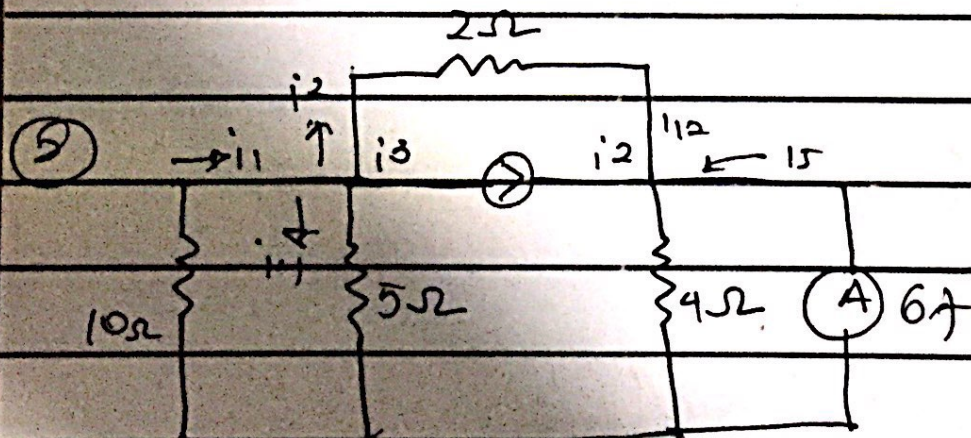
$$V_1 = 80V \quad V_2 = 64V \quad V_3 = 156V$$



Node KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{v_0 - v_1}{10} = \frac{v_1 - v_3}{2} + 12 + \frac{v_1 - v_2}{5}$$

$$0 - v_1 = 5[v_1 - v_2] + 120 + 2[v_1 - 0]$$

$$-v_1 = 5v_1 - 5v_2 + 120 + 2v_1$$

$$120 = -8v_1 + 5v_2 \quad \text{--- (1)}$$

Node 2

$$i_3 + i_2 + i_5 = 16$$

$$12 + \frac{v_1 - v_2}{2} + 6 = \frac{v_2 - 0}{4}$$

$$96 + 4[v_1 - v_2] + 48 = 2[v_2]$$

$$144 + 4v_1 - 4v_2 = 2v_2$$

$$144 = -4v_1 + 6v_2 \quad \text{--- (2)}$$

Using elimination method

$$120 = -8v_1 + 5v_2 \quad \text{--- (1)} \times 4$$

$$144 = -4v_1 + 6v_2 \quad \text{--- (2)} \times 8$$

$$-480 = 32v_1 - 20v_2 \quad \text{--- (3)}$$

$$-1152 = 32v_1 - 48v_2 \quad \text{--- (4)}$$

Subtract eqn 3 from 4

$$-672 = 0 - 28v_2$$

$$-672 = -28v_2$$

$$v_2 = \frac{-672}{-28}$$

$$v_2 = 24 \text{ V}$$

Sub v_2 into eqn 2

$$144 - 4v_1 + 6v_2$$


$$v_1 = \frac{144 - 6[24]}{-4}$$

$$V_1 = \frac{144 - 144}{-4} = 0V$$

$$V_1 = 0V \quad V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = -10A$$

Classwork

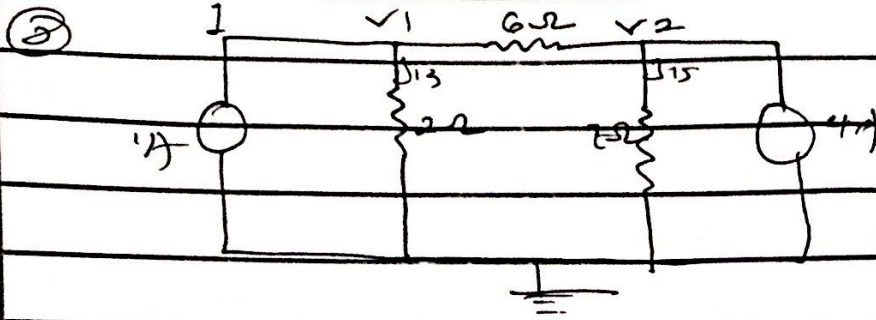

Node 1

$$I_1 = i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad (1)$$

Node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} - 4 + \frac{V_2}{3}$$

$$7[V_1 - V_2] = 16 + 6V_2$$

$$16V = 7V_1 = 13V_2 \quad (2)$$

from eqn (1)

$$v_2 = 4v_1 - 6$$

$$\text{Sub } v_2 = 4v_1 - 6 \text{ into eqn (2)}$$

$$168 = 7v_1 - 15[4v_1 - 6]$$

$$168 = 7v_1 - 60v_1 + 90$$

$$90 = -53v_1$$

$$v_1 = 90 / -53$$

$$v_1 = -2 \text{ V}$$

Subs $v_1 = -2$ into eqn 1

$$6 = 4[-2] - v_2$$

$$6 = -8 - v_2$$

$$v_2 = -8 - 6$$

$$v_2 = -14 \text{ V}$$


$$v_1 = -2 \text{ V}, v_2 = -14 \text{ V}$$

Current through the resistance

$$i_2 = \frac{v_1 - v_2}{6} = \frac{-2 - (-14)}{6} = 2 \text{ A}$$

$$i_3 = \frac{v_1}{2} = \frac{-2}{2} = -1 \text{ A}$$
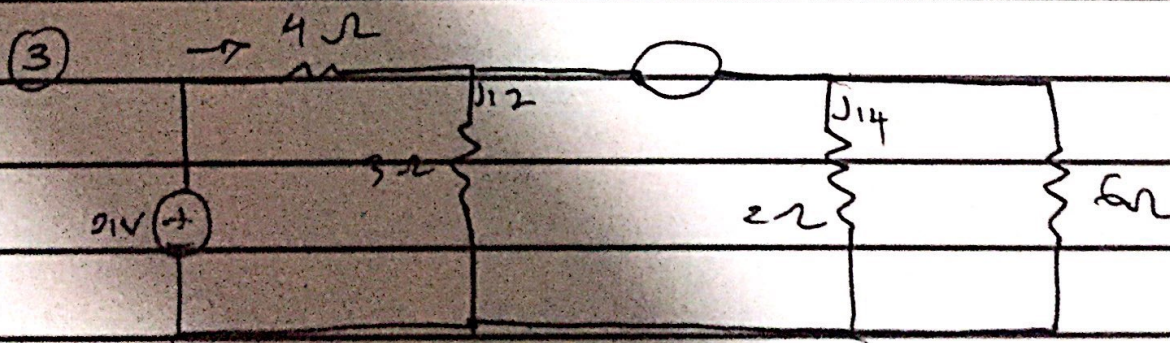
$$i_5 = \frac{v_2}{7} = \frac{-14}{7} = -2 \text{ A}$$



Find the current through 3Ω , 2Ω & 6Ω

Using KCL at Node 1

$$1 \cdot i_2 + i_3 = 0$$

$$\frac{v_1}{4} + \frac{v_1 + v_2}{3} + \frac{v_3}{2}$$

$$7v_1 + 8v_2 - 63 = 0 \quad \text{--- (1)}$$

taking KVC for loop 1

$$-v_1 - 9 + v_2 = 0$$

$$-v_1 + v_2 = 9 \quad \text{--- (2)}$$

$$7v_1 + 8v_2 = 63 \quad \text{--- (1) } \times 1$$

$$-v_1 + v_2 = 9 \quad \times 7$$

$$7v_1 + 8v_2 = 63$$

$$-7v_1 + 7v_2 = 63$$

$$11v_2 = 126$$

from eqn 2 $-v_1 + v_2 = 9$

$$v_2 = 9 + v_1 \quad \text{put into eqn (1)}$$

$$7v_1 + 8(9 + v_1) = 63$$

$$7v_1 + 72 + 8v_1 = 63$$

$$15v_1 = 63 - 72$$

$$15v_1 = -9$$

$$v_1 = -9/15$$

$$v_1 = -0.6V$$

sub $v_1 = 0.61n$ $9u$ (1)

$$-[-0.6] v_2 = 9$$

$$0.6 v_2 = 9$$


$$v_2 = 9 - 0.6 = 8.4 \text{ V}$$

$$v_1 = 0.6 \text{ V} \quad v_2 = 8.4 \text{ V}$$

Current through 3Ω and 2Ω

$$i_3 = \frac{v_2}{3} = \frac{-0.6 - 8.4}{3} \text{ at } 3\Omega$$
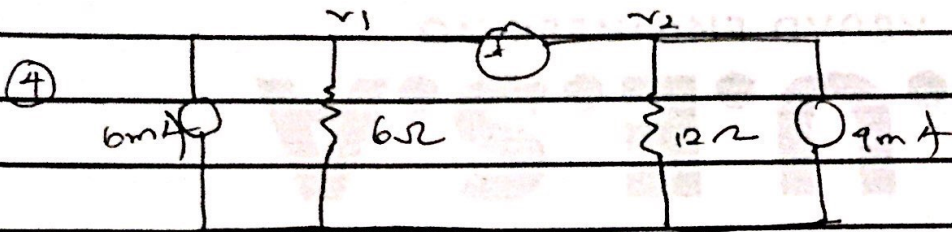
$$i_4 = \frac{v_1}{2} = \frac{8.4}{2} = 4.2 \text{ A at } 2\Omega$$



Find the nodes of the voltage and the current through the 6Ω & 12Ω resistor

$$\text{Take } v_1 - v_2 = 6 \text{ V} \rightarrow i_3$$

at node 1, using KCL

$$6 \text{ mA} = i_3 + i_4$$

$$6 \text{ mA} = \frac{v_1 - 0}{6} + [v_1 - v_2]$$

$$36 = v_1 + 6[v_1 - v_2]$$

$$36 = v_1 + 6v_1 - 6v_2$$

$$36 = 7v_1 - 6v_2 \quad \text{--- (1)}$$

at node 2

$$i_2 = i_3 + i_4$$

$$v_1 = v_2 - 4 \text{ mA} + \frac{v_2 - 0}{12}$$

$$12[V_1 - V_2] = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \text{--- (2)}$$

solving simultaneously

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

Current through the 6Ω resistor -

$$i_1 = \frac{V_1 - V_2}{6} = \frac{9.5 - 5.1}{6} = 1.58 \text{ A}$$

$$i_2 = V_1 - V_2 = 9.5 - 5.1$$

$$= 4.4$$

Current through 5Ω

$$i_4 = \frac{V_2}{5} = \frac{5.1}{5} = 1.02 \text{ A}$$

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

$$i_1 = 1.58 \text{ A}$$

$$i_4 = 1.02 \text{ A}$$