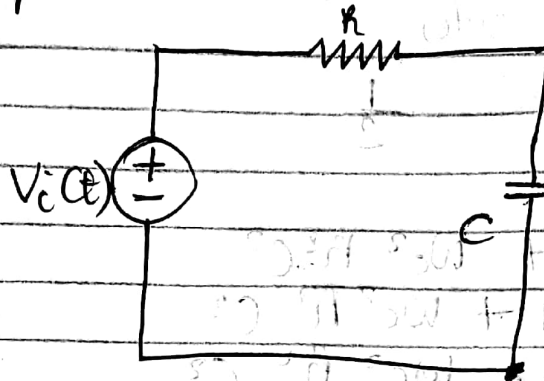


UIDSMADU CELESTINE CHIBURU

17/ENG05/039

Mechatronics Eyr.

2 phase - ENG 322 assignment.



Determine the type of filter shown above and show that its cut-off frequency is  $\omega_c = 1/RC$ .

Solu.

Converting to frequency domain.

$$R = R$$

$$C = 1/j\omega C$$

$$H(\omega) = \frac{V_o}{V_i}$$

Using KVL (series connection)

$$H(\omega) = \frac{V_o}{V_i} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1/j\omega C}{\frac{j\omega RC + 1}{j\omega C}}$$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

where  $H(0) = 1$ ,  $H(\infty) = 0$

The half power frequency which is equivalent to the corner frequency on the BODE plots but in the context of filters is called cut-off frequency  $\omega_c$ , obtained by setting magnitude of  $H(\omega)$   $= \frac{1}{\sqrt{2}}$

Substituting  $\omega_c$   
 $H(\omega_c) =$

$$\frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}}$$

Square both sides

$$\frac{1^2}{1 + \omega_c^2 R^2 C^2} = \frac{1}{2}$$

$$2 \cdot 1^2 = 1 + \omega_c^2 R^2 C^2$$

$$2 = 1 + \omega_c^2 R^2 C^2$$

$$2 - 1 = \omega_c^2 R^2 C^2$$

$$1 = \omega_c^2 R^2 C^2$$

Taking square root of both sides

$$\sqrt{1} = \sqrt{\omega_c^2 R^2 C^2}$$

$$1 = \omega_c R C$$

$$\therefore \omega_c = \frac{1}{RC}$$