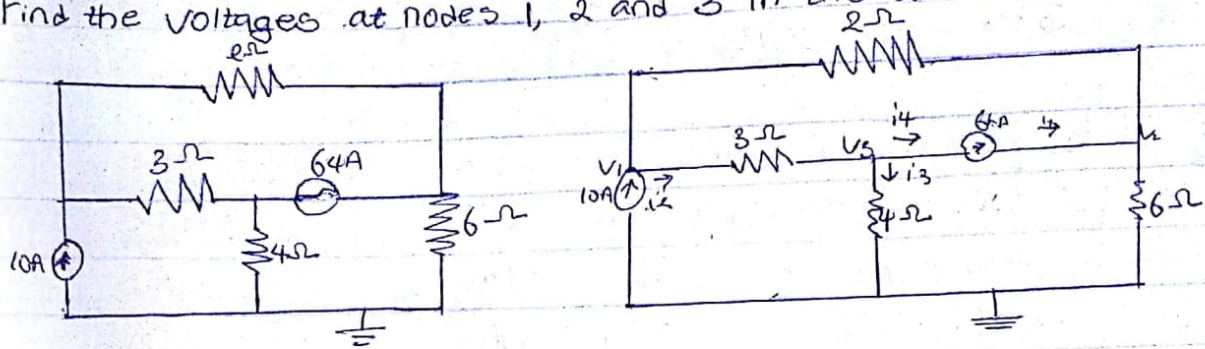


OKOH JOSHUA CHUKWUMA
COMPUTER ENGINEERING
171ENG02/066

1) Find the voltages at nodes 1, 2 and 3 in the circuit below



At node 1, KCL;

$$10 = i_1 + i_2$$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \dots (i)$$

At node 2, KCL;

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2 + 0$$

$$768 = 4V_1 - 7V_2 \dots (ii)$$

At node 3, KCL

$$64 + i_1 = i_5$$

$$64 = i_5 - i_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3$$

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \dots (i)$$

$$4V_1 - 7V_2 = 768 \dots (ii)$$

$$-3V_1 + 4V_3 = 384 \dots (iii)$$

In Matrix Representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{Where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 5(-28-0) + 2(16+0) - 3(0-21) \\ &= -140 + 32 + 63 \\ &= -45 \end{aligned}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 60(-28-0) - 768(-8-0) + 384(0-21) \\ &= -1680 + 6144 - 8064 \\ &= -3600 \end{aligned}$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$\text{For } V_2 : \Delta = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= \cancel{5(768 \times 4) - 0} - \cancel{4((60 \times 4) - (384 \times -3))} - \cancel{3(0 - 768 \times -3)}$$

$$= 2880$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

$$= 5(768 \times 4) - (384 \times 0) - 60(344 \times 4) - (-3 \times 16) + 3((4 \times 384) - (-3 \times 768))$$

$$= 5(3072 - 0) - 60(16 - 0) - 3(1536 + 2304)$$

$$= 5(3072) - 60(16) - 3(3840)$$

$$= 15360 - 960 - 11520$$

$$= 2880V$$


$$\text{For } V_3 : \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5((-7 \times 384) - 0) - 4((-2 \times 384 - 0)) - 3((-2 \times 768) - (-7 \times 60))$$

$$= -7020$$

$$\therefore V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

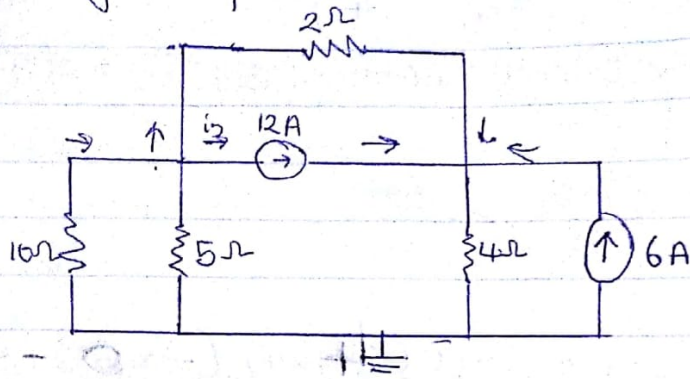2) Find the voltages at Nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below



At node 1; KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_0}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \dots (i)$$

At node 2

$$i_3 + i_2 + i_5 = i_6$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \dots (ii)$$

Using elimination method

$$\times 4 \quad 120 = -8V_1 + 5V_2 \dots (i)$$

$$\times -8 \quad 144 = -4V_1 + 6V_2 \dots (ii)$$

$$-480 = 32V_1 - 20V_2 \quad \text{--- iii}$$

$$-1152 = 32V_1 - 48V_2 \quad \text{--- iv}$$

Subtract eqn (iii) from (iv)

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$V_2 = 24V$$

Subs $V_2 = 24$ in eqn (ii)


$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6V_2}{-4}$$

$$V_1 = 0$$

$$\therefore V_1 = 0V, V_2 = 24V$$

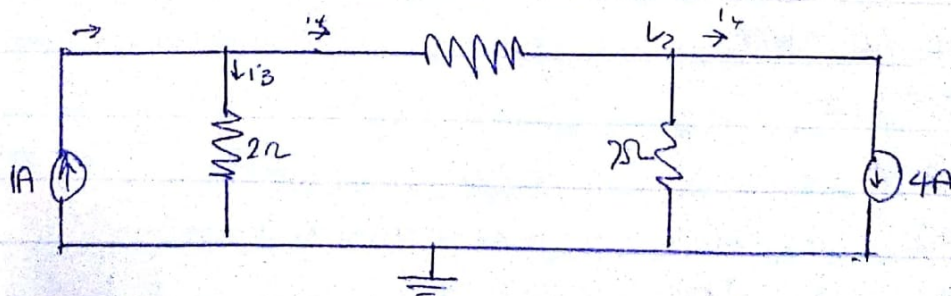*) Obtain V_1 and V_2 and the currents through the resistor for the circuit in example (ic) if the 2A current source was replaced by a 1A current source



At Node 1

$$i = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (i)}$$

At node 2

$$i_2 = i_4 + i_3$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (ii)}$$

From eqn (i), $V_2 = 4V_1 - 6$

Subs $V_2 = 4V_1 - 6$ in eqn (ii)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45}$$

$$V_1 = -2V$$

Sub. $V_1 = -2$ in eqn (i)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$

$$V_1 = -2V, \quad V_2 = -14V$$

Current through the resistor

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$