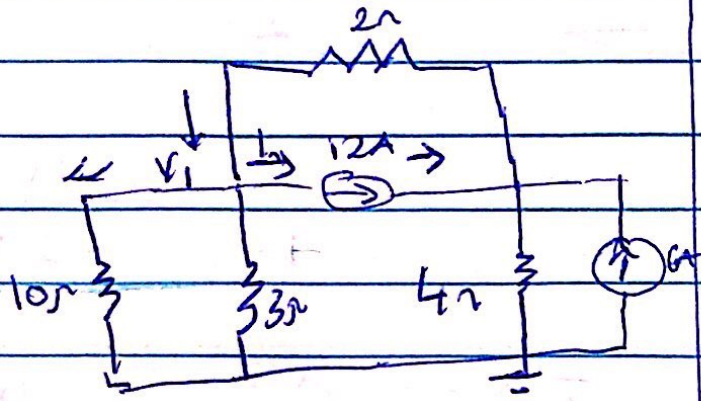


# Okole Steven Ugochukwu

17/ENAO2/070

Computer Engineering  
EEE 322



at node  $v_1$

$$i_3 = i_1 + i_5 + i_6 = 12 \text{ A}$$

$$+ i_6 \quad \therefore 12 = i_3 - i_5 - i_6$$

~~$$12 = \frac{v_1 - v_2}{2}$$~~

$$12 = \frac{v_2 - v_1}{2} \left[ \frac{v_1 - 0}{5} \right] - \left[ \frac{v_1 - 0}{10} \right]$$

$$12 = \frac{v_2 - v_1}{2} - \frac{v_1}{5} - \frac{v_1}{10}$$

$$12 = 5(v_2 - v_1) - 2(v_1) - v_1/10$$

$$120 = 5v_2 - 5v_1 - 2v_1 - v_1$$

$$120 = 5v_2 - 8v_1 \quad \text{--- (1)}$$

from node  $v_2$

$$i_1 + i_2 = i_3 + i_4$$

$$12 + 0 = \frac{v_2 - v_1}{2} + \left[ \frac{v_2}{4} \right]$$

$$18 = \frac{v_2 - v_1}{2} + \frac{v_2}{4}$$

$$18 = 2(v_2 - v_1) + \frac{v_2}{4}$$

$$72 = 3v_2 - 2v_1 \quad \text{--- (2)}$$

Using Simultaneous eqn

$$120 = 5v_2 - 8v_1 \quad \text{--- x 2}$$

$$240 = 10v_2 - 16v_1$$

$$576 = 24v_2 - 16v_1$$

$$-336 = -14v_2$$

$$v_2 = 24 \text{ V}$$

from Eqn (1)

$$120 = 5(24) - 8v_1$$

$$120 = 120 - 8v_1$$

$$8v_1 = 120 - 120$$

$$v_1 = 0 \text{ V}$$

Current flowing through the 2Ω resistor


$$= \frac{v_2 - v_1}{2} = \frac{24 - 0}{2} = 12 \text{ A}$$

while ~~12A~~ current flowing through the 4Ω resistor

$$= \frac{4}{4} = \frac{24}{4} = 3 \text{ A}$$

Due to  $v_1$  being at the end moving through the 10Ω & 5Ω resistor both equal

zero (0).

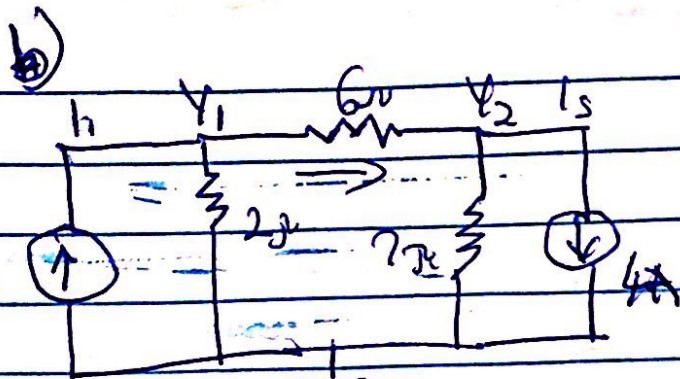

at node 2

$$i_1 = i_2 + i_3$$

$$1 = \left[ \frac{V_1 - V_2}{6} \right] + \left[ \frac{V_1 - V_2}{2} \right]$$

$$1 = \frac{V_1 - V_2}{6} + V_1/2$$

~~$$1 = V_1 - V_2/6$$~~

$$1 = V_1 - V_2 + 3V_1/6$$

~~$$6 = 4V_1 - 2V_2$$~~

$$6 = 4V_1 - 2V_2 \quad (1)$$

$$i = i_4 + i_5$$

$$\left[ \frac{V_1 - V_2}{6} \right] = \left[ \frac{V_2}{7} \right] + 4$$

$$V_1 - V_2/6 - V_2/7 = 4$$

$$7(V_1 - V_2) - 6V_2/7 = 4$$

$$108 = 7V_1 - 13V_2 - 2$$

Solving simultaneously

$$V_1 = -2V \text{ and } V_2 = 14V$$

from this current moving through

the 6Ω

$$V_1 - V_2/6$$

$$= \frac{-2 \cdot 14}{6} = -16/6$$


$$= -2.67A$$

from the current moving through the 2Ω resistor

$$= V_1/2 = -2/2 = -1A$$

current moving through 7Ω

$$= V_2/7 = 14/7 = 2A$$

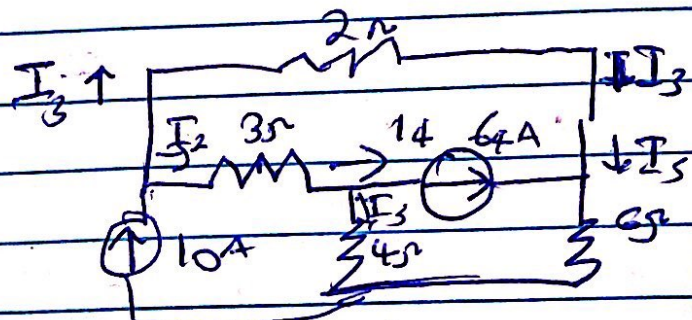

from node 1

$$I_1 = I_2 + I_3$$

$$\Rightarrow 10 = V_1 - V_2/3 + V_1 - V_3/3$$

$$10 = (V_1 - V_2)/3 + (V_1 - V_3)/3$$

$$60 = 2V_1 - 2V_2 + 3V_1 - 3V_3 \quad (1)$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad (1)$$

from node 2

$$I_2 = I_3 + I_4$$

$$V_1 - V_2/3 = V_2/4 + 4$$

$$4V_1 - 4V_2 - 3V_2/12 = 64$$

$$4V_1 - 7V_2/12 = 64$$

$$4V_1 - 7V_2 = 768 - (2)$$

from node 3

$$I_4 + I_5 = I_3$$

$$64 + V_1 - V_3/2 = V_3/6$$

$$64 = \frac{V_3}{6} - \frac{V_1 - V_3}{2}$$

$$64 = \frac{2V_3 - 3V_1 + 3V_3}{6}$$

$$384 = 4V_3 - 3V_1 \quad \text{--- (3)}$$

$$66 = 5V_1 - 2V_2 - 3V_3$$

$$768 = 4V_1 - 7V_2 + 0V_3$$

$$384 = -3V_1 + 0V_2 + 4V_3$$

Using Cramer's rule

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5 \begin{vmatrix} -7 & 0 \\ 0 & 4 \end{vmatrix} + 2 \begin{vmatrix} 4 & 0 \\ -3 & 4 \end{vmatrix} - 3 \begin{vmatrix} 4 & -7 \\ -3 & 0 \end{vmatrix}$$

$$= 5(-28 - 0) + 2(16 - 0) - 3(0 - 21)$$

$$= -140 + 32 + 63 = -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -1 \\ 668 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28) + 2(3072 - 0)$$

$$- 3(60 + 2688)$$

$$= 1680 + 6144 - 8064$$

$$= 6144 - 9744$$

$$= -3600$$

$$V_1 = \frac{-3600}{-45} = 80V$$

$$\Delta = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(3072 - 0) - 60(16 - 0)$$

$$- 3(1536 + 2304)$$

$$= 15360 - 960 - 11520$$

$$= 15360 - 12480$$

$$= 2880$$

$$V_2 = \frac{2880}{-45} = -64V$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5(-2688 - 0) + 2$$

$$(1536 + 2304) + 60(0 - 21)$$

$$= -13440 + 7080 - 1260$$

$$= -7020$$

$$V_3 = \frac{-7020}{-45}$$

$$= 156V$$