

OGBONNA VICTOR CHIBUZO



17/ENGR04048

Electrical/Electronics Engineering

EE E 322 Circuit Theory 2 Assignment

Solution

① Redrawing the circuit diagram

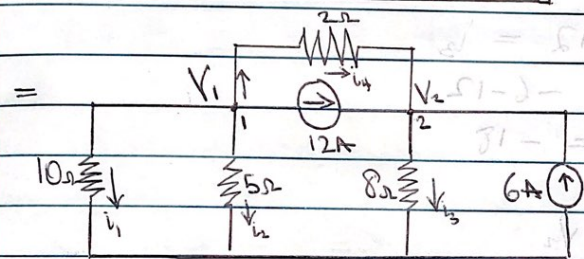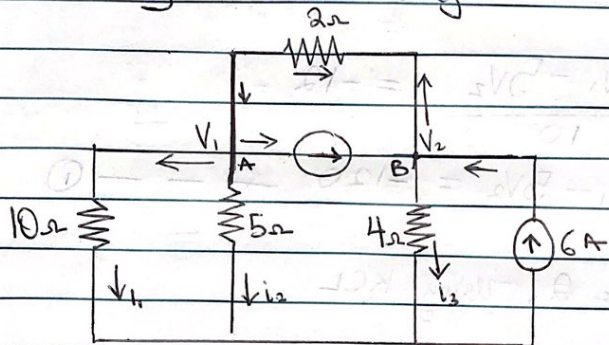

② From node 1, using KCL = $0 - iV = i$

$$i_1 + i_2 + i_4 = -12A$$

$$\Rightarrow i_1 + i_2 + i_4 + 12 = 0$$

$$\Rightarrow i_1 = \frac{V_1 - 0}{10} = \frac{V_1}{10}$$

$$i_2 = \frac{V_1 - 0}{5} = \frac{V_1}{5}$$

$$i_4 = \frac{V_1 - V_2}{2}$$

$$\Rightarrow \frac{V_1}{10} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = -12$$

$$= \frac{V_1}{10} + \frac{2V_1}{10} + \frac{5(V_1 - V_2)}{10} = -12$$

$$\Rightarrow \frac{V_1 + 2V_1 + 5V_1 - 5V_2}{10} = -12$$

$$\Rightarrow \frac{8V_1 - 5V_2}{10} = -12$$

$$\Rightarrow 8V_1 - 5V_2 = -120 \quad \text{--- (i)}$$

from node 2; using KCL

$$i_4 + 6 + 12 = i_3$$

$$i_4 - i_3 = -6 - 12$$

$$i_4 - i_3 = -18$$

$$i_4 = \frac{V_1 - V_2}{2}$$

$$i_3 = \frac{V_2 - 0}{4} = \frac{V_2}{4}$$

$$\Rightarrow \frac{V_1 - V_2}{2} - \frac{V_2}{4} = -18$$

$$= \frac{2(V_1 - V_2) - V_2}{4} = -18$$

$$\frac{2V_1 - 2V_2 - V_2}{4} = -18$$

$$2V_1 - 3V_2 = (-18 \times 4)$$

$$\Rightarrow 2V_1 - 3V_2 = -72 \quad \text{--- (ii)}$$

$$8V_1 - 5V_2 = -120 \text{ --- (i) } \times 3$$

$$2V_1 - 3V_2 = -72 \text{ --- (ii) } \times 5$$

$$24V_1 - 15V_2 = -360$$

$$-10V_1 - 15V_2 = -360$$

$$14V_1 = 0$$

$$V_1 = 0$$

Substitute $V_1 = 0$ into any of the eqns

$$8(0) - 5V_2 = -120$$

$$-5V_2 = -120$$

$$V_2 = \frac{-120}{-5} = 24V$$

$$V_1 = 0 \text{ \& } V_2 = 24V$$

$$\therefore i_1 = \frac{V_1}{10} = \frac{0}{10}$$

$$= 0A$$

$$i_2 = \frac{V_1}{5} = \frac{0}{5}$$

$$= 0A$$

$$i_3 = \frac{V_2}{4} = \frac{24}{4}$$

$$= 6A$$

$$i_4 = \frac{V_1 - V_2}{2} = \frac{0 - 24}{2} = -12A$$

$$\therefore V_1 = 0V, V_2 = 24V$$


$$i_1 = 0A$$

$$i_3 = 6A$$

$$i_2 = 0A$$

$$i_4 = -12A$$

Question 2 Solution

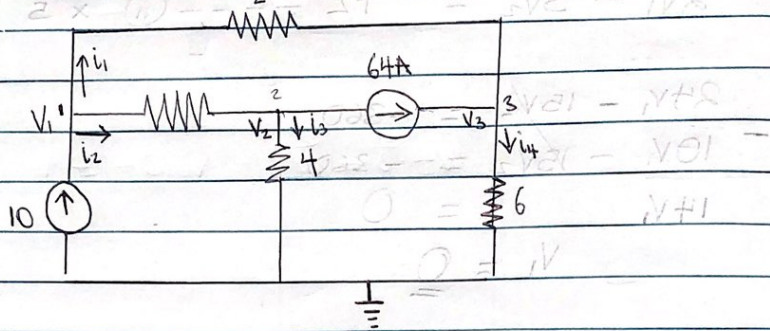

(a) For node 1; $i_1 + i_2 = 10$
using KCL

$$\frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3} = 10$$

(b) node 2; using KCL

$$\frac{V_1 - V_2}{3} = 64 + \frac{V_2}{4}$$

$$\therefore i_2 = 64 + i_3$$

(c) node 3; using KCL

$$\frac{V_3}{6} = 64 + \frac{V_1 - V_3}{2}$$

$$\therefore i_4 = 64 + i_1$$

Simplify;

$$10 = \frac{5}{6}V_1 - \frac{1}{3}V_2 - \frac{1}{2}V_3$$

$$64 = \frac{1}{3}V_1 - \frac{7}{12}V_2 + 0V_3$$

$$64 = -\frac{1}{2}V_1 - 0V_2 + \frac{2}{3}V_3$$

Using matrix form to solve;

$$\begin{bmatrix} 10 \\ 64 \\ 64 \end{bmatrix} = \begin{bmatrix} \frac{5}{6} & -\frac{1}{3} & -\frac{1}{2} \\ \frac{1}{3} & -\frac{7}{12} & 0 \\ -\frac{1}{2} & 0 & \frac{2}{3} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$b = Ax$

$$x = A^{-1}b = \dots = \dots + \dots$$

$$A^{-1}b = \begin{bmatrix} 3.73 & -2.13 & 2.8 \\ 2.13 & -2.93 & 1.6 \\ 2.8 & -1.6 & 3.6 \end{bmatrix} \begin{bmatrix} 10 \\ 64 \\ -64 \end{bmatrix}$$

$$x = \begin{bmatrix} 80 \\ -64 \\ 156 \end{bmatrix}$$

$$\Rightarrow V_1 = 80V \quad V_2 = -64V \quad V_3 = 156V$$

Question 3 Solution

Using KCL @ node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\rightarrow \frac{V-21}{4} + \frac{V}{3} + \frac{V_1}{6} + \frac{V_1}{2} = 0$$

$$\Rightarrow \frac{3(V-21) + 4V + 2V_1 + 6V_1}{12} = 0$$

$$\Rightarrow 3V - 63 + 4V + 2V_1 + 6V_1 = 0$$

$$7V + 8V_1 - 63 = 0$$

$$7V + 8V_1 = 63 \quad \text{--- --- --- (1)}$$

Using KVL for loop 1

$$\rightarrow -V - 9 + V_1 = 0$$

$$-V + V_1 = 9 \quad \text{--- --- --- (2)}$$

$$7V + 8V_1 = 63$$

$$-V + V_1 = 9$$

Solving simultaneously,

$$V = -0.6V \quad V_1 = 8.4V$$

* Current through the 3Ω resistor;
Using nodal analysis

$$I_{3\Omega} = \frac{V - 0}{3}$$

$$= \frac{-0.6 - 0}{3} = -0.2$$

$$\therefore I_{3\Omega} = -0.2A //$$


* Current through the 2Ω resistor,

$$I_{2\Omega} = \frac{V_1 - 0}{2}$$

$$= \frac{8.4 - 0}{2} = 4.2$$

$$\therefore I_{2\Omega} = 4.2A //$$

Question 4 Solution

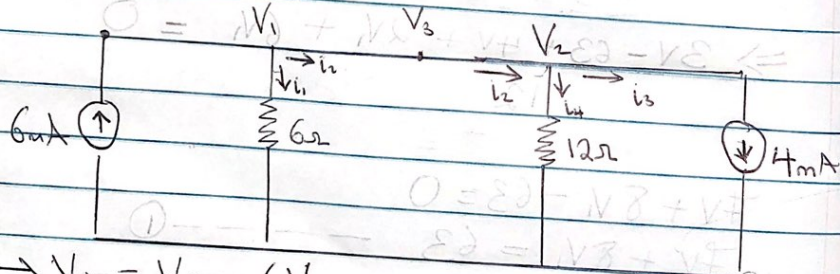

$$\rightarrow V_1 - V_2 = 6V$$

assume $V_1 - V_2 = i_2$

at node 1, using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1}{6} + (V_1 - V_2)$$

$$6 \text{ mA} = \frac{V_1 + 6(V_1 - V_2)}{6}$$

$$6 \text{ mA} = \frac{V_1 + 6V_1 - 6V_2}{6}$$

$$36 = 7V_1 - 6V_2 \quad \text{--- --- --- (i)}$$

(*) at node 2 using KCL

$$i_2 = i_4 + i_3$$

$$i_2 = i_4 + 4 \text{ mA}$$

$$\Rightarrow 4 \text{ mA} = i_2 - i_4$$

$$4 \text{ mA} = \frac{(V_1 - V_2) - V_2}{12}$$

$$4 \text{ mA} = \frac{12(V_1 - V_2) - V_2}{12}$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \text{--- --- --- (ii)}$$

Solving eqn (i) & (ii) simultaneously, we have

$$V_1 = 9.5 \text{ V} \quad V_2 = 5.1 \text{ V}$$

Current through the 6Ω ($I_{6\Omega}$) \Rightarrow Current through the 12Ω ($I_{12\Omega}$)

$$i_1 = \frac{V_1}{6}$$

$$= \frac{9.5}{6}$$

$$= 1.58 \text{ A} //$$

$$i_2 = V_1 - V_2$$

$$= 9.5 - 5.1 = 4.4 \text{ A} //$$

$$i_4 = \frac{V_2}{12}$$

$$= \frac{5.1}{12} = 0.43 \text{ A}$$

$$\therefore V_1 = 9.5 \text{ V}, \quad V_2 = 5.1 \text{ V}$$

$$I_{6\Omega} = 1.58 \text{ A} \quad \& \quad I_{12\Omega} = 0.43 \text{ A}$$