


Ugah - Uche Chukwura

17/ENG04/071

ELECT / BLECT

Circuit Theory Assignment

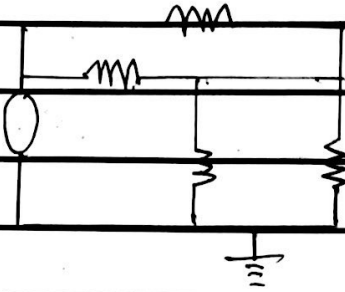① Find the voltages at node 1, 2 and 3 in the circuit below.



Node 1 KCL

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3}$$

multiply through by 6

$$60 = 3(V_1 - V_2) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 3V_2 - 2V_2 \quad \text{--- (1)}$$

At Node 2 KCL

$$I_2 = i_3 + i_4$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

~~$$V_1 = 0V \quad V_2 = 24V$$~~

~~$$i_1 = 0A, \quad i_2 = 0A, \quad i_3 = 6A, \quad i_4 = -12A$$~~

multiply through by 7

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (2)}$$

Node 3 kcl

$$64 + i_1 = 13$$

$$64 = 13 - i_1$$

$$64 = \frac{V_3 - 6}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \quad \text{--- (3)}$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (1)}$$

$$4V_1 - 7V_2 + 0V_3 = 768 \quad \text{--- (2)}$$

$$-3V_1 + 0V_2 + 4V_3 = 384$$

matrix Rep

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 5(-28-0) + 2(16+0) - 3(0-21) \\ &= -140 + 32 + 63 \\ &= -45 \end{aligned}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28-0) - 768(-8-0) - 384(0-21)$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80V$$

$$V_2 = \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5((768 \times 4) - 0) - 4((60 \times 4) - (384 \times 3)) - 3(0 - (768 \times 3))$$

$$= 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$


$$V_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5((-7 \times 384) - 0) - 4((-2 \times 384) - 0) - 3((-2 \times 768) - (-7 \times 60))$$

$$= -7020$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$
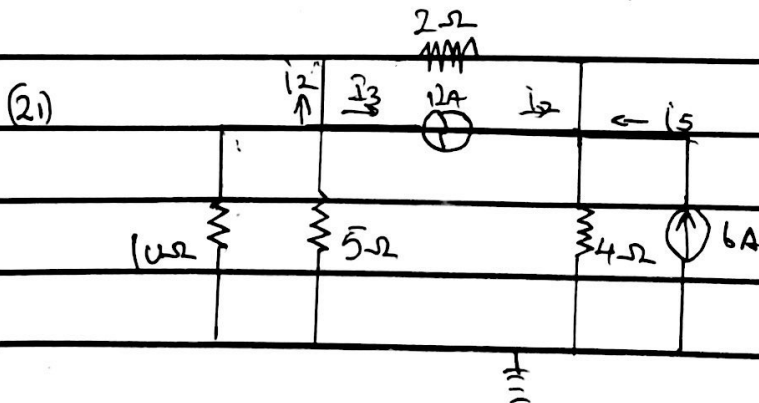
$$\therefore V_1 = 80V, V_2 = -64V, V_3 = 156V$$



Node 1 KCL

$$i_1 = i_2 + i_3 + i_4$$

$$V_0 - V_1 = V_1 - V_2 + 12 + V_1 - V_2$$

10 2 5

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$+120 = -8V_1 + 5V_2 \quad \text{--- (1)}$$

Node 2

$$i_3 + i_2 + i_5 = 16$$

$$12 + \frac{V_1 - V_2}{2} + 6 = V_2 - 0$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 + 48 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (2)}$$

Using Elimination method

$$120 = -8V_1 + 5V_2 \quad \text{--- (1) } \times 4$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (2) } \times 8$$

$$-480 = 32V_1 + 20V_2 \quad \text{--- (iii)}$$

$$-1152 = 32V_1 - 48V_2 \quad \text{--- (iv)}$$

Subtract eqn (3) from (4)

$$-672 = 0 - 28V_2$$

$$-672 = -28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$-28$$

$$V_2 = 24 \text{ V}$$

Sub V_2 into eq (1)


$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6(-24)}{-4}$$

$$V_1 = \frac{-144 - 144}{-4} = 0V$$

$$V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = -12A$$

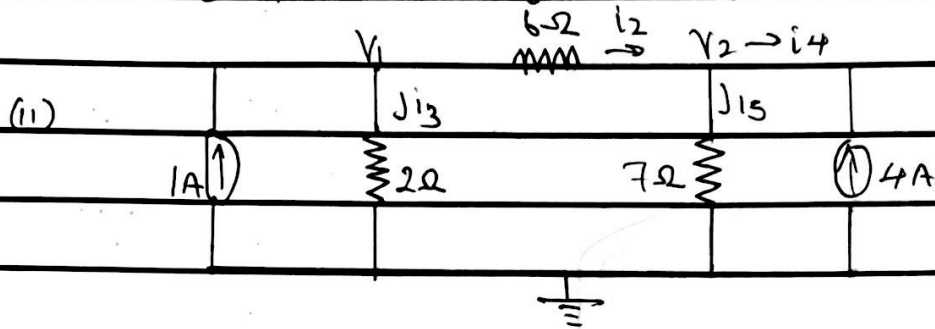

Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (1)}$$

Node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 6(4 + V_2)$$

$$7V_1 - 7V_2 = 168 + 6V_2$$

$$\therefore 168 = 7V_1 - 13V_2 \quad \text{--- (2)}$$

From equation (1)

$$V_2 = 4V_1 - 6$$

$$\text{Sub } V_2 = 4V_1 - 6 \text{ into eqn (2)}$$

$$168 = 7V_1 - 13(4V_1 - 0)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45}$$

$$V_1 = -2V$$

Subs $V_1 = -2$ into eqn (1)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$V_1 = -2V, V_2 = -14V$$

Current through the resistors.

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
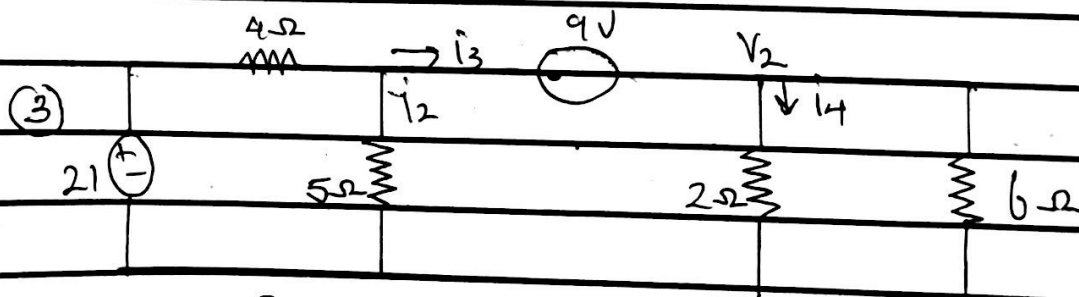
$$i_3 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the 3Ω and 2Ω resistors

Use KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - b_3 = 0 \quad \text{--- (1)}$$

taking KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (1)}$$

$$7V_1 + 8V_2 = b_3 \quad \text{--- (1)}$$

$$-V_1 + V_2 = 9$$

from eqn (2) $-V_1 + V_2 = 9$

$$V_2 = 9 + V_1 \quad \text{put into eqn (1)}$$

$$7V_1 + 8(9 + V_1) = b_3$$

$$7V_1 + 72 + 8V_1 = b_3$$

$$15V_1 = b_3 - 72$$

$$V_1 = \frac{-9}{15}$$

$$V_1 = -0.6 \text{ V}$$

Sub $V_1 = -0.6$ in eqn (1)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = 9 - 0.6 = 8.4 \text{ V}$$


$$\therefore V_1 = 0.6 \text{ V} \quad V_2 = 8.4 \text{ V}$$

Current through 3Ω and 2Ω

$$i_3 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2 \text{ A at } 3\Omega$$
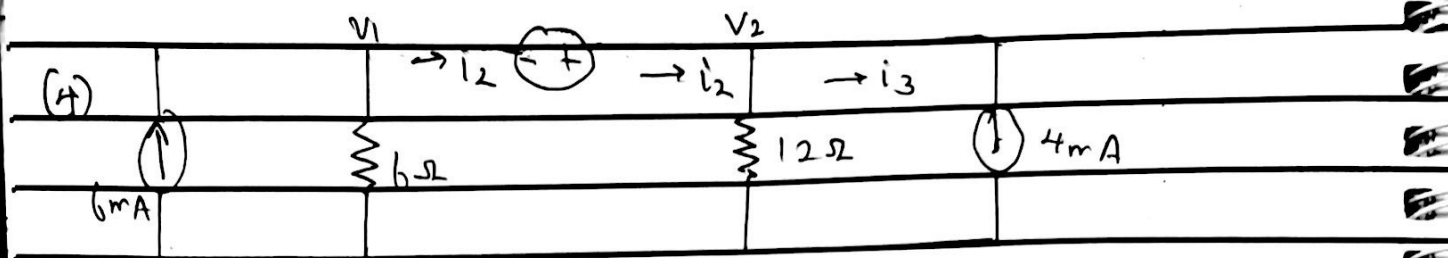
$$i_4 = \frac{V_2}{4} = \frac{8.4}{4} = 2.1 \text{ A at } 2\Omega$$





find the nodes at the voltage and the current through the 6Ω and 12Ω resistor.

Take $V_1 - V_2 = 6V \rightarrow i_2$

at node 1 Using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$31 = 7V_1 - 6V_2 \quad \text{--- (1)}$$

At Node 3

$$i_2 = i_3 + i_4$$

$$\frac{V_1 - V_2}{12} = 4mA + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 + V_2$$

$$48 = 12V_1 - 11V_2 \quad \text{--- (2)}$$

Solving V_1 and V_2 Simultaneously we have

$$V_1 = 9.5V$$

$$V_2 = 5.1V$$

Current through the 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

$$i_2 = \frac{V_1 - V_2}{6} = \frac{9.5 - 5.1}{6} = 0.73A = 730mA$$

Current through 12Ω

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43 \text{ A}$$

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

$$I_1 = 1.58 \text{ A}$$

$$I_4 = 0.43 \text{ A}$$