

Name: Udangha Rite Chidum.


Matric No: 17/ENG 04/1069.

Department: Electrical Electronics Engineering.

EEE 323

Circuit theory. 2.

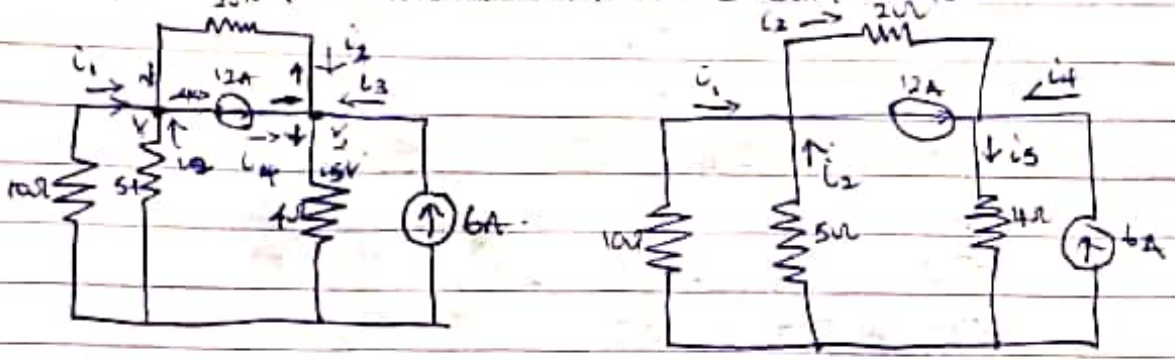1) Find the voltages of nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below.



Solution -

At node 1:

$$\frac{-V_1}{10} - \frac{V_1}{5} = 12 + \frac{V_1 - V_2}{2}$$

$$\frac{-V_1 - 2V_1}{10} = 12 + \frac{V_1 - V_2}{2}$$

$$\frac{-3V_1}{10} = 12 + \frac{V_1 - V_2}{2}$$

$$-3V_1 = 120 + 5V_1 - 5V_2.$$

$$-120 = 8V_1 - 5V_2 \rightarrow \text{eqvi.}$$

At node 2:

$$\frac{V_2 - 0}{4} = 12 + 6 + \frac{V_1 - V_2}{2}$$

$$\frac{V_2}{4} = 18 + \frac{V_1 - V_2}{2}$$

$$V_2 = 72 + 2V_1 - 2V_2.$$

$$-72 = 2V_1 - 3V_2. \rightarrow \text{eqvii}$$

$$-120 = 8V_1 - 5V_2 \rightarrow \text{equi ii}$$

$$-72 = 2V_1 - 3V_2 \rightarrow \text{equi iii}$$

Solving simultaneously:

$$-120 = 8V_1 - 5V_2 \times 2$$

$$-72 = 2V_1 - 3V_2 \times 8$$

$$-240 = 16V_1 - 10V_2$$

$$-576 = 16V_1 - 24V_2$$

$$-336 = -14V_2$$

$$V_2 = \frac{-336}{-14}$$

$$V_2 = 24$$

Sub V_2 in equi iii

$$-72 = 2V_1 - 3(24)$$

$$-72 + 72 = 2V_1$$

$$V_1 = 0$$

$$i_1 = \frac{-V_1}{10}$$

$$i_1 = \frac{0}{10} = 0$$

$$i_3 = \frac{V_1 - V_2}{2}$$

$$= \frac{-24}{2}$$

$$= -12 \text{ A}$$


$$i_2 = \frac{V_1}{5}$$

$$= 0$$

$$i_4 = 6 \text{ A}$$

$$i_5 = \frac{V_2}{4}$$

$$= 0$$

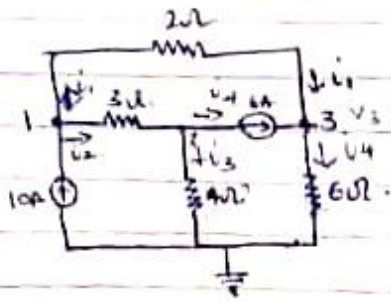

Find the voltages at node 1, 2 and 3 in the circuit.

At node 1

Using KCL.

$$10A = i_1 + i_2.$$

$$10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$10 = \frac{3(V_1 - V_3) + 2(V_1 - V_2)}{6}$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \rightarrow \text{equation (i)}$$

At node 2,

Using KCL

$$i_2 = i_3 + 6A$$

$$\frac{V_1 - V_2}{3} = \frac{V_2 - 0}{4} + 6A$$

$$\frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4} = 6A$$

$$\frac{4(V_1 - V_2) - 3V_2}{12} = 6A$$

$$4V_1 - 7V_2 = 72 \rightarrow \text{equation (ii)}$$

At node 3;

Using KCL

$$i_4 = i_1 + i_3$$

$$6A = i_1 + i_3$$

$$6A = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$6A = \frac{V_3 - 3V_1 + 3V_3}{6}$$

$$\begin{array}{c|c|c} 2 & 6 & 2 \\ \hline 6 & 3 & \end{array}$$

$$384 = V_3 - 3V_1 + 3V_2$$

$$384 = 4V_3 - 3V_1 \rightarrow \text{eq. vi}$$

$$60 = 5V_1 - 2V_2 - 3V_3 \rightarrow \text{eq. vi}$$

$$768 = 4V_1 - 7V_2 - 0 \rightarrow \text{eq. vii}$$

$$384 = -3V_1 - 0 + 4V_3 \rightarrow \text{eq. viii}$$

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$\Delta = 5(-28) - (-2(16)) - 3(-21)$$

$$= -140 + 32 + 63$$

$$= 95 - 140$$

$$= -45$$

For A_1

$$\begin{bmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ -384 & 0 & 4 \end{bmatrix}$$

$$A_1 = 60(-28) - (-2(3072)) - 3(2688)$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$V_1 = \frac{A_1}{\Delta} = \frac{-3600}{-45} = 80V$$

For Δ_2

$$\Delta_2 = \begin{bmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{bmatrix}$$

$$= 5(768 \times 4) - 60(16) - 3(1536 - (-2304))$$

$$= 15360 - 960 - 3(11520)$$

$$= 15360 - 12480$$

$$= 2880$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64V$$

For A_3

$$A_3 = \begin{bmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{bmatrix}$$

$$\begin{aligned} \rightarrow \frac{5}{\Delta} &= 5(2688) - (-2(1536 - 62304)) + 60(-21) \\ &= -26880 + 7680 - 1260 \\ &= -28140 + 7680 - 14700 + 7680 \\ &= -20460 - 7020 \end{aligned}$$


$$V_3 = \frac{A_3}{\Delta}$$

$$= \frac{-20460}{45} = \frac{-7020}{-45} = 156v$$

$$V_1 = 80v$$

$$V_2 = 64v$$

$$V_3 = 156v$$

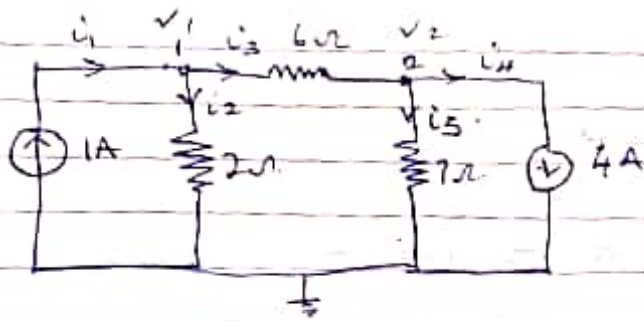

At node 1.

$$1 = \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{6}$$

$$1 = \frac{3V_1 + V_1 - V_2}{6}$$

$$6 = 4V_1 - V_2 \rightarrow \text{eqvi}$$

At node 2

$$\frac{V_1 - V_2}{6} = \frac{V_2 - 0}{7} + 4$$

$$4 = \frac{V_1 - V_2}{6} - \frac{V_2}{7}$$

$$4 = \frac{7V_1 - 7V_2 - 6V_2}{42}$$

$$168 = 7V_1 - 13V_2 \rightarrow \text{eqvii}$$

$$6 = 4V_1 - V_2 \rightarrow \text{eqvi}$$

$$168 = 7V_1 - 13V_2 \rightarrow \text{eqvii}$$

Solving simultaneously.

$$4 \cdot 6 = 4V_1 - V_2 \rightarrow \text{eqvi} \times 7$$

$$168 = 7V_1 - 13V_2 \rightarrow \text{eqvii} \times 4$$

$$42 = 28V_1 - 7V_2$$

$$672 = 28V_1 - 52V_2$$

$$630 = -45V_2$$

$$V_2 = \frac{-630}{45}$$

$$V_2 = -14V$$

Sub V_2 in eqvi

$$6 = 4V_1 - (-14)$$

$$6 - 14 = 4V_1 \quad -8 = 4V_1 \quad V_1 = -2V$$

$$i_1 = 1A$$

$$i_2 = \frac{V_1}{2} = \frac{2}{2} = 1A - 1A =$$

$$i_3 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = \frac{12}{6} = 2A$$

$$i_4 = 4A$$

$$i_5 = \frac{V_2}{7}$$

$$= \frac{-14}{7}$$

$$= -2A$$

$$i_1 = 1A$$

$$i_2 = 7A$$

$$i_3 = 2A$$

$$i_4 = 4A$$

$$i_5 = -2A$$