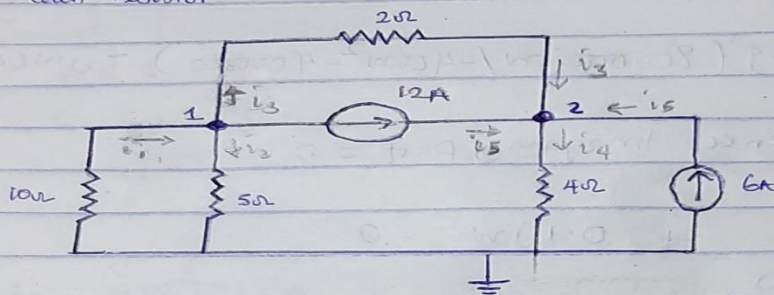


**OLOMOWEWE RASHIDA OMOWUNMI**  
**17/ENG04/057**  
**ELECTRICAL ELECTRONICS ENGINEERING**  
**CIRCUIT THEORY (EEE322)**  
**SOLUTION:**

OLOMOWEWE RASHIDA OMOWUNMI  
 17/ENG04/057  
 ELECTRICAL ELECTRONICS ENGINEERING  
 CIRCUIT THEORY II (EEE 322)

Q1

Find the Voltage at node 1 and 2 and determine the Current flowing through each resistor.



Solution.

At Node 1, Applying KCL

$$i_5 + i_2 + i_3 = i_1$$

Where;

$$i_5 = 12A, \quad i_2 = \frac{V_1}{5}, \quad i_3 = \frac{V_1 - V_2}{2}, \quad i_1 = \frac{-V_1}{10}$$

$$\therefore \frac{12}{5} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = \frac{-V_1}{10}$$

Multiply thro by 10.

$$\therefore 120 + 2V_1 + 5V_1 - 5V_2 = -V_1$$

$$120 = -7V_1 - V_1 + 5V_2$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (1)}$$

At Node 2.

Applying KCL

$$i_4 = i_5 + i_6 + i_3$$

$$i_4 = \frac{V_2}{4}, \quad i_5 = 12A, \quad i_6 = 6A, \quad i_3 = \frac{V_1 - V_2}{2}$$

$$\Rightarrow \frac{V_2}{4} = 12 + 6 + \frac{V_1 - V_2}{2}$$

Multiply thro by 4

$$\Rightarrow V_2 = (18 \times 4) + 2V_1 - 2V_2$$

$$V_2 = 72 + 2V_1 - 2V_2$$

$$72 = -2V_2 - V_2 + 2V_1$$

$$72 = +3V_2 - 2V_1 \quad \dots \text{eq (2)}$$

Solving eq (1) and eq (2) simultaneously!

$$120 = -8V_1 + 5V_2$$

$$72 = +8V_2 - 2V_1 \quad \otimes 4$$

$$\therefore 120 = -8V_1 + 5V_2$$

$$-288 = +8V_1 + 12V_2$$

$$-168 = 0 - 7V_2$$

$$-168 = -7V_2$$

$$V_2 = 168 / 7$$

$$V_2 = 24 \text{ V}$$

\(\therefore\) Put  $V_2 = 24$  into eq (2).

$$\therefore 72 = 8V_2 - 2V_1$$

$$72 = 8(24) - 2V_1$$

$$72 = 72 - 2V_1$$

$$-2V_1 = 0$$

$$V_1 = 0$$

$$V_2 = 24 \text{ V}$$

$$V_1 = 0$$

$$i_1 = 0 \text{ A}$$

$$i_2 = 0 \text{ A}$$

$$i_3 = -12 \text{ A}$$

$$i_4 = 6 \text{ A}$$

$$i_5 = 12 \text{ A}$$

$$i_6 = 6 \text{ A}$$

Current Values:

$$i_5 = 12 \text{ A}$$

$$i_2 = V_1 / 5 \quad \therefore i_2 = 0 \text{ A}$$

$$i_3 = (V_1 - V_2) / 2$$

$$i_3 = -24 / 2$$

$$i_3 = -12 \text{ A}$$

$$i_1 = -V_1 / 10 = 0 \text{ A}$$

$$i_4 = 24 / 4 = 6 \text{ A}$$

$$i_6 = 6 \text{ A}$$

Current across resistor ( $10\Omega$ );  $i_1 = 0A$ .


Current across resistor ( $5\Omega$ );  $i_2 = 0A$ .

Current across resistor ( $2\Omega$ );  $i_3 = -12A$ .

Current across resistor ( $4\Omega$ );  $i_4 = 6A$ .

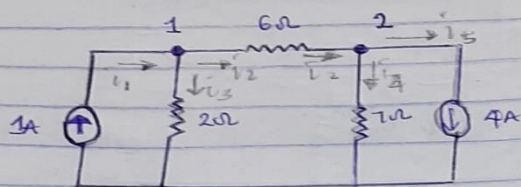Q2.

Obtain  $V_1$  and  $V_2$  and the current through the resistor the circuit in example (ii) if the  $2A$  current source was replaced by a  $1A$  current source.



Solution:

At Node 1; Applying KCL

$$i_1 = i_2 + i_3$$

$$\text{where } i_1 = 1A \quad i_2 = \frac{V_1 - V_2}{6} \quad i_3 = \frac{V_1}{2}$$

$$\therefore 1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

Multiply through by 6.

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \dots \text{eqn (1)}$$

At Node 2; Applying KCL

$$i_2 = i_4 + i_5$$

$$\therefore \text{where } i_2 = \frac{V_1 - V_2}{6} \quad i_4 = \frac{V_2}{7} \quad i_5 = 4$$

$$\therefore \frac{V_1 - V_2}{6} = \frac{V_2}{7} + 4$$

Multiply through by 42.

$$\therefore 7V_1 - 7V_2 = 6V_2 + 168$$

$$168 = 7V_1 - 13V_2 \quad \dots \text{eqn (2)}$$

From equation (1) Make  $V_2$  subject.

$$V_2 = 6 - 4V_1 \quad \text{--- (eq 3)}$$

∴ Put eq (3) into eqn (2)

$$∴ 168 = 7V_1 - 13V_2$$

$$168 = 7V_1 - 13(6 + 4V_1)$$

$$168 = 7V_1 + 78 - 52V_1$$

$$∴ 168 + (78) = 7V_1 - 52V_1$$

$$168 - 78 = 7V_1 - 52V_1$$

$$90 = -45V_1$$

$$V_1 = -2$$

∴ Put  $V_1 = -2$  into eqn 3

$$∴ V_2 = -6 + 4V_1$$

$$V_2 = -6 + 4(-2)$$

$$V_2 = -6 - 8$$

$$V_2 = -14 \text{ V}$$

Current Across each resistor;

∴ At resistor ( $2\Omega$ );  $i_3$

$$∴ i_3 = V_1 / 2$$

$$= -2 / 2$$

$$= -1 \text{ A}$$

at resistor ( $6\Omega$ );  $i_2$

$$i_2 = (V_1 - V_2) / 6$$

$$\Rightarrow -2 - (-14) / 6$$

$$\Rightarrow 12 / 6$$

$$= 2 \text{ A}$$

at resistor ( $7\Omega$ );  $i_4$


$$i_4 = V_2 / 7$$

$$= -14 / 7$$

$$= -2 \text{ A}$$

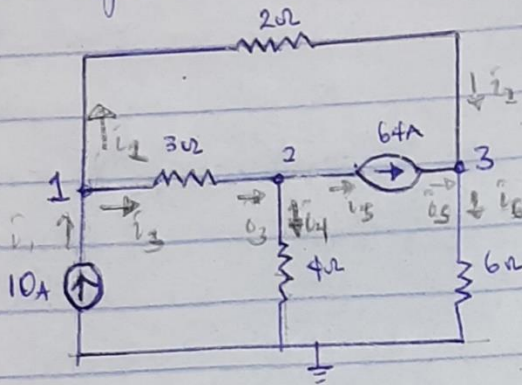Q3.

Find the Voltages at Nodes 1, 2 and 3 in the Circuit below;



Solution:

At Node 1:

$$\bar{i}_1 = \bar{i}_2 + \bar{i}_3$$

$$\bar{i}_1 = 10A, \quad \bar{i}_2 = \frac{V_1 - V_3}{2} \quad ; \quad \bar{i}_3 = \frac{V_1 - V_2}{3}$$

$$i. \quad 10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

Multiply thro by 6.

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 3V_3 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \dots \quad \text{eq(1)}$$

At Node 2:

$$\bar{i}_4 + \bar{i}_5 = \bar{i}_6$$

Where

$$\bar{i}_5 = 64A, \quad \bar{i}_3 = \frac{V_1 - V_2}{3}, \quad \bar{i}_4 = \frac{V_2}{4}$$

$$64 + \frac{V_2}{4} = \frac{V_1 - V_2}{3}$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2}{4}$$

Multiply through by 12.

$$768 = 4(V_1 - V_2) - 3(V_2)$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \quad \dots \text{eqn (2)}$$

At Node B:

$$i_5 + i_2 = i_6$$

where  $i_5 = 64$ ,  $i_2 = \frac{V_1 - V_3}{2}$ ,  $i_6 = \frac{V_3}{6}$ .

$$\therefore 64 + \frac{V_1 - V_3}{2} = \frac{V_3}{6}$$

$$64 = \frac{V_3}{6} - \frac{(V_1 - V_3)}{2}$$

Multiply through by 6.

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = \cancel{3V_3} + 3V_3 - 3V_1 + 3V_3$$

$$384 = 4V_3 - 3V_1 \quad \dots \text{eqn (3)}$$

From eqn 1 Make  $V_1$  Subject

$$\therefore 768 = 4V_1 - 7V_2$$

$$768 + 7V_2 = 4V_1$$

$$V_1 = 192 + 1.75V_2 \quad \dots \text{eq (4)}$$

put eqn (4) into eqn (3)

$$384 = 4V_3 - 3V_1$$

$$384 = 4V_3 - 3(192 + 1.75V_2)$$

$$384 = 4V_3 - 3(192 + 1.75V_2)$$

$$384 = 4V_3 - 576 - 5.25V_2$$

$$960 = 4V_3 - 5.25V_2$$

Divide through by (4)

$$240 = V_3 - 1.3125V_2$$

$$\therefore V_3 = 240 + 1.3125V_2 \quad \dots \text{Eq 5}$$

$\therefore$  Put eqn (4) and eqn (5) into eqn (1)

$$\text{eqn 4} \Rightarrow V_1 = 192 + 1.75V_2$$

$$\text{eqn 5} \Rightarrow V_3 = 240 + 1.3125V_2$$

$$\therefore \text{eqn 1} \Rightarrow 60 = 5V_1 - 2V_2 - 3V_3$$

$$\therefore 60 = 5(192 + 1.75V_2) - 2V_2 - 3(240 + 1.3125V_2)$$

$$60 = 960 + 8.75V_2 - 2V_2 - 720 - 3.9375V_2$$

$$\therefore 60 = 240 + 2.8125V_2$$

$$240 - 60 = 2.8125V_2$$

$$2.8125V_2 = -180$$

$$V_2 = -180 \div (2.8125)$$

$$V_2 = -64 \text{ V}$$

$\therefore$  put  $V_2 = -64$  into eqn (5) and eqn (4)

$\therefore$  eqn (5)

$$V_3 = 240 + 1.3125V_2$$

$$V_3 = 240 + 1.3125(-64)$$

$$V_3 = 240 - 84$$

$$V_3 = 156 \text{ V}$$

$$\text{eqn (4)} ; V_1 = 192 + 1.75V_2$$

$$V_1 = 192 + 1.75(-64)$$

$$V_1 = 192 + (-112)$$

$$V_1 = 80 \text{ V}$$

$$\therefore V_1 = 80 \text{ V}, \quad V_2 = -64 \text{ V}, \quad V_3 = 156 \text{ V}$$