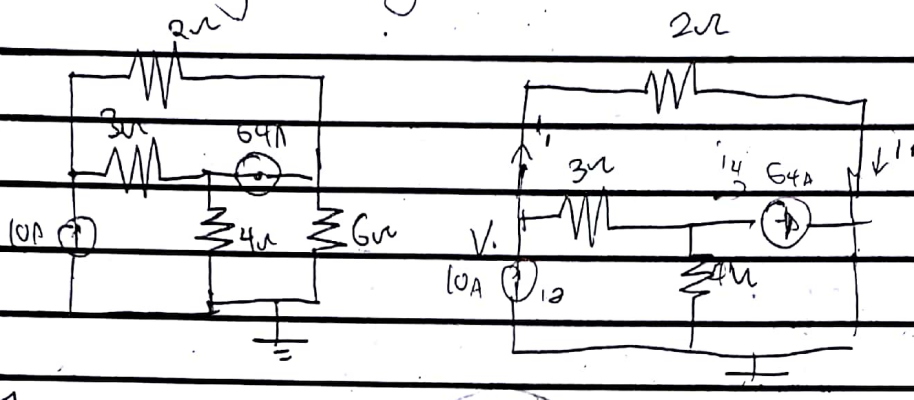


Modulim Tochukwu Adrian

17/Eng04/041

Electrical/Electronics Engineering

Circuit Theory assignment II



node 1, kel

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{3}$$

$$60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 3V_3 - 2V_2 \quad \text{--- i)}$$

node 2 -

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \quad \text{--- ii)}$$

node 3

$$64 + i_1 = i_5$$

$$64 = i_5 - i_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{3}$$

$$6 \quad 2$$

$$384 = V_1 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \quad \dots \text{ (ii)}$$

Cramer's rule

$$5V_1 - 2V_2 - 3V_3 = 0$$

$$4V_1 - 7V_2 + 0V_3 = 768$$

$$-3V_1 + 0V_2 + 4V_3 = 384$$

convert to matrix

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

find determinant

$$= 5(-28 - 0) - (-2(16 - 0)) + (-3(0 - 21))$$

$$\Rightarrow -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$\text{determinant} = 60(-28 - 0) + 2(-768(-8 - 0)) - 384(0 - 21)$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$\therefore V_1 = \frac{-3600}{-45} = 80V$$

$$-45$$

$$V_2 = \Delta_2 \begin{bmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{bmatrix}$$

$$= 5((768 \times 4) - 0) - 4(240 - 1152) - 3(0 - 2304)$$

$$= 72880$$

$$V_2 = \frac{72880}{-45} = -64V$$

$$V_3 = \Delta_3 \begin{bmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{bmatrix}$$

$$= 5((-7 \times 384) - 0) - 4((-2 \times 384) - 0) - 5((-2 \times 768) - (7 \times 60))$$

$$= -7020$$


$$V_3 = \Delta_3 = \frac{-7020}{-45} = 156V$$

$$V_1 = 80V$$

$$V_2 = 64V$$

$$V_3 = 156V$$

2) Find Voltage

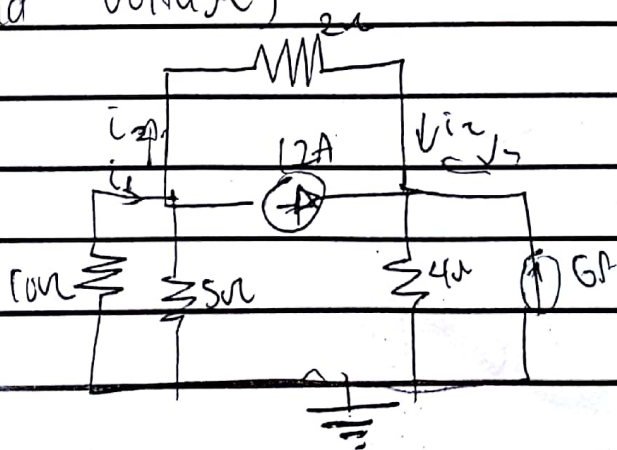

At node 1, KCL

$$i_1 = 6 + 4$$

$$i_1 = i_2 + i_3 + i_4$$

$$V_0 - V_1 = \frac{V_1 - V_2}{2} + i_2 + \frac{V_1 - V_2}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \dots \text{I}$$

node 2

$$i_5 + i_2 + i_3 = 6$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \dots \text{II}$$

using elimination method

$$120 = -8V_1 + 5V_2 \dots \text{I}$$

$$144 = -4V_1 + 6V_2$$

$$-480 = 32V_1 - 20V_2 \dots \text{III}$$

$$-1152 = 32V_1 - 48V_2 \dots \text{IV}$$

$$+672 = 0 - 28V_2$$

$$\therefore V_2 = 24V$$

Sub V_2 in eq II)

$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6(24)}{-4}$$

$$V_1 = 0$$

$$V_1 = 0V$$

$$V_2 = 24V$$


$$i_3 = 6A$$

$$\therefore i_1 = 0A \quad i_4 = 12A$$

$$i_2 = 0A$$

$$i_3 = 6A$$

11) Obtain V_1 and V_2

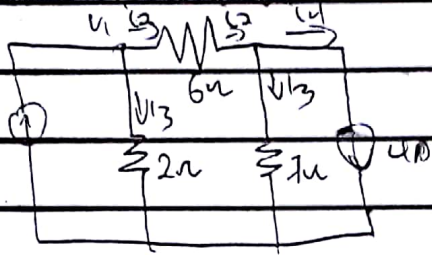

node 1

$$i = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2} \Rightarrow 6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \text{--- (1)}$$

At node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (1)}$$

from eqn (1) $V_2 = 4V_1 - 6$

sub $V_2 = 4V_1 - 6$ in eqn (1)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = -2V$$

sub $V_1 = -2$ in (1)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$V_1 = -2V, \quad V_2 = -14V$$

Current through the resistors

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - 14}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A = 1A$$
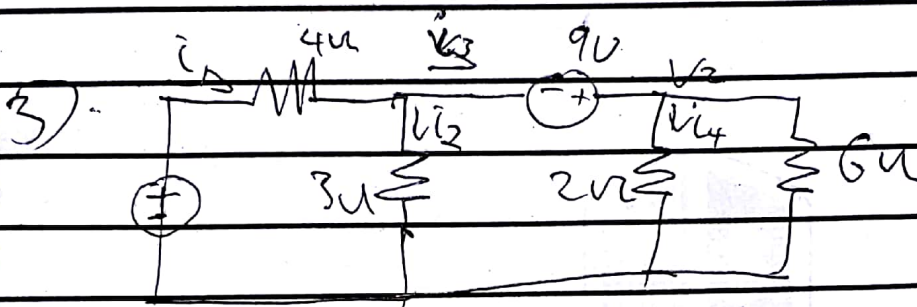
$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Using KCL of node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 9}{4} + \frac{V_1}{3} + \frac{V_1 - V_2}{6} + \frac{V_1}{4} = 0$$

$$7V_1 + 8V_2 - 63 = 0$$

$$-V_1 - 9 + V_2 = 0 \quad \text{KVL for loop 3}$$

$$-V_1 + V_2 = 9 \quad \text{--- (i)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (ii)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

By simplifying

$$V_2 = 9 + V_1 \quad \text{--- (iii)}$$

Substitute in (ii)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$\therefore 15V_1 = -9$$

$$V_1 = -0.6V$$

Substitute $V_1 = -0.6$ in eqn (1)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = 8.4V$$


$$\therefore V_1 = -0.6V \text{ and } V_2 = 8.4V$$

Current through the 3Ω resistor

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the 2Ω resistor

$$\frac{V_2}{4} = \frac{8.4}{4} = 2.1A$$

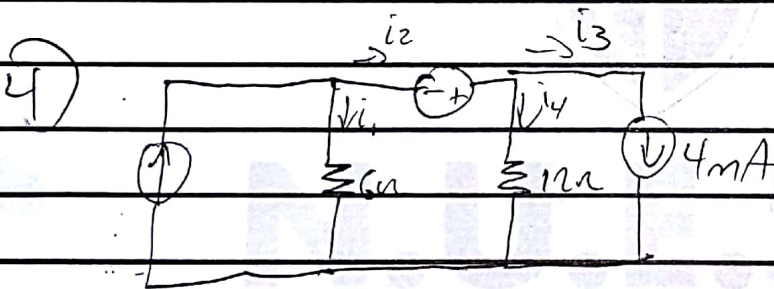

find the node voltages and current

assume $V_1 - V_2 = 6V \Rightarrow i_2$

at node 1, using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \dots \dots 1)$$

At Node 2

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4\text{mA} + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \dots (1)$$

Solving V_1 and V_2 simultaneously

$$V_1 = 9.5\text{V} \quad \text{and} \quad V_2 = 5.1\text{V}$$

Current through 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58\text{A}$$

$$i_2 = V_1 - V_2 = 9.5 - 5.1 \\ = 4.4\text{A}$$

Current through the 12Ω resistor

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43\text{A}$$

$$V_1 = 9.5\text{V}$$

$$V_2 = 5.1\text{V}$$

$$i_1 = 1.58\text{A}$$

$$i_2 = 0.43\text{A}$$