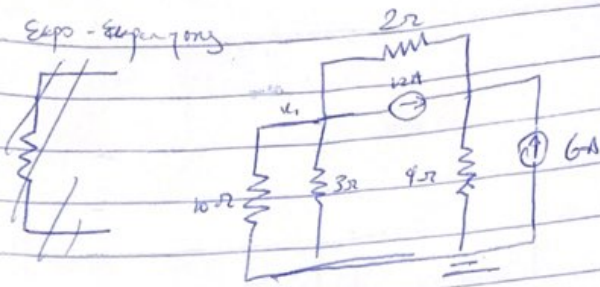


17/05/2018

Electric Circuit

Oru Supra-superpony



at node v_1

$$i_3 = i_1 + i_5 + i_6 = 12 + i_5 + i_6$$

$$\therefore 12 = i_3 - i_5 - i_6$$

$$12 = \frac{v_2 - v_1}{2} - \left[\frac{v_1 - 0}{5} \right] - \left[\frac{v_1 - 0}{10} \right]$$

$$12 = \frac{5(v_2 - v_1) - 2(v_1) - v_1}{10}$$

$$120 = 5v_2 - 5v_1 - 2v_1 - v_1$$

$$120 = 5v_2 - 8v_1 \rightarrow (1)$$

from node v_2

$$i_1 + i_2 + i_3 + i_4$$

$$12 + 6 = \frac{v_2 - v_1}{2} + \left[\frac{v_2}{4} \right]$$

$$18 = \frac{v_2 - v_1}{2} + \frac{v_2}{4}$$

$$18 = \frac{2(v_2 - v_1) + v_2}{4}$$

$$72 = 3v_2 - 2v_1 \rightarrow (2)$$

$$120 = 5v_2 - 8v_1$$

$$72 = 3v_2 - 2v_1$$

$$240 = 10V_2 - 16V_1$$

$$576 = 24V_2 - 16V_1$$

$$\underline{-336 = -14V_2}$$

$$V_2 = 24V$$

from eq (i)

$$120 = 5(24) - 8V_1$$

$$120 = 120 - 8V_1$$

$$8V_1 = 120 - 120$$

$$V_1 = 0V$$

Current flowing through the 2Ω resistor

$$= \frac{V_2 - V_1}{2} = \frac{24 - 0}{2} = 12A$$


Current through the 4Ω resistor

$$= \frac{V_2}{4} = \frac{24}{4} = 6A$$

Due to V_1 being zero the current going through the 10Ω and 5Ω resistor through the 10Ω and 5Ω resistor both equals zero.

17

①

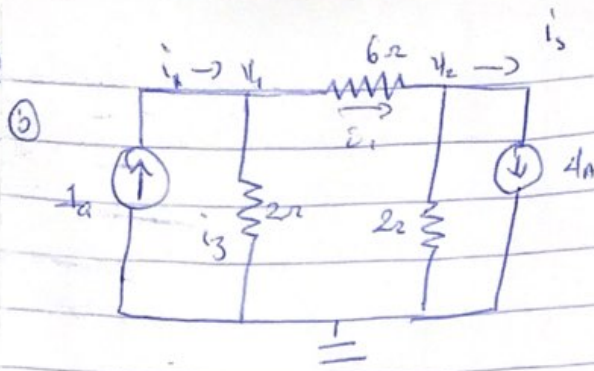

at node 1

$$i_1 = i_2 + i_5$$

$$1 = \left[\frac{V_1 - V_2}{6} \right] + \left[\frac{V_1 - 0}{2} \right]$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$1 = \frac{V_1 - V_2 + 3V_1}{6}$$

$$6 = 4V_1 - V_2 \quad \text{--- (i)}$$

at node 2

$$i_2 = i_4 + i_5$$

$$\left[\frac{V_1 - V_2}{6} \right] = \left[\frac{V_2}{2} \right] + 4$$

$$\frac{V_1 - V_2}{6} - \frac{V_2}{2} = 4$$

$$\frac{7(V_1 - V_2) - 6V_2}{42} = 4$$

$$108 = 7V_1 - 13V_2 \quad \text{--- (2)}$$

$$V_1 = -2V \quad \text{and} \quad V_2 = -14V$$

From this Current through the 6Ω

$$= \frac{V_1 - V_2}{6}$$

$$= \frac{-2 - 14}{6} = \frac{-16}{6}$$


$$= -2.67\text{A}$$

Current through the 2Ω resistor

$$\frac{V_1}{2} = \frac{-2}{2} = -1\text{A}$$

Current through 7Ω
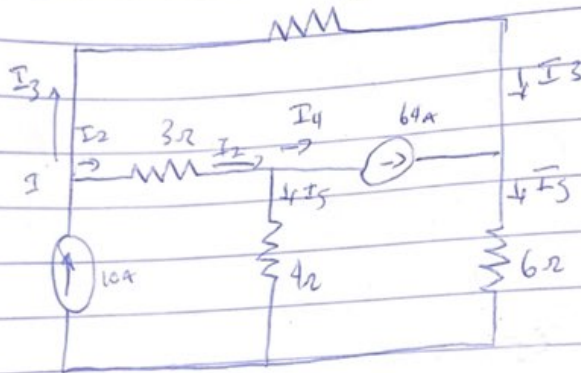
$$= \frac{V_2}{7} = \frac{-14}{7} = -2\text{A}$$



From node 1

$$I_1 = I_2 + I_3$$

$$10 = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{3}$$

$$10 = \frac{(V_1 - V_2)2 + (V_1 - V_3)3}{6}$$

$$60 = 2V_1 - 2V_2 + 3V_1 - 3V_3$$

$$60 = 5V_1 - 2V_2 - 3V_2 \quad (1)$$

from node 2

$$\underline{I_2} = \underline{I_8} + \underline{I_4}$$

$$\frac{V_1 - V_2}{3} = \frac{V_2}{4} + 64$$

$$\frac{V_1 - V_2}{3} - \frac{V_2}{4} = 64$$

$$\frac{4V_1 - 4V_2 - 3V_2}{12} = 64$$

$$\frac{4V_1 - 7V_2}{12} = 64$$

$$4V_1 - 7V_2 = 768 \quad (2)$$

from node 3

$$\underline{I_4} + \underline{I_3} = \underline{I_5}$$

$$64 + \frac{V_1 - V_3}{2} = \frac{V_3}{6}$$

$$64 = \frac{V_3}{6} - \frac{(V_1 - V_3)}{2}$$

$$64 = \frac{2V_3 - 3V_1 + 3V_1}{6}$$

$$384 = 4V_3 - 3V_1 \quad (3)$$

$$\therefore 60 = 5V_1 - 5V_2 - 3V_3$$

$$768 = 4V_1 - 7V_2 + 0V_3$$

$$384 = -3V_1 + 0V_2 + 4V_3$$

using Cramer's Rule

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5 \begin{vmatrix} -7 & 0 \\ 0 & 4 \end{vmatrix} + 2 \begin{vmatrix} 4 & 0 \\ -3 & 4 \end{vmatrix} - 3 \begin{vmatrix} 4 & -7 \\ -3 & 0 \end{vmatrix}$$

$$= 5(-28 - 0) + 2(16 - 0) - 3(0 - 21)$$

$$= -140 + 32 + 63 = -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -1 \\ 168 & -3 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28) + 2(3072 - 0) - 3(0 + 2688)$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$V_1 = \frac{-3600}{-45} = 80 \text{ V}$$

$$\Delta_2 = \begin{vmatrix} 5 & 62 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(3072 - 0) - 60(16 - 0) - 3(1536 + 2304)$$

$$= 15360 - 960 - 11520$$

$$= 15360 - 12480 = 2880$$

$$V_1 = \frac{2880}{-45} = -64 \text{ V}$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -3 & 765 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5(-2688 - 0) + 2(1536 + 2304) + 60(0 - 21)$$

$$= -13440 + 7680 - 1260$$

$$V_3 = \frac{-7020}{-45} = 156 \text{ V}$$