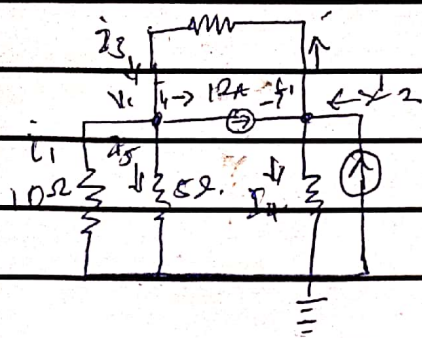


AA.)



$$I_1 = 12 \text{ Amps}$$

$$I_2 = 6 \text{ Amps}$$

at node  $V_1$

$$I_3 = I_1 + I_5 + I_6 = 12 + I_5 + I_6$$

$$12 = I_3 - (I_5 + I_6)$$

$$12 = \frac{V_2 - V_1}{2} - \left( \frac{V_1 - 0}{5} \right) - \left( \frac{V_1 - 0}{10} \right)$$

$$12 = \frac{V_2 - V_1}{2} - \frac{V_1}{5} - \frac{V_1}{10}$$

$$12 = \frac{5(V_2 - V_1) - 2(V_1) - V_1}{10}$$

$$12 = \frac{5V_2 - 5V_1 - 2V_1 - V_1}{10}$$

$$12 = \frac{5V_2 - 8V_1}{10}$$

$$5V_2 - 8V_1 = 120 \quad \text{--- (1)}$$

at node  $V_2$

$$I_1 + I_2 = I_3 + I_4$$

$$12 + 6 = \frac{V_2 - V_1}{2} + \left( \frac{V_2 - 0}{4} \right)$$

$$18 = \frac{V_2 - V_1}{2} + \frac{V_2}{4}$$

$$18 = \frac{2(V_2 - V_1) + V_2}{4} = \frac{2V_2 - 2V_1 + V_2}{4}$$

$$18 = \frac{3V_2 - 2V_1}{4}$$



$$72 = 3V_2 - 2V_1$$

$$3V_2 - 2V_1 = 72$$

Solving Simultaneously

$$5V_2 - 8V_1 = 120$$

$$5V_2 - 2V_1 = 72$$

$$V_1 = 0, V_2 = 24V$$

Current is flowing through the  $8\Omega$  resistor


$$I_3 = \frac{V_2 - V_1}{2} = \frac{24 - 0}{2}$$

$$I_3 = 12A$$

Current flowing through the  $4\Omega$  resistor

$$I_4 = \frac{V_2 - 0}{4} = \frac{24 - 0}{4} = 6A$$

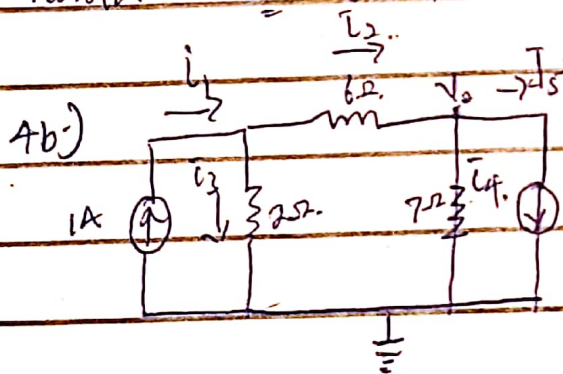Since voltage at node  $V_1 = 0$ , hence current flowing through  $5\Omega$  and  $10\Omega$  resistor = 0 ( $I_5 = I_6 = 0$ )



$$I_1 = 1 \text{ Amps}$$

$$I_5 = 4 \text{ Amps}$$

at node  $V_1$ :

$$I_1 = I_2 + I_3$$

$$1 = \left[ \frac{V_1 - V_2}{6} \right] + \left[ \frac{V_1 - 0}{2} \right]$$

$$1 = V_1 - V_2/6 + V_1/2$$

$$1 = \frac{V_1 - V_2 + 3V_1}{6}$$



$$4V_1 - V_2 = 6 \quad \dots \quad (1)$$

at node  $V_2$ :

$$\bar{V}_2 = 14 + i5.$$

$$\left[ \frac{V_1 - V_2}{6} \right] = \left[ \frac{V_2 - 0}{7} \right] + 1.$$

$$\frac{V_1 + V_2}{6} = \frac{V_2}{7} = 4$$

$$\frac{7(V_1 - V_2) - 6V_2}{42} = 4$$

$$7V_1 - 7V_2 - 6V_2 = 168$$

solving simultaneously

$$4V_1 - V_2 = 6.$$

$$7V_1 - 13V_2 = 168$$

$$V_1 = -24$$

$$V_2 = -144$$

Current flowing through the  $6\Omega$  resistor


$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-4)}{6}$$

$$\bar{V}_2 = \frac{12}{6} = 2A//.$$

Current flowing through the  $2\Omega$  resistor

$$\bar{V}_3 = \frac{V_1 - 0}{2} = \frac{-2}{2} = -1A//$$
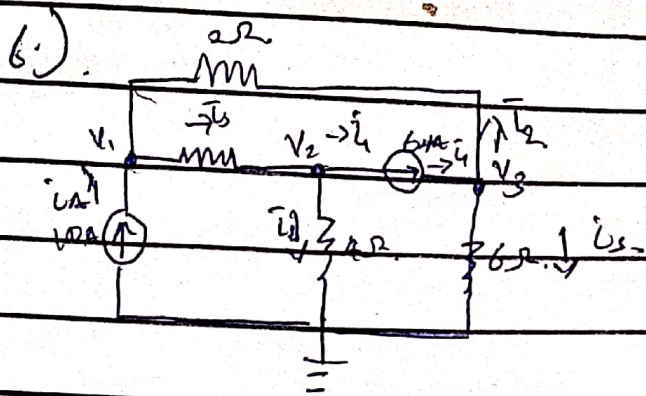
$$\text{Current flowing through the } 7\Omega \text{ resistor } \bar{V}_4 = \frac{V_2 - 0}{7} = -14, \bar{V}_4 = -2A//$$



$$\bar{I}_1 = 6 \text{ Amps.}$$

$$\bar{I}_4 = 10 \text{ Amps.}$$

at node  $V_1$

$$\bar{I}_2 + \bar{I}_4 = \bar{I}_5$$

$$\therefore \frac{V_3 - V_1}{2} + 10 = \left[ \frac{V_1 - V_2}{3} \right]$$

$$10 = \left[ \frac{V_1 - V_2}{3} - \frac{V_3 - V_1}{2} \right]$$

$$60 = \frac{2(V_1 - V_2) - 3(V_3 - V_1)}{6}$$

$$60 = \frac{3V_1 - 2V_2 - 3V_3 + 3V_1}{6}$$

$$60 = 5V_1 - 2V_2 - 3V_3$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \dots \quad (1)$$

at node  $V_2$

$$\bar{I}_5 = \bar{I}_1 + \bar{I}_2$$

$$\frac{V_1 - V_2}{3} = 6 + \left[ \frac{V_2 - V_3}{4} \right]$$

$$6 = \frac{V_1 - V_2}{3} - \frac{V_2 - V_3}{4}$$

$$64 = \frac{4(V_1 - V_2) - 3(V_2 - V_3)}{12}$$

$$768 = 4V_1 - 7V_2 \quad \dots \quad \text{eqn (2)}$$



at node ~~2~~ 3

$$i_2 = i_2 + i_3$$

$$64 = \left[ \frac{V_3 - V_1}{2} \right] + \left[ \frac{V_3 - 0}{6} \right]$$

$$64 = \frac{V_3 - V_1}{2} + \frac{V_3}{6}$$

$$64 = \frac{3(V_3 - V_1) + V_3}{6}$$

$$64 = \frac{3V_3 - 3V_1 + V_3}{6} = \frac{4V_3 - 3V_1}{6}$$

$$384 = -3V_1 + 4V_3$$
$$= -3V_1 + 4V_3 = 384$$

Solving Simultaneously

$$5V_1 - 2V_2 - 3V_3 = 60$$

$$4V_1 - 7V_2 + 0 = 768$$

$$-3V_1 + 0 + 4V_3 = 384$$

$$V_1 = 80V, V_2 = -64V, V_3 = 156V.$$