
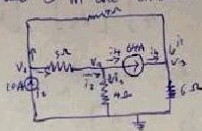


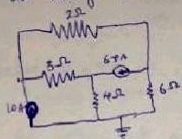1) Find the voltage at nodes 1, 2 and 3 in the circuit below



At node 1, KCL:

$$10 = i_1 + i_2 = 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{3}$$

$$\Rightarrow 60 = 3(V_1 - V_2) + 2(V_1 - V_3)$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_3$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad (i)$$

At node 2, KCL:

$$i_2 = i_3 + 6A$$

$$6A = i_2 - i_3$$

$$6A = \frac{V_1 - V_2}{5} - \frac{V_2 - V_3}{4}$$

$$768 = 4(V_1 - V_2) - 5(V_2 - V_3)$$

$$768 = 4V_1 - 4V_2 - 5V_2 + 5V_3$$

$$768 = 4V_1 - 9V_2 + 5V_3 \quad (ii)$$

At node 3, KCL:

$$6A + i_1 = 10$$

$$6A = 10 - i_1$$

$$6A = \frac{V_2 - 0}{6} - \frac{V_1 - V_2}{2}$$

$$384 = V_2 - 3(V_1 - V_2)$$

$$384 = -3V_1 + 4V_2 \quad (iii)$$

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \dots (i)$$

$$4V_1 - 7V_2 = 768 \dots (ii)$$

$$-3V_1 + 4V_3 = 384 \dots (iii)$$

In Matrix Representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 5(-28-0) + 2(16+0) - 3(0-21) \\ &= -140 + 32 + 63 \\ &= -45 \end{aligned}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 60(-28-0) - 768(-4-0) + 384(0-21) \\ &= -1680 + 3144 - 8064 \\ &= -3600 \end{aligned}$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45} = 80$$

$$\text{For } V_2: \Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$\begin{aligned} &= 5((768 \times 4) - 0) - 4((60 \times 4) - (384 \times 3)) - 3(0 - (768 \times 4)) \\ &= 2880 \end{aligned}$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45} = -64$$

$$\text{For } V_0 \begin{vmatrix} 5 & -2 & 00 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$


$$= 5((-7 \times 384) - 0) - 4((-2 \times 384) - 0) - 3((-2 \times 768) - (-7 \times 00))$$

$$= -7020$$

$$\therefore V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-468} = 15 \text{ V}$$

Therefore, $V_1 = 80 \text{ V}$, $V_2 = -64 \text{ V}$, $V_3 = 15 \text{ V}$

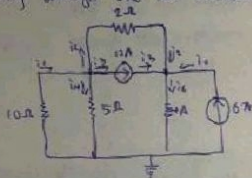- 2 Find the voltages at nodes 1 and 2 and determine the currents flowing through the four resistors in the circuit below



At Node 1, KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - V_0}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots (i)$$

At Node 2

$$i_2 = i_3 + i_4$$

$$\frac{V_2 - 0}{4} = 12 + \frac{V_1 - V_2}{2} + 6$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \dots (ii)$$

Using elimination method

From eqn (i)

$$120 = -8V_1 + 5V_2 \dots (i) \quad x - 4$$

$$144 = -4V_1 + 6V_2 \dots (ii) \quad x - 8$$

$$-480 = 32V_1 - 20V_2 \dots (iii)$$

$$-1152 = 32V_1 - 48V_2 \dots (iv)$$

Subtract eqn (iii) from (iv)

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{-672}{-28}$$

$$V_2 = 24V$$

Subs $V_2 = 24$ in eqn (i)

$$144 = -4V_1 + 6V_2$$

$$V_1 = \frac{144 - 6V_2}{-4}$$


$$V_1 = \frac{144 - 6V_2}{-4}$$

$$V_1 = 0$$

$$\therefore V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 0A, i_4 = -12A$$

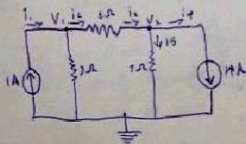ii obtain v_1 and v_2 and the currents through the resistors for the circuit in example (i) if the 2A current source was replaced by a 1A current source.



At Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{7}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \dots (i)$$

At Node 2

$$i_2 = i_4 + i_3$$

$$\frac{V_1 - V_2}{6} = 1 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \dots (ii)$$

From eqn (1),

$$V_2 = 4V_1 - 6$$

Substitute $V_2 = 4V_1 - 6$ in eqn (2)

$$16V_1 = 7V_1 - 13(4V_1 - 6)$$

$$16V_1 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45}$$

$$V_1 = -2V$$

Substitute $V_1 = -2$ in eqn (1)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$

$$\therefore V_1 = -2V, V_2 = -14V$$


Current through the resistors

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = 2A$$

$$i_5 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$

$$i_3 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$

3)

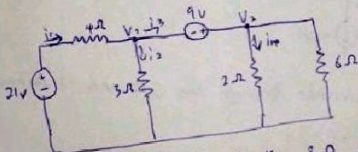

Find the current through the 3Ω and 2Ω resistors

Using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 2}{4} - \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \dots (i)$$

Using KVL for Loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \dots (ii)$$

$$7V_1 + 5V_2 = 63 \quad \dots (i)$$

$$-V_1 + V_2 = 9 \quad \dots (ii)$$

(i) let $V_2 = 9 + V_1$

Substitute $V_2 = 9 + V_1$ in eqn (i)

$$7V_1 + 5(9 + V_1) = 63$$

$$7V_1 + 45 + 5V_1 = 63$$

$$12V_1 = 18$$

$$V_1 = 1.5 \text{ V}$$

Substitute $V_1 = 1.5$ in eqn (ii)

$$-1.5 + V_2 = 9$$

$$V_2 = 10.5 \text{ V}$$

$$V_2 = 10.5 \text{ V}$$

$$\therefore V_1 = 1.5 \text{ V and } V_2 = 10.5 \text{ V}$$


Current through the 3Ω resistor

$$i_2 = \frac{V_1}{3} = \frac{1.5}{3} = 0.5 \text{ A}$$

Current through the 2Ω resistor

$$i_1 = \frac{V_2}{2} = \frac{10.5}{2} = 5.25 \text{ A}$$

H

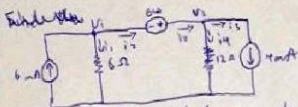

Find the node voltages and the currents through the 6Ω and 12Ω resistor

$$\text{Let's assume } V_1 - V_2 = 6 \text{ V} = i_2$$

At node 1, using KCL

$$6 \text{ mA} = i_1 + i_2$$

$$6 \text{ mA} = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \dots (i)$$

At Node 2

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4 \text{ mA} + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \dots (ii)$$

Solving V_1 and V_2 simultaneously, we have

$$V_1 = 9.5V \text{ and } V_2 = 5.1V$$

∴ current through the 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

$$i_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4A$$

Current through the 12Ω resistor

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A$$

$$\therefore V_1 = 9.5V, V_2 = 5.1V$$

$$i_1 = 1.58A, i_4 = 0.43A$$