


ASITA OBONISO

17/ENG06/014

MECHATRONICS ENGINEERING

CIRCUIT THEORY

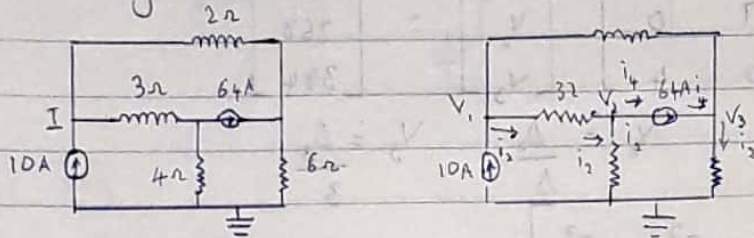1. Find the voltages at node 1, 2 and 3 in the circuit below



Nodal KCL

$$10 = i_1 + i_2$$

$$\Rightarrow 10 = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{3}$$

$$60 = 3(V_1 - V_2) + 2(V_1 - V_2) \quad [\text{multiplying through by 6}]$$

$$60 = 3V_1 - 3V_2 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 3V_2 - 2V_2 \quad \longrightarrow 1$$

At Node 2 KCL

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$\Rightarrow 64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0) \quad [\text{multiplying through by 12}]$$

$$768 = 4V_1 - 4V_2 - 3V_2 - 0$$

$$768 = 4V_1 - 7V_2 \quad \longrightarrow 2$$

Node 3 KCL

$$64 + i_1 = i_5$$

$$64 = i_5 - i_4$$

$$\Rightarrow 64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = (V_3 - 0) - 3(V_1 - V_3) \quad [\text{multiplying through by 6}]$$

$$384 = V_3 - 3V_1 + 3V_3$$

$$384 = -3V_1 + 4V_3 \quad \longrightarrow 3$$

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \longrightarrow 1$$

$$4V_1 - 7V_2 + 0V_3 = 768 \quad \longrightarrow 2$$

$$-3V_1 + 0V_2 + 4V_3 = 384 \longrightarrow 3$$

Matrix Representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$= 60(-28-0) - 768(-8-0) - 384(0-21)$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$V_1 = \frac{-3600}{-45} = 80V$$

$$\Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5(3072-0) - 4(240 - \frac{384}{-158}) - 3(0 - \frac{765}{-384})$$

$$= 2880$$

$$V_2 = \frac{2880}{-45} = -64V$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$= 5[3072-0] - 4[240-384] - 3[0-765]$$

$$= 2880$$

$$= 2880$$

$$-45 \times -64V$$


$$= 5(-2688-0) - 4(-768-0) - 3(-1536 - -420)$$

$$= -7020$$

$$V_3 = \frac{-7020}{-45} = 156V$$

$$-45 = 156V$$

2

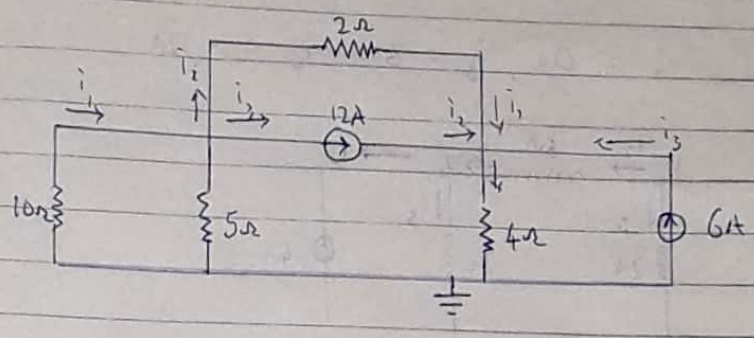

Node 1 KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{V_1 - 0}{10} = \frac{V_1 - V_2}{5} + 12 + \frac{V_1 - V_2}{2}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \longrightarrow 1$$

Node 2

$$i_3 + i_2 + i_5 = i_6$$

$$12 + \frac{V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \longrightarrow 2$$

Using elimination method

$$120 = -8V_1 + 5V_2 \longrightarrow 1 \times 4$$

$$144 = -4V_1 + 6V_2 \longrightarrow 2 \times 8$$

$$-480 = 32V_1 - 20V_2 \longrightarrow 3$$

$$-1152 = 32V_1 - 48V_2 \longrightarrow 4$$

$$-672 = 0 - 28V_2$$

$$V_2 = \frac{672}{28}$$

$$24 = 24V$$

Substitute "V₂ = 24" in eqn 2


$$144 = -4V_1 + 6(24)$$

$$144 = -4V_1 + 144$$

$$V_1 = \frac{144 - 144}{-4} = 0$$

$$i_1 = 0A, \quad i_2 = 0A, \quad i_3 = 6A, \quad i_4 = -12A$$

3

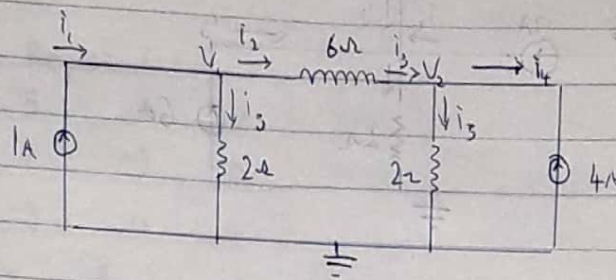

Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$6 = 4V_1 - V_2 \quad \rightarrow 1$$

Node 2

$$i_2 = i_4 + i_3$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{2}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \rightarrow 2$$

From eqn 1

$$V_2 = 4V_1 - 6$$

Substitute " $V_2 = 4V_1 - 6$ " into eqn 2

$$168 = 7V_1 - 13[4V_1 - 6]$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45} = -2V$$

Substitute " $V_1 = -2$ " in eqn 1

$$6 = 4[-2] - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$V_1 = -2V \quad \& \quad V_2 = -14V$$

Current through the resistor

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_2 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
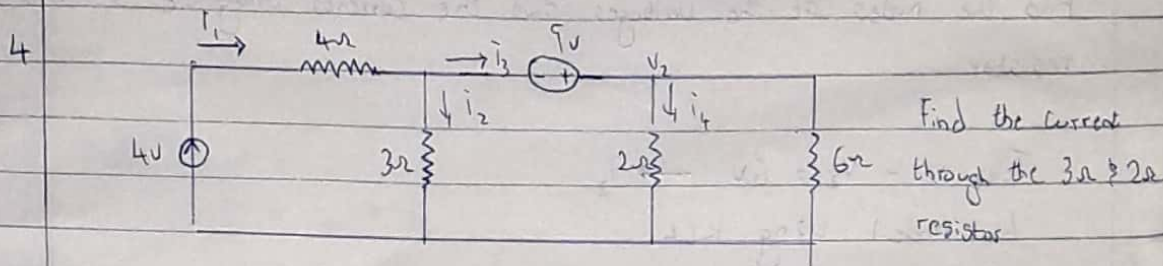
$$i_3 = \frac{V_1}{7} = \frac{-14}{7} = -2A$$



Using KCL at Node

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2} = 0$$

$$7V_1 + 8V_2 - 63 = 0 \quad \longrightarrow 1$$

taking KVL for loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \longrightarrow 2$$

From eqn 2

$$V_2 = 9 + V_1$$

Substitute " $V_2 = 9 + V_1$ " in eqn 1

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = 63 - 72$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

Substitute " $V_1 = -0.6$ " in eqn 1

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$


$$V_2 = 9 - 0.6 = 8.4V$$

Current through 3Ω & 2Ω

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A \quad \text{at } 3\Omega$$

$$i_4 = \frac{V_2}{2} = \frac{8.4}{2} = 4.2A \quad \text{at } 2\Omega$$

5

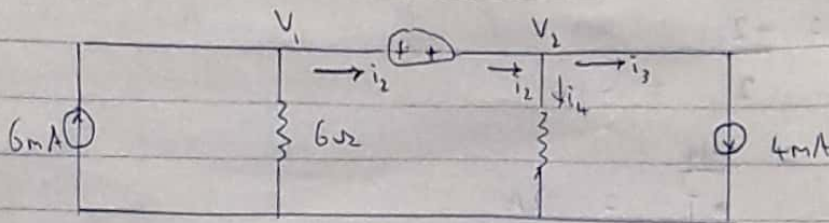

Find the nodes of the voltages and the currents through the 6Ω and 12Ω resistor

$$\text{Take } V_1 - V_2 = 6V \rightarrow i_2$$

At node 1 using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \rightarrow 1$$

At Node 2

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = 4mA + \frac{V_2 - 0}{12}$$

$$12[V_1 - V_2] = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \rightarrow 2$$

Solving V_1 & V_2 simultaneously we have

$$V_1 = 9.5V \text{ \& } V_2 = 5.1V$$

Current through the 6Ω resistor

$$i_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58A$$

$$i_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4mA$$

Current through i_2

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43A$$

$$V_1 = 9.5V$$

$$V_2 = 5.1V$$

$$i_1 = 1.58A$$

$$i_4 = 0.43A$$