
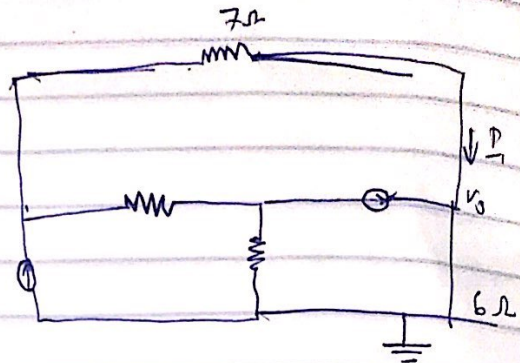


ORPALA Christopher  
 171ENG021068  
 Computer Engineering

EEB322

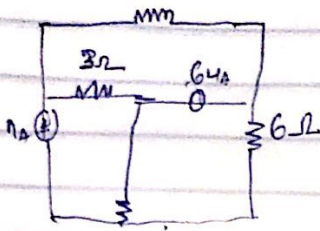1. find the voltages of nodes 1, 2 & 3 in the circuit below



At node 1, KCL:

$$10 - I_1 + I_2 \rightarrow 10 \cdot \frac{V_1 - V_2}{3} + \frac{V_1 - V_2}{3}$$

$$\rightarrow 60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \dots (i)$$

At node 2, KCL

$$I_2 = I_3 + I_4$$

$$64 = I_2 - I_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3[V_2 - 0]$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \dots (ii)$$

At Node 3, KCL

$$I_4 + I_1 = I_5$$

$$64 = I_3 - I_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_1 - V_3}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = 3V_1 + 4V_3 \dots (iii)$$

Using Cramer's Rule

$$5v_1 - 2v_2 - 3v_3 = 60 \quad \dots (i)$$

$$4v_1 - 7v_2 = 768 \quad \dots (ii)$$

$$-3v_1 + 4v_3 = 384 \quad \dots (iii)$$

In matrix representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$v_1 = \frac{\Delta_1}{\Delta}, \quad v_2 = \frac{\Delta_2}{\Delta}, \quad v_3 = \frac{\Delta_3}{\Delta}$$

where  $\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 6 & 4 \end{vmatrix}$

$$= 5(-28 - 0) + 2(16 + 0) - 3(6 - 21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix} = 60(-28 - 0) - 768(-28 - 0) + 384(6 - 21)$$

$$= -1680 + 21504 - 8064$$

$$= 11640$$

$$\therefore v_1 = \frac{\Delta_1}{\Delta} = \frac{11640}{-45} = -258.67$$

$$v_2 = \frac{\Delta_2}{\Delta} = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5[(768 + 4) - 0] - 4(160 + 4) - 3(384 - 3)$$

$$= 7880$$





At node 2

$$I_1 + I_2 + I_3 = I_4$$

$$I_2 = \frac{V_1 - V_2}{2} = 0 = \frac{V_2 - 0}{4}$$

$$16 + 4(V_1 - V_2) + 4V_2 = 2(V_2)$$

$$16 + 4V_1 - 4V_2 + 4V_2 = 2V_2$$

$$16 + 4V_1 - 4V_2 = 2V_2 \quad \dots (1)$$

Using elimination method

$$12 \cdot 0 = -8V_1 + 5V_2 \quad \dots (1) \quad + \cdot 4$$

$$16 + 4V_1 - 4V_2 = 2V_2 \quad \dots (1) \quad + \cdot 4$$

$$-48 = 32V_1 - 20V_2 \quad \dots (11)$$

$$-1152 = 32V_1 - 208V_2 \quad \dots (12)$$

Sub eqn (11) by eqn (12)

$$-672 = 0 - 288V_2$$

$$V_2 = \frac{-672}{-288} \therefore V_2 = 2.33V$$


Sub

$$16 + 4V_1 - 6V_2 = 0$$

$$V_1 = \frac{6V_2 - 16}{4} \quad , \quad V_1 = \frac{16 - 6V_2}{4} \therefore V_1 = 0$$

$$\therefore V_1 = 0V, \quad V_2 = 2.33V, \quad I_1 = 0A, \quad I_2 = 2A, \quad I_3 = 6A, \quad I_4 = -12A$$

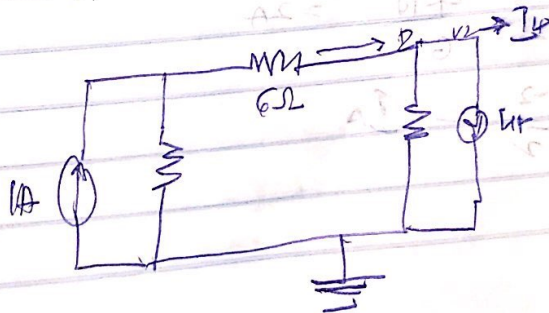(ii) Often  $V_1$  &  $V_2$  are the current through the resistors of the circuit in example (i) if the 3A current source was replaced by 2.1A current source





At node 1

$$I_1 = I_2 + I_3$$

$$I = \frac{V_1 - V_2}{6} + \frac{V_1}{2}$$

$$6 = V_1 - V_2 + 3V_1$$

$$8 = 4V_1 - V_2 \quad \text{--- (1)}$$

At node 2

$$I_2 = I_4 + I_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 28 + 6V_2$$

$$7V_1 - 13V_2 = 28 \quad \text{--- (2)}$$

from eqn (1)  $V_2 = 4V_1 - 8$

Sub  $(4V_1 - 8)$  in eqn (2)

$$7V_1 = 7(4V_1 - 8) + 28$$

$$7V_1 = 28V_1 - 56 + 28$$

$$9V_1 = -28$$

$$V_1 = \frac{-28}{9}$$

$$V_1 = -20$$

Sub  $-20$  in eqn (1)

$$8 = 4(-20) - V_2$$

$$8 = -8 - V_2$$

$$V_2 = -16$$


Current  $I = \frac{V_1 - V_2}{6} = \frac{-20 - (-16)}{6} = \frac{-4}{6} = -\frac{2}{3} \text{ A}$

current through the resistors

$$I_2 = \frac{V_1 - V_2}{6} = \frac{-20 - (-16)}{6} = -\frac{4}{6} = -\frac{2}{3} \text{ A}$$

$$I_5 = \frac{V_1}{2} = \frac{-20}{2} = -10 \text{ A}$$
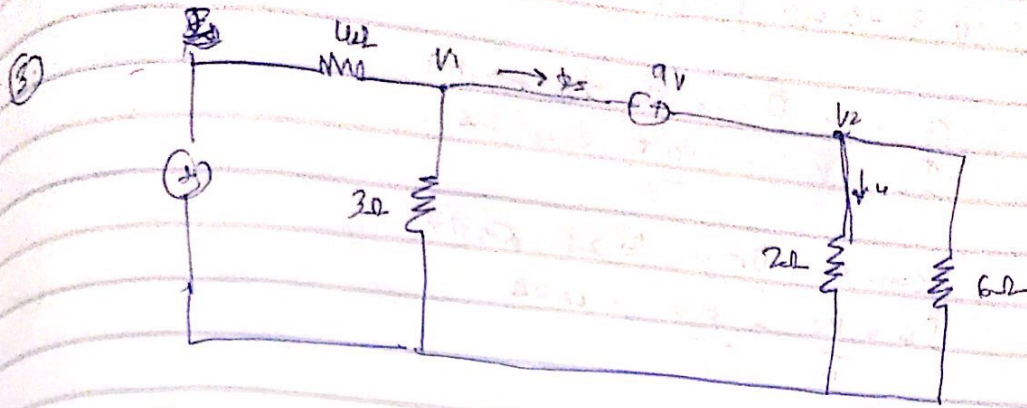
$$I_s = \frac{V_2}{4} = \frac{-16}{7} = -2A$$



Find the current through the 3Ω and 2Ω resistors

Using KCL at node 1

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{V_1 - 9}{3} - \frac{V_1}{2} + \frac{V_1}{6} + \frac{V_2}{4} = 0$$

$$7V_1 + 8V_2 - 18 = 0 \quad \text{--- (1)}$$

Using KVL for loop 1

$$-V_1 - 9 + V_2 = 0 \quad \text{--- (2)}$$

$$7V_1 + 8V_2 = 18 \quad \text{--- (1)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (2)}$$

$$\text{--- (1) } \times 1 \quad V_2 = 9 + V_1$$

Sub  $V_2 = 9 + V_1$  in eqn (1)

$$7V_1 + 8(9 + V_1) = 18$$

$$7V_1 + 72 + 8V_1 = 18$$

$$15V_1 = -54$$

$$V_1 = -3.6V$$

Sub in --- (2) in eqn (2)

$$-(-3.6) + V_2 = 9$$

$$3.6 + V_2 = 9$$



$$V_2 = r \cdot u$$


$$\therefore V_1 = -0.6V \text{ \& } V_2 = r \cdot u$$

Current through the  $3\Omega$  resistor

$$I_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the  $2\Omega$  resistor
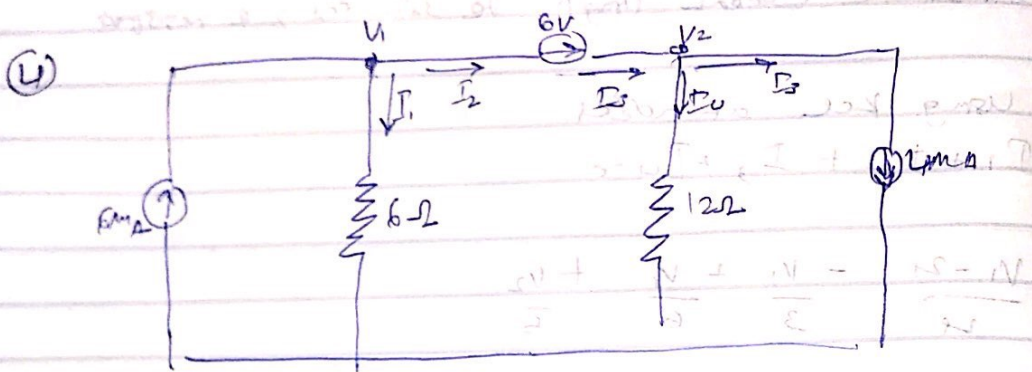
$$I_4 = \frac{V_2}{4} = \frac{r \cdot u}{4} = 4.2A$$



Find the node voltages and the current through the  $6\Omega$  &  $12\Omega$  resistor (lets assume both  $v_1 - v_2 = 6V \rightarrow$ )

As Node 1 using KCL

$$6mA = I_1 - I_2$$

$$6mA = \frac{v_1 - 0}{6} - (v_1 - v_2)$$

$$36 = v_1 - 6(v_1 - v_2)$$

$$36 = v_1 + 6v_1 - 6v_2 = (7v_1 - 6v_2)$$

$$36 = 7v_1 - 6v_2 \quad (1)$$

As Node 2

$$I_2 - I_3 + I_4 = 0$$

$$V_1 - V_2 = 6mA + \frac{V_2}{4} = 0$$

$$12(V_1 - V_2) = 48I - V_2$$

$$48I = 12V_1 - V_2 - V_2$$

$$48I = 12V_1 - 2V_2 \quad \text{--- (1)}$$

Solving  $V_1$  &  $V_2$  simultaneously, we have  
 $V_1 = 9.5 \text{ V}$  &  $V_2 = 5.1 \text{ V}$

$\therefore$  current through the  $6 \Omega$  resistor

$$I_1 = \frac{V_1}{6} = \frac{9.5}{6} = 1.58 \text{ A} \quad I_2 = 4 \text{ V} \quad V_L = 4.5 - 5$$

$$I_2 = 0 \text{ A}$$

current through the  $11 \Omega$  resistor

$$I_3 = \frac{V_2}{11} = \frac{5.1}{11} = 0.46 \text{ A}$$

$$V_1 = 9.5 \text{ V} \quad \therefore V_2 = 5.1 \text{ V}$$

$$I_1 = 1.58 \text{ A} \quad \therefore I_2 = 0 \text{ A}$$