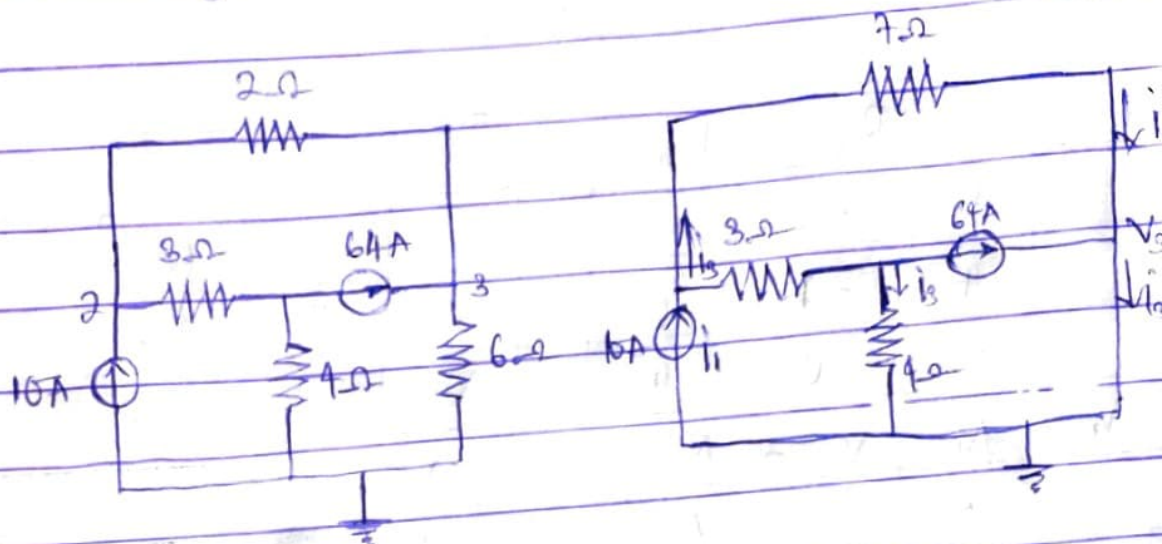


# ENG 322 Assignment

① Find the voltages at nodes 1, 2 and 3 in the circuit below



At nodes 1, KCL;

$$10 = i_1 + i_2 \Rightarrow 10 = \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{3}$$

$$\Rightarrow 60 = 3(V_1 - V_3) + 2(V_1 - V_2)$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 2V_2 - 3V_3 \quad \text{--- (i)}$$

At Node 2, KCL;

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

$$768 = 4(V_1 - V_2) - 3(V_2 - 0)$$

$$768 = 4V_1 - 4V_2 - 3V_2$$

$$768 = 4V_1 - 7V_2 \quad \text{--- (ii)}$$

At node 3, KCL;

$$64 + i_1 = i_5$$

$$64 = i_5 - i_1$$

$$64 = \frac{V_3 - 0}{6} - \frac{V_3 - V_2}{2}$$

$$384 = V_3 - 3(V_1 - V_3)$$

$$384 = -3V_1 + 4V_3 \quad \text{--- (iii)}$$

Using Cramer's Rule

$$5V_1 - 2V_2 - 3V_3 = 60 \quad \text{--- (i)}$$

$$4V_1 - 7V_2 = 768 \quad \text{--- (ii)}$$

$$-3V_1 + 4V_3 = 384 \quad \text{--- (iii)}$$

La Matrix Representation

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}$$

$$\text{where } \Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5(-280) + 2(16+0) - 3(0-21)$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\begin{aligned} \Delta_1 &= + \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix} = 60(-28-0) - 768(-8-0) - 384(0-21) \\ &= -1680 + 6144 - 8064 \\ &= -3600 \end{aligned}$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45}$$

$$= 80V$$

$$\text{For } V_2: \Delta_2 = + \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$= 5((768 \times 4) - 0) - 4((60 \times 4) - (384 \times 3)) - 3(0 - (768 \times 3))$$

$$= 2880$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{2880}{-45}$$

$$= -64V$$

For $V_3$ ;	+	5	-2	60
	-	4	-7	768
	+	-3	0	384

$$= 5(-7 \times 384 - 0) - 4(-2 \times 384 - 0) - 3(-2 \times 768)(-7 \times 60)$$


$$= -7020$$

$$\therefore V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$\Delta = -45 = 156V$$

$$\text{Hence } V_1 = 80V, V_2 = -64V, V_3 = 156V$$

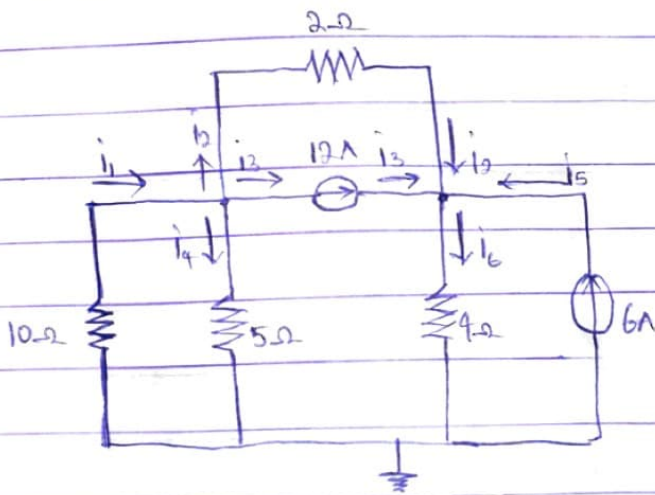Find the voltages at node 1 and 2 and determine the currents flowing through the four resistors in the circuit below



At Node 1, KCL

$$i_1 = i_2 + i_3 + i_4$$

$$V_2 - V_1 = V_1 - V_2 + 12 + V_1 - V_2$$

$$10 \quad \quad \quad 2 \quad \quad \quad 5$$

$$10 - V_1 = 5(V_1 - V_2) + 12 + 2(V_1 - 0)$$

$$-V_1 = 5V_1 - 5V_2 + 12 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots (1)$$

At nodes 2

$$i_3 + i_2 + i_5 = i_6$$

$$i_2 + V_1 - V_2 + 6 = V_2 - 0$$

$$2 \quad \quad \quad 4$$

$$96 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 = -4V_1 + 6V_2 \quad \dots (ii)$$

Using elimination method

$$120 = -8V_1 + 5V_2 \quad \dots (i) \times 9$$

$$144 = -4V_1 + 6V_2 \quad \dots (ii) \times 8$$

$$-980 = 32V_1 - 20V_2 \quad \dots (iii)$$

$$-1152 = 32V_1 - 48V_2 \quad \dots (iv)$$

Subtract eqn (iii) from (iv)

$$-672 = 0 = -28V_2$$

$$V_2 = -672$$

$$-28$$

$$V_2 = 24V$$

Subs  $V_2 = 24$  in eqn (ii)

$$144 = -4V_1 + 6V_2$$

$$V_1 = 144 - 6V_2$$

$$-4$$

$$V_1 = 144 - 6V_2$$


$$-4$$

$$V_1 = 0$$

$$\therefore V_1 = 0V, V_2 = 24V$$

$$i_1 = 0A, i_2 = 0A, i_3 = 6A, i_4 = 12A.$$

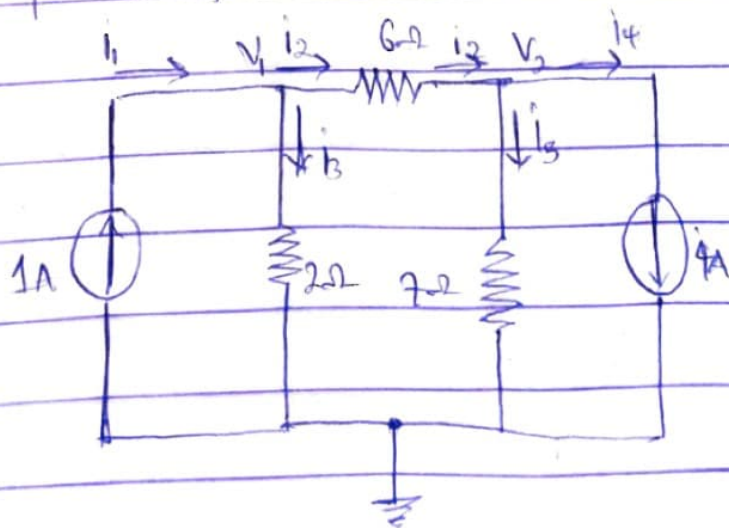Obtain  $V_1$  and  $V_2$  and the currents through the resistors for the circuit example (ii) if the 2A current source was replaced by a 1A current source.



At Node 1

$$i_1 = i_2 + i_3$$

$$1 = \frac{V_1 - V_2}{6} + \frac{V_2}{2}$$

$$6 = V_1 - V_2 + 3V_2$$

$$6 = 4V_1 - V_2 \quad \text{--- (C)}$$

At Node 2

$$i_2 = i_4 + i_5$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{7}$$

$$7(V_1 - V_2) = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \text{--- (D)}$$

From eqn (C)  $V_2 = 4V_1 - 6$

Subs  $V_2 = 4V_1 - 6$  in eqn (D)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = \frac{90}{-45}$$

$$V_1 = -2V$$

Subs  $V_1 = -2$  in eqn (C)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$-V_2 = 6 + 8$$

$$-V_2 = 14$$

$$V_2 = -14$$


$$V_1 = -2V, V_2 = -14V$$

Current through the resistors

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 - (-14)}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
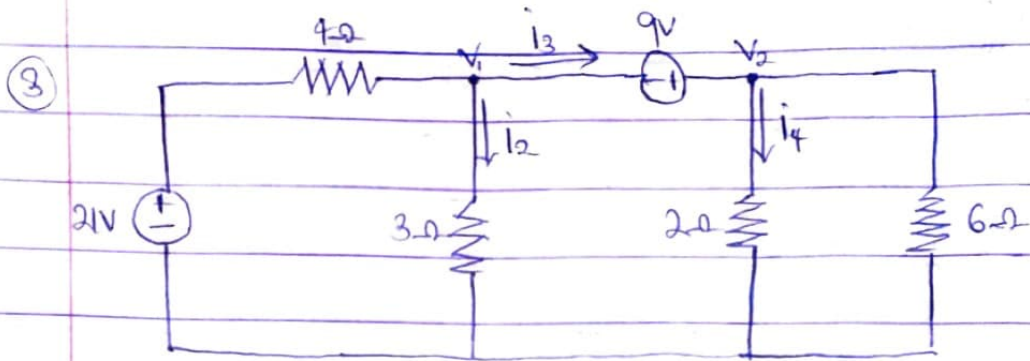
$$i_5 = \frac{V_2}{7} = \frac{-14}{7} = -2A$$



Find the current through the 3Ω and 2Ω resistors

Using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2}$$

$$7V_1 + 8V_2 - 63 = 0 \quad \text{--- (i)}$$

Using KVL for Loop 1

$$-V_1 - 9 + V_2 = 0$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

$$7V_1 + 8V_2 = 63 \quad \text{--- (i)}$$

$$-V_1 + V_2 = 9 \quad \text{--- (ii)}$$

from (ii) let  $V_2 = 9 + V_1$

Substitute  $V_2 = 9 + V_1$  in eqn (i)

$$7V_1 + 8(9 + V_1) = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = -9$$

$$V_1 = -0.6V$$

Substitute  $V_1 = -0.6$  in eqn (ii)

$$-(-0.6) + V_2 = 9$$

$$0.6 + V_2 = 9$$

$$V_2 = 8.4V$$


$$\therefore V_1 = -0.6V \text{ and } V_2 = 8.4V$$

Current through the  $3\Omega$  resistor

$$i_2 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A$$

Current through the  $2\Omega$  resistor
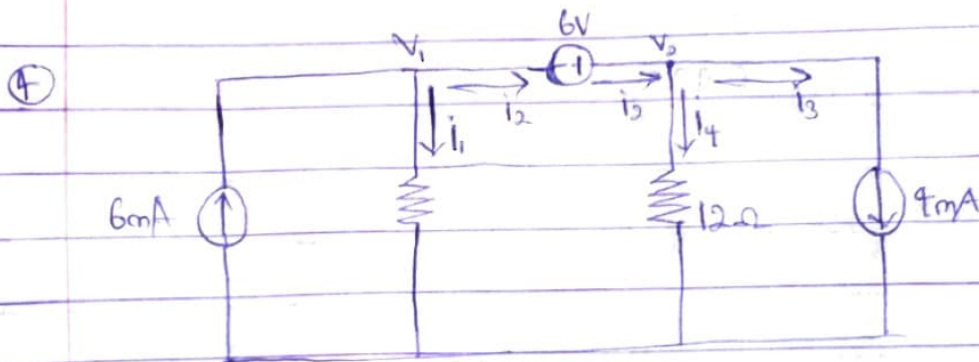
$$i_4 = \frac{V_2}{2} = \frac{8.4}{2} = 4.2A$$



Find the node voltages and the currents through the  $6\Omega$  and  $12\Omega$  resistors

Let's assume that  $V_1 = V_2 = 6V \Rightarrow i_2$

At node 1, using KCL

$$6mA = i_1 + i_2$$

$$6mA = \frac{V_1 - 0}{6} + (V_1 - V_2)$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \dots (i)$$

At node 2:

$$i_2 = i_3 + i_4$$

$$V_1 - V_2 = \frac{4mA}{12} + \frac{V_2 - 0}{12}$$

$$12(V_1 - V_2) = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2$$

$$48 = 12V_1 - 13V_2 \quad \dots (ii)$$

Solving  $V_1$  and  $V_2$  simultaneously, we have  $V_1 = 9.5V$  and  $V_2 = 5.1V$ .

∴ Current through the 6Ω resistor

$$i_1 = V_1/6 = 9.5/6 = 1.58\text{A}; \quad i_2 = V_1 - V_2 = 9.5 - 5.1 = 4.4\text{A}$$

Current through the 12Ω resistor

$$i_4 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43\text{A}$$

$$\therefore V_1 = 9.5\text{V}; \quad V_2 = 5.1\text{V}$$

$$i_1 = 1.58\text{A}; \quad i_4 = \underline{\underline{0.43\text{A}}}$$