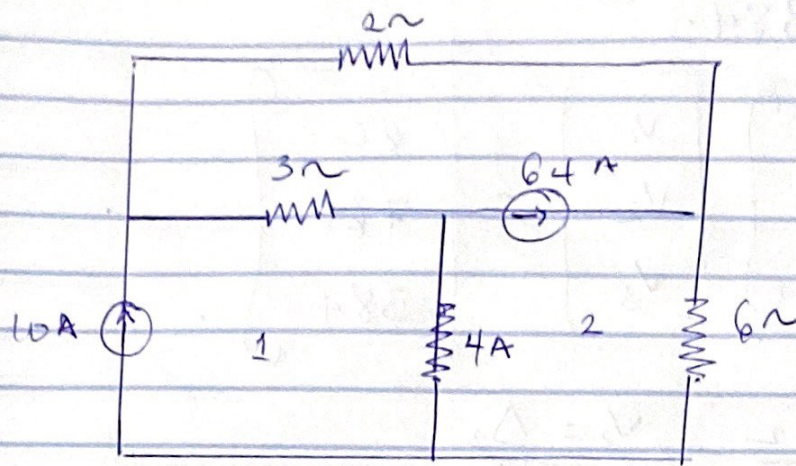


Bakare Sharafdeen omogbolahan.

171 Eng 04/014

EEE 322 CIRCUIT THEORY II

ELECTROELECT.



At node 1, KCL

$$10 = i_1 + i_2 = \frac{v_1 - v_3}{2} + \frac{v_1 - v_2}{3}$$

$$60 = 2(v_1 - v_2) + 3(v_1 - v_3)$$

$$60 = 5v_1 - 2v_2 - 3v_3 \quad \text{--- (i)}$$

At node 2, KCL

$$i_2 = i_3 + 64$$

$$64 = i_2 - i_3$$

$$64 = \frac{v_1 - v_2}{3} - \left(\frac{v_2 - 0}{4} \right)$$

$$768 = 4(v_1 - v_2) - 3v_2$$

$$768 = 4v_1 - 7v_2 \quad \text{--- (ii)}$$

At Node 3, KCL

$$64 + i_1 = i_3$$

$$64 = i_3 - i_1$$

$$64 = \frac{v_3 - 0}{6} - \frac{(v_1 - v_2)}{2}$$

$$384 = v_3 - 3(v_1 - v_2)$$

$$384 = -3v_1 + 4v_3 \quad \text{--- (iii)}$$

Using Cramer's rule to solve the matrix.

$$5V_1 - 2V_2 - 3V_3 = 60$$

$$4V_1 - 7V_2 = 768$$

$$-3V_1 + 0 + 4V_3 = 384.$$

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}.$$

$$V_1 = \frac{\Delta_1}{\Delta}, \quad V_2 = \frac{\Delta_2}{\Delta}, \quad V_3 = \frac{\Delta_3}{\Delta}.$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$+5 \begin{vmatrix} -7 & 0 \\ 0 & 4 \end{vmatrix} + 2 \begin{vmatrix} 4 & 0 \\ -3 & 4 \end{vmatrix} - 3 \begin{vmatrix} 4 & -7 \\ 3 & 0 \end{vmatrix}.$$

$$5(-28) + 2(16 - 0) - 3(0 + 21)$$

$$\Delta = -45 \cdot 11.$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{vmatrix}$$

$$\Delta_1 = 60 \begin{vmatrix} -7 & 0 \\ 0 & 4 \end{vmatrix} + 2 \begin{vmatrix} 768 & 0 \\ 384 & 4 \end{vmatrix} - 3 \begin{vmatrix} 768 & -7 \\ 384 & 0 \end{vmatrix}$$

$$\Delta_1 = -3600 \cdot 11.$$

$$\Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{vmatrix}$$

$$\Delta_2 = 5 \begin{vmatrix} 768 & 0 \\ 384 & 4 \end{vmatrix} - 60 \begin{vmatrix} 4 & 0 \\ -3 & 4 \end{vmatrix} + 3 \begin{vmatrix} 4 & 768 \\ -3 & 384 \end{vmatrix}$$

$$\Delta_2 = 2800$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{vmatrix}$$

$$\Delta_3 = 5 \begin{vmatrix} -7 & 768 \\ 0 & 384 \end{vmatrix} + 2 \begin{vmatrix} 4 & 768 \\ -3 & 384 \end{vmatrix} + 60 \begin{vmatrix} 4 & -7 \\ -3 & 0 \end{vmatrix}$$


$$\Delta_3 = -7020$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-36000}{-45} = 80V$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{2800}{45} = 64V$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

②

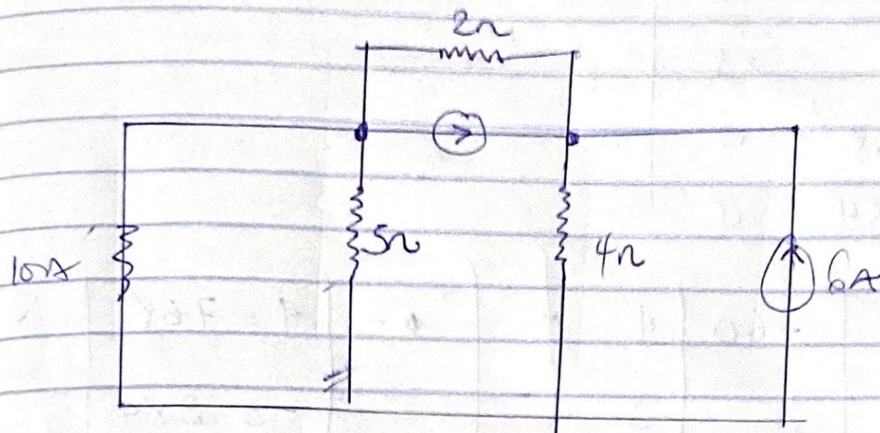

At node 1, using KCL

$$i_1 = i_2 + i_3 + i_4$$

$$\frac{0 - V_1}{10\Omega} = \frac{V_1 - V_2}{2} + 12 + \frac{V_1 - 0}{5}$$

$$-V_1 = 5(V_1 - V_2) + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \text{--- (1)}$$

At node 2

$$i_5 + i_2 + i_3 = i_6$$

$$\frac{12 + V_1 - V_2}{2} + 6 = \frac{V_2 - 0}{4}$$

$$96 + 4(V_1 - V_2) + 48 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \text{--- (2)}$$

$$120 = -8V_1 + 5V_2$$


$$144 = -4V_1 + 6V_2$$

$$V_1 = 0, V_2 = 24V$$

$$i_2 = \frac{V_1 - V_2}{2} = 12A$$

$$i_6 = \frac{V_2 - 0}{4} = \frac{24}{4} = 6A$$
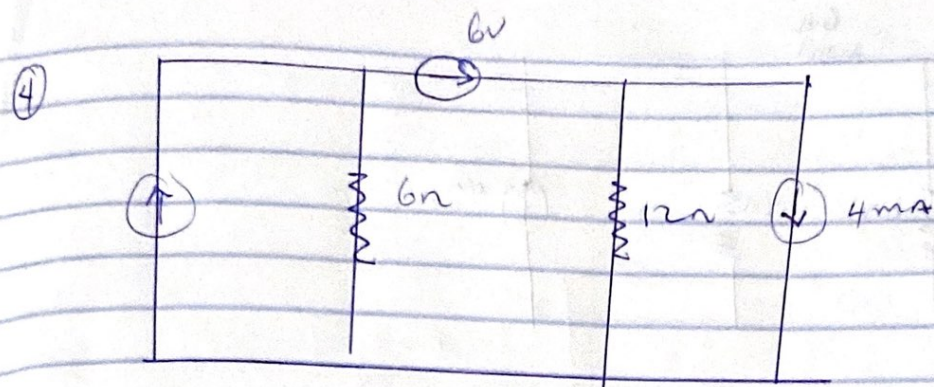
$$i_1 = \frac{0 - V_1}{10} = 0A \quad i_4 = \frac{V_1 - 0}{5} = 0A$$



$$V_1 - V_2 = 6V \quad \text{--- (1)}$$

At node 1

$$6mA = i_1 + i_2$$

$$6 \times 10^{-3} = V_1 / 6 + V_1 - V_2$$

$$36 \times 10^{-3} = V_1 + 6(V_1 - V_2)$$

$$36 \times 10^{-3} = 7V_1 - 6V_2 \quad \text{--- (2)}$$

At node 2

$$i_2 = i_3 + 0.4$$

$$V_1 - V_2 = V_1 / 12 + 4 \times 10^{-3}$$

$$12(V_1 - V_2) = V_2 + (4 \times 10^{-3}) \times 12$$

$$12(V_1 - V_2) = V_2 + 48 \times 10^{-3}$$

$$48 \times 10^{-3} = 12V_1 - 13V_2 \quad \text{--- (3)}$$

Solving V_1 & V_2 simultaneously.

$$V_1 = 0.0095V \quad V_2 = 0.005V$$

$$V_1 = 9.5mV \quad V_2 = 5mV$$

$$i_1 = \frac{V_1}{6} = \frac{9.5 \times 10^{-3}}{6} = 1.583mA //$$

$$i_2 = \frac{V_2}{12} = \frac{5.1 \times 10^{-3}}{12} = 0.425mA //$$