

Claris Databasi Ubanga



17/ENC02009

Computer Engineering

EEE 8

Assignment

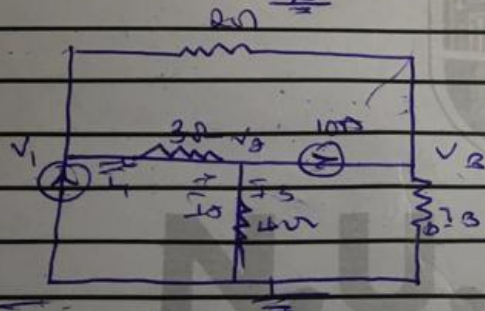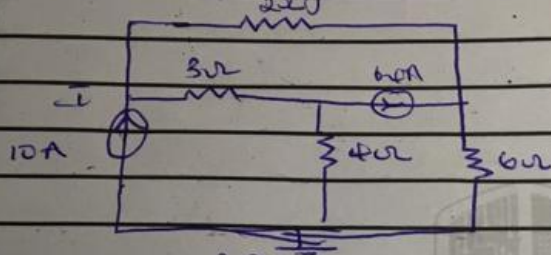Find the voltage at node 1, 2, and 3 in the circuit below



From Node 1

$$10 = i_1 + i_2 \rightarrow 10 = \frac{V_1 - V_3}{3} + \frac{V_1 - V_2}{3}$$

Multiplying through by 3

$$60 = 3[V_1 - V_3] + 2[V_1 - V_2]$$

$$60 = 3V_1 - 3V_3 + 2V_1 - 2V_2$$

$$60 = 5V_1 - 3V_3 - 2V_2 \dots \textcircled{1}$$

From node 2,

$$i_2 = i_3 + 6A$$

$$6A = i_2 - i_3$$

$$6A = \frac{V_1 - V_2}{3} - \frac{V_2 - 0}{4}$$

Multiply through by 4

$$768 = 4(v_1 - v_2) - 3(v_2 - 0)$$

$$768 = 4v_1 - 7v_2 \quad \dots (3)$$

From node 3

$$6A + 2v_4 = 15$$

$$6A = 15 - 2v_4$$

$$6A = v_3 - 0 \quad \frac{-v_4 - v_3}{0}$$

$$384 = v_3 - 3(v_1 - v_3)$$

$$384 = -3v_1 + 4v_3 \quad \dots (7)$$

$$5v_1 - 2v_2 - 3v_3 = 60 \quad \dots (1)$$

$$5v_1 - 7v_2 + 0v_3 = 768 \quad \dots (2)$$

$$-3v_1 + 0v_2 + 4v_3 = 384 \quad \dots (4)$$

In Matrix form

$$\begin{bmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 768 \\ 384 \end{bmatrix}$$

$$v_1 = \frac{\Delta_1}{\Delta} ; v_2 = \frac{\Delta_2}{\Delta} ; v_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 5 & -2 & -3 \\ 4 & -7 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$$= 5[-28-0] + 2[16+0] - 3[0-21]$$

$$= -140 + 32 + 63$$

$$= -45$$

$$\Delta_1 = \begin{bmatrix} 60 & -2 & -3 \\ 768 & -7 & 0 \\ 384 & 0 & 4 \end{bmatrix}$$

$$= 60(-20-0) - 768[-8-0] - 384(0-21)$$

$$= -1680 + 6144 - 8064$$

$$= -3600$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-3600}{-45}$$

$$= 80V$$

$$V_2 = \frac{\Delta_2}{\Delta} = \begin{bmatrix} 5 & 60 & -3 \\ 4 & 768 & 0 \\ -3 & 384 & 4 \end{bmatrix}$$

$$= 5([768 \times 4] - 0) - 4(60 \times 4) - [384 \times 3] - 3[0 - 768 - 3]$$

$$\Rightarrow 2880$$

$$V_2 = \frac{2880}{-45} = -64V$$

$$V_3 = \begin{bmatrix} 5 & -2 & 60 \\ 4 & -7 & 768 \\ -3 & 0 & 384 \end{bmatrix}$$

$$= 5[(-7 \times 384) - 0] - 4[(-2 \times 384) - 0] - 3[(-2 \times 768) - (7 \times 60)]$$

$$\Rightarrow 7020$$


$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-7020}{-45} = 156V$$

$$V_1 = 80V$$

$$V_2 = -64V$$

$$V_3 = 156V$$

Questions

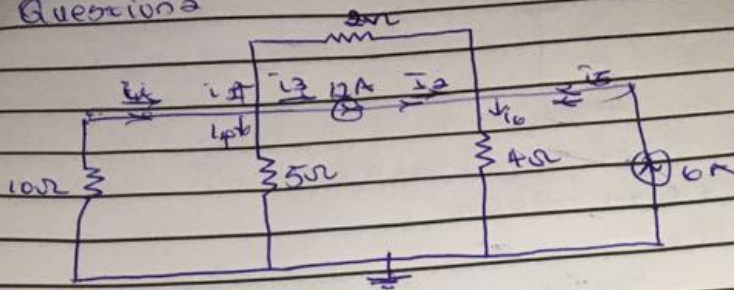

From node 1:

$$i_1 = i_2 + i_3 + 2A$$

$$\frac{V_0 - V_1}{10} = \frac{V_1 - V_2}{5} + 12 + \frac{V_1 - V_0}{5}$$

$$0 - V_1 = 5(V_1 - V_2) + 120 + 2(V_1 - 0)$$

$$\Rightarrow V_1 = 5V_2 - 5V_0 + 120 + 2V_1$$

$$120 = -8V_1 + 5V_2 \quad \dots (1)$$

From Node 2:

$$i_3 + i_4 + 6 = 0$$

$$12 + \frac{V_1 - V_2}{5} + 6 = \frac{V_2 - 0}{4}$$

$$18 + 4(V_1 - V_2) + 48 = 2(V_2)$$

$$144 + 4V_1 - 4V_2 = 2V_2$$

$$144 = -4V_1 + 6V_2 \quad \dots (2)$$

$$120 = -8V_1 + 5V_2 \quad \dots (1) \quad \dots \times 4$$

$$144 = -4V_1 + 6V_2 \quad \dots (2) \quad \dots \times 8$$

$$-480 = 32V_1 - 20V_2$$

$$-1152 = 32V_1 - 48V_2$$

$$-672 = 28V_2$$

$$v_2 = \frac{-672}{-28}$$

$$v_2 = 24V$$

Equating ($v_2 = 24V$) into eqn (c)

$$144 = -4v_1 + 6v_2$$

$$v_1 \Rightarrow \frac{144 - 6(24)}{-4}$$

$$v_1 = \frac{144 - 144}{-4}$$

$$\Rightarrow 0V$$


$$v_1 = 0$$

$$v_1 = 0V$$

$$v_2 = 24V$$

$$i_1 = 0A \quad i_3 = 6A$$

$$i_2 = 0A \quad i_4 = -12A$$

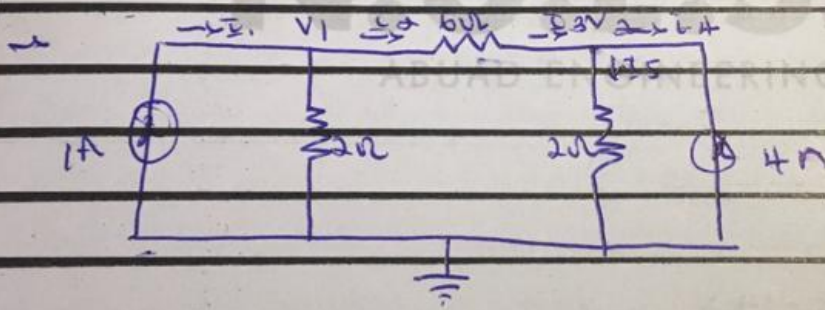

From Node 1

$$i_1 = i_2 = i_3$$

$$i = \frac{v_1 - v_2}{6} + \frac{v_1}{2}$$

$$6 = v_1 - v_2 + 3v_1$$

$$6 = 4v_1 - v_2 \quad (1)$$

$$V_3 = 4 + 10i$$

$$\frac{V_1 - V_2}{6} = 4 + \frac{V_2}{4}$$

$$7[V_1 - V_2] = 168 + 6V_2$$

$$168 = 7V_1 - 13V_2 \quad \dots (1)$$

From equation 1

$$V_2 = 4V_1 - 6$$

Equating $(V_2 = 4V_1 - 6)$ into eqn (1)

$$168 = 7V_1 - 13(4V_1 - 6)$$

$$168 = 7V_1 - 52V_1 + 78$$

$$90 = -45V_1$$

$$V_1 = 90 / -45$$

$$V_1 = -2V$$

Substituting $V_1 = -2$ into eqn (1)

$$6 = 4(-2) - V_2$$

$$6 = -8 - V_2$$

$$V_2 = -8 - 6$$

$$V_2 = -14V$$


$$V_1 = -2V ; V_2 = -14V$$

Calculating current through the resistor

$$i_2 = \frac{V_1 - V_2}{6} = \frac{-2 + 14}{6} = 2A$$

$$i_3 = \frac{V_1}{2} = \frac{-2}{2} = -1A$$
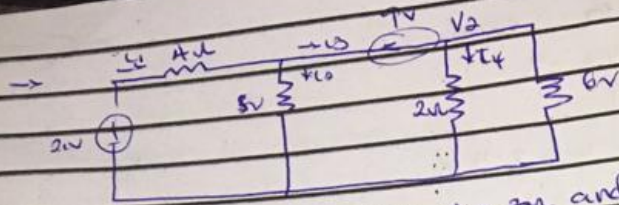
$$i_4 = \frac{V_2}{4} = \frac{-14}{4} = -3.5A$$



Find the current through the 3Ω and 2Ω resistor

Using KCL at Node 1

$$i_1 + i_2 + i_3 + i_4 = 0$$

$$\frac{V_1 - 2}{15} + \frac{V_1}{5} + \frac{V_2}{2} + \frac{V_2}{6} = 0$$

$$7V_1 + 8V_2 - 63 = 0 \quad \dots (1)$$

taking KVL for loop

$$-V_1 - 7 + V_2 = 0$$

$$-V_1 + V_2 = 7 \quad \dots (2)$$

$$7V_1 + 8V_2 = 63 \quad \dots (1)$$

$$-V_1 + V_2 = 7 \quad \dots (2)$$

$$7V_1 + 8V_2 = 63$$

$$-7V_1 + 7V_2 = 63$$

$$11V_2 = 126$$

$$\text{From equation 2} = -V_1 + V_2 = 7$$

$$V_2 = 7 + V_1$$

Substituting into equation 1

$$7V_1 + 8[7 + V_1] = 63$$

$$7V_1 + 72 + 8V_1 = 63$$

$$15V_1 = 63 - 72$$

$$15V_1 = -9$$

$$V_1 = -9/15$$

$$V_1 = -0.6V$$

Equating $V_1 = 0.6$ in equation (1)

$$-I - 0.6I + V_2 = 9$$

$$0.4V_2 = 9$$

$$V_2 = 9 / 0.4 = 22.5V$$


$$V_1 = -0.6V$$

$$V_2 = 22.5V$$

Calculating current through 3Ω and 2Ω

$$I_3 = \frac{V_1}{3} = \frac{-0.6}{3} = -0.2A \text{ at } 3\Omega$$
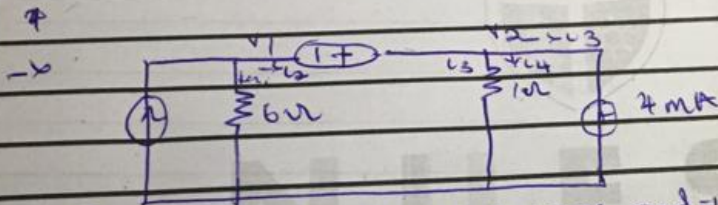
$$I_4 = \frac{V_2}{4} = \frac{22.5}{4} = 5.625A \text{ at } 2\Omega$$



Find the nodes at the voltage and the current through 6Ω and 12Ω resistor

From node 1,

$$\text{Take } V_1 - V_2 = 6V = \text{sum } I_3$$

$$6mA = I_1 + I_2$$

$$6mA = \frac{V_1 - 0}{6} + \frac{(V_1 - V_2)}{12}$$

$$36 = V_1 + 6(V_1 - V_2)$$

$$36 = V_1 + 6V_1 - 6V_2$$

$$36 = 7V_1 - 6V_2 \quad \text{--- (1)}$$

From Node 2

$$I_3 = I_4 + I_5$$

$$V_1 - V_2 = 4 \text{ mA} + V_2 - 0 / 12$$

$$12[V_1 - V_2] = 48 + V_2$$

$$48 = 12V_1 - 12V_2 - V_2 \quad \therefore$$

$$48 = 12V_1 - 13V_2 \quad \dots (10)$$

Solving V_1 and V_2 simultaneously

$$V_1 = 9.5 \text{ V and } V_2 = 5.1 \text{ V}$$

Calculating current through the 6Ω resistor

$$i = \frac{V_1}{6} = \frac{9.5}{6} = 1.58 \text{ A}$$

$$V_0 = V_1 - V_2 = 9.5 - 5.1 = 4.4 \text{ mV}$$

Current through 12Ω

$$i_2 = \frac{V_2}{12} = \frac{5.1}{12} = 0.43 \text{ A}$$

$$V_1 = 9.5 \text{ V}$$

$$V_2 = 5.1 \text{ V}$$

$$i_1 = 1.58 \text{ A}$$

$$i_2 = 0.43 \text{ A}$$